
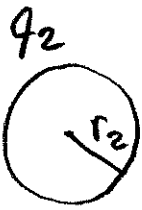


# Devre Teorileri

(1)

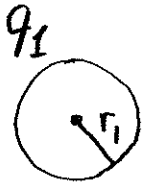

Küreler birbirlerine dokundurulursa üzerlerindeki yeni yükler

$$q_T = q_1 + q_2$$
$$= \bar{q}_1 + \bar{q}_2$$


$$\bar{q}_1 = q_T \frac{r_1}{r_1 + r_2}, \quad \bar{q}_2 = q_T \frac{r_2}{r_1 + r_2}$$

$$F = k \frac{q_1 q_2}{d^2}$$

Yitme veya çekme kuvveti.


Küreler ikiside pozitif veya ikiside negatif ise birbirlerini iter. Biri pozitif diğeri negatif ise birbirlerini çekerler.

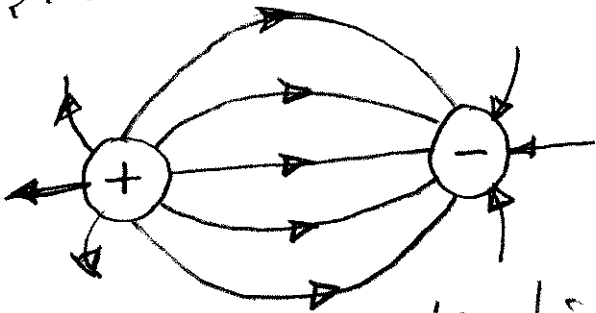İki küre birbirlerine bir tel ile bağlansaydı yükler dengeye gelene kadar telden elektrik akımı geçirdi. Kürelerin içinde elektrik alan sıfırdır. Yüzeyinde veya dışında ise  $E = k \cdot q / d^2$ .



Kürenin yükü + ise elektrik alan yönü dışarı, - ise içeri doğrudur.

Voltaj ise yönlü bir büyüklük olmayıp formülü
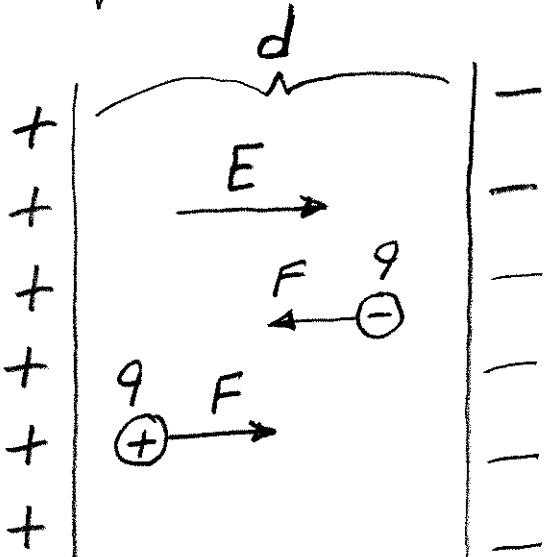
$$V = E \cdot d = k \frac{q}{d}$$


Farklı yüklü iki levha arasındaki elektrik alan şiddeti sabittir.

$$V = E \cdot d \Rightarrow E = V/d$$

$$F = q \cdot E = q \frac{V}{d}$$

$$i(t) = \frac{dq(t)}{dt}, \quad q(t) = \int_{-\infty}^t i(z) dz = q(t_0) + \int_{t_0}^t i(z) dz \quad (2)$$

Birim zamanda geçen yük miktarına akım denir.

$$1 \text{ Amper} = \frac{1 \text{ Coulomb}}{1 \text{ saniye}} \quad 1 \text{ sn'de } 1 \text{ C'luk yük geçmesi}$$

$$1 \text{ A'lik akım manasına gelir.}$$

$$w(t) = \int_{-\infty}^t p(z) dz = w(t_0) + \int_{t_0}^t p(z) dz \quad \text{İş birimi}$$

$$\text{Joule (J)'dir.}$$

$$p(t) = \frac{dw(t)}{dt} = \frac{dw(t)}{dq(t)} \frac{dq(t)}{dt} = V(t) \cdot i(t)$$

$$\text{Güç birimi Watt (W)'dir. } 1 \text{ W} = 1 \text{ V} \times 1 \text{ A} = 1 \text{ VA}$$

$$1 \text{ Volt} = \frac{1 \text{ Joule}}{1 \text{ Coulomb}} \quad 1 \text{ C'luk yük } 1 \text{ J'luk iş yaparsa}$$

$$1 \text{ V'luk voltaj manasına gelir.}$$

$$1 \text{ wh} = 3600 \text{ J} \quad 1 \text{ WattSaatt } 3600 \text{ Joule'dir.}$$

Bir lamba üzerinden 1 dakika boyunca 2 A'lik akım geçmektedir. Lamba 15 kJ'luk enerjiyi ısı ve ışık olarak dışarı veriyor. Lamba üzerindeki voltajı bul.

$$q = i \cdot t = 2 \text{ A} \times 60 \text{ sn} = 120 \text{ C}$$

$$V = \frac{w}{q} = \frac{15 \text{ kJ}}{120 \text{ C}} = \frac{15000 \text{ J}}{120 \text{ C}} = 125 \text{ V}$$


25 W'lık bir lamba 8 saatte kaç kJ'luk enerji tüketir.

$$W = p \cdot t = 25 \text{ W} \times 8 \text{ h} = 200 \text{ wh}$$

$$= 200 \times 3600 \text{ J}$$

$$= 720000 \text{ J}$$

$$= 720 \text{ kJ}$$

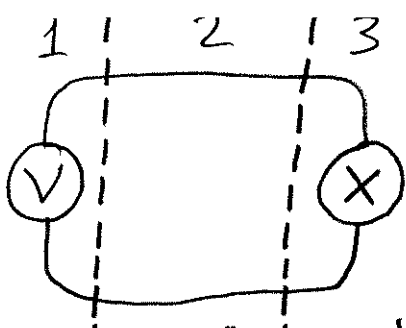







- 1- Kaynak (Üreteç)  
2- iletim Hattı (Tel)  
3- Yük (Tüketeci)

(3)


## Elektrik Devresi

Bir elektrik devresinde üretilen enerji ile tüketilen enerji birbirlerine eşittir. Yani, devredeki toplam enerji sıfırdır. Elektronların hareket yönü ise tanımlanan akım yönüne zıttır.  $I = -I_e$ .

## Kaynaklar

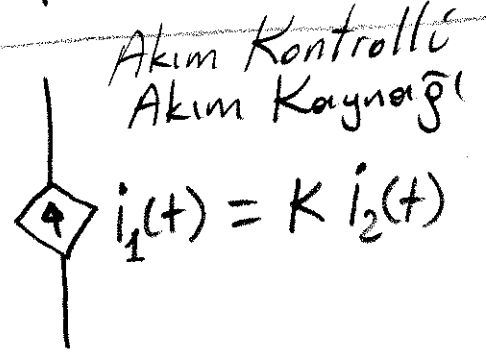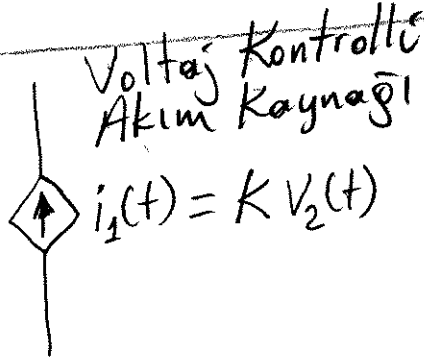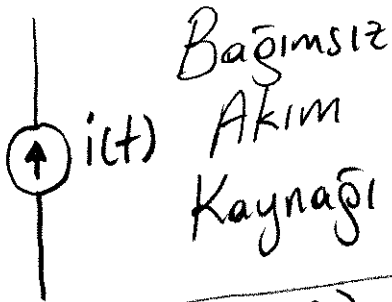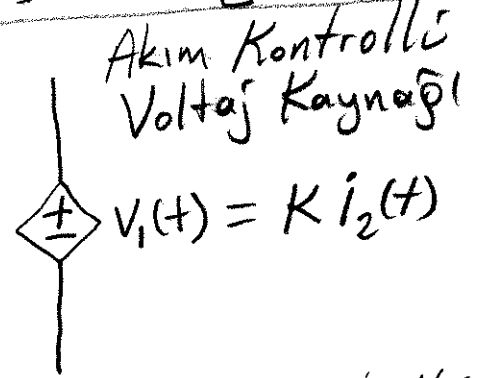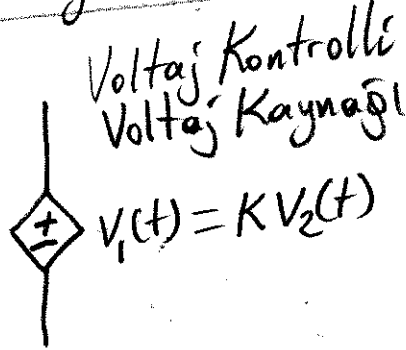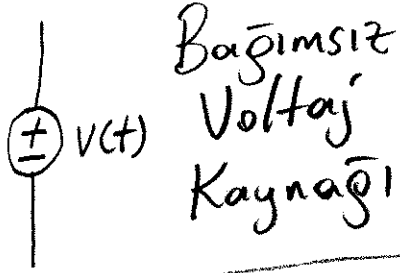

## Direnç (R)

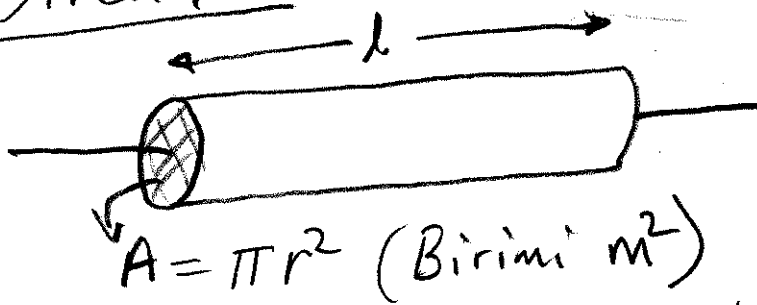

$$R = \int \frac{l}{A} = \frac{l}{\sigma \cdot A}$$

Özdirenç  $\Omega \cdot m$       İletkenlik  $S/m$

$$G = \frac{1}{R}$$





↓ Geriçekenlik  
mho,  $\Omega^{-1}$   
Simens, S

↓ Direnç  
Ohm,  $\Omega$

$l = 1km$ ,  $r = 1mm$  olan bakır telin direncini bulunuz.

$$\sigma_{cu} = 5.8 \times 10^7 S/m$$

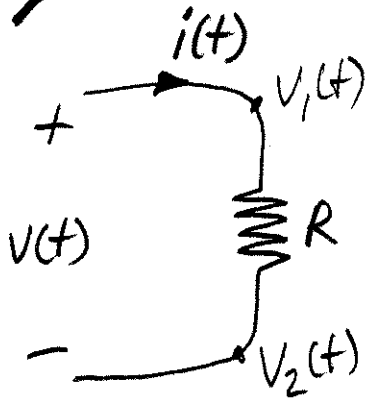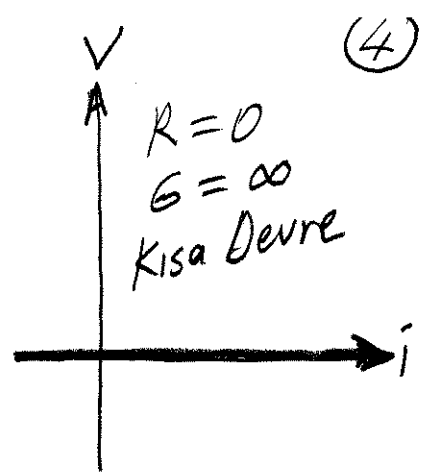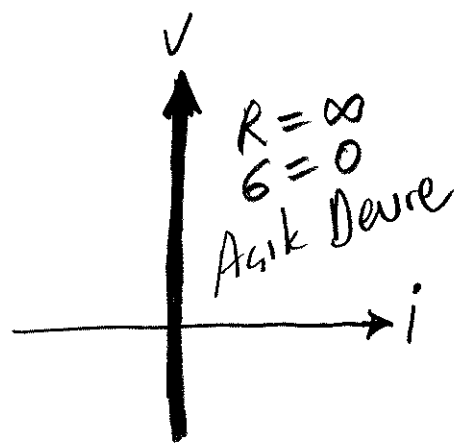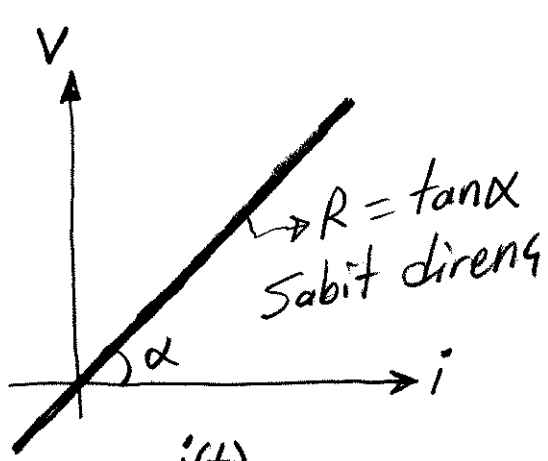
$$R_{cu} = \frac{l}{\sigma_{cu} \cdot A} = \frac{10^3}{5.8 \times 10^7 \times \pi \times 10^{-6}} \approx 5.49 \Omega$$



$$V(t) = V_1(t) - V_2(t) > 0$$

$$V(t) = R i(t) \quad p(t) = V(t) \cdot i(t)$$

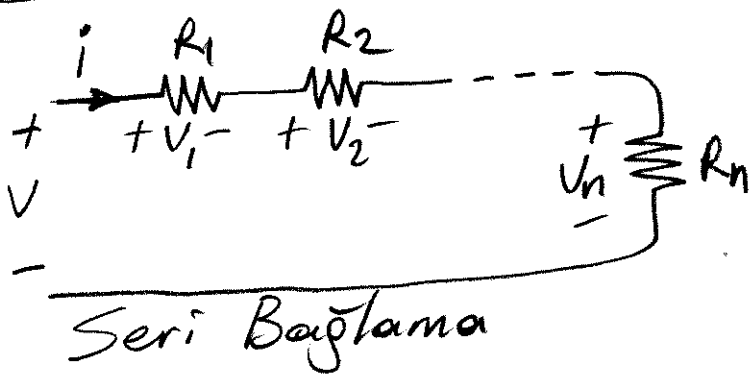
$$i(t) = G V(t) \quad = R i^2(t) = \frac{V^2(t)}{R}$$



$$i = i_1 = i_2 = \dots = i_n$$

$$V = V_1 + V_2 + \dots + V_n$$

$$R_T = R_1 + R_2 + \dots + R_n$$

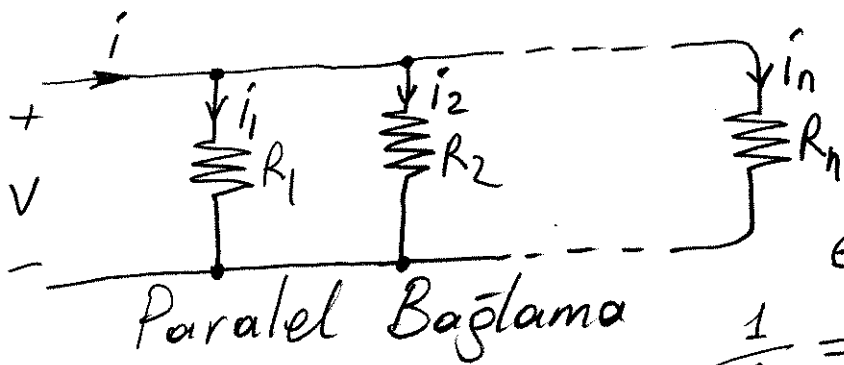


$$V = V_1 = V_2 = \dots = V_n$$

$$i = i_1 + i_2 + \dots + i_n$$

$$G_T = G_1 + G_2 + \dots + G_n$$
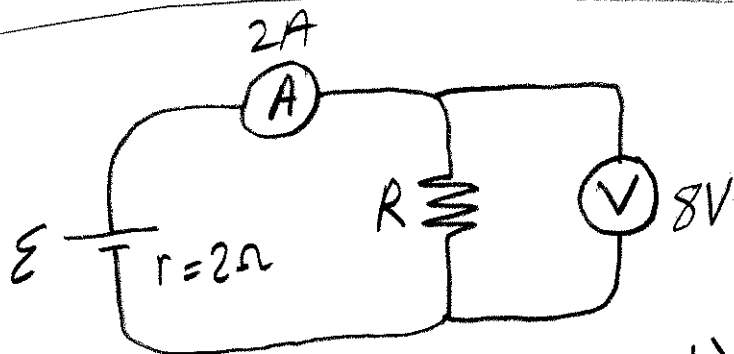
$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$




$\mathcal{E}$  (Elektromotor Kuvvet - Emk) bulunuz.

Ampermetre 2A, Voltmetre 8V ölçüyor.

$$R = \frac{V}{I} = \frac{8V}{2A} = 4\Omega$$

$$\begin{aligned} \mathcal{E} &= (R + r) I \\ &= 6\Omega \times 2A \\ &= 12V \end{aligned}$$

(5)

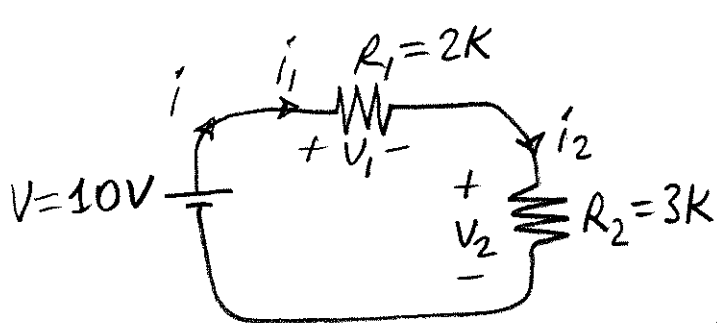Seri Bağlama

$$R_T = R_1 + R_2 = 2K + 3K = 5K$$

$$i = i_1 = i_2 = \frac{V}{R_T} = \frac{10V}{5K} = 2mA$$

$$V_1 = R_1 i_1 = 2K \times 2mA = 4V$$


$$P_1 = V_1 i_1 = 4V \times 2mA = 8mW$$

$$V_2 = R_2 i_2 = 3K \times 2mA = 6V$$

$$P_2 = V_2 i_2 = 6V \times 2mA = 12mW$$

$$P_{\text{tut}} = V i = 10V \times 2mA = 20mW$$

$$P_{\text{tut}} = P_1 + P_2 = 8mW + 12mW = 20mW$$

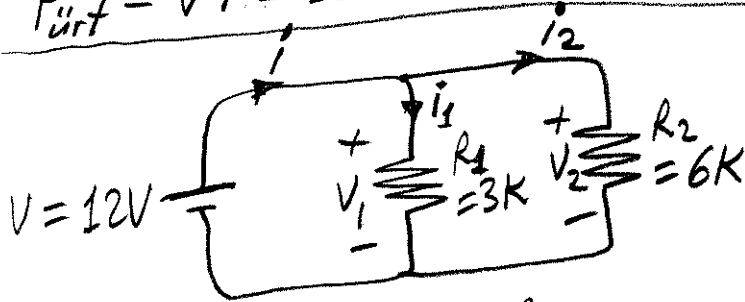Paralel Bağlama

$$V = V_1 = V_2 = 12V$$

$$i_1 = \frac{V_1}{R_1} = \frac{12V}{3K} = 4mA$$

$$i_2 = \frac{V_2}{R_2} = \frac{12V}{6K} = 2mA$$

$$i = i_1 + i_2 = 6mA$$

$$R_{eq} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2} = \frac{3K \times 6K}{3K + 6K} = 2K$$


$$i = \frac{V}{R_{eq}} = \frac{12V}{2K} = 6mA$$

$$P_1 = V_1 i_1 = 12V \times 4mA = 48mW$$

$$P_{\text{tut}} = V i = 12V \times 6mA = 72mW$$

$$P_2 = V_2 i_2 = 12V \times 2mA = 24mW$$
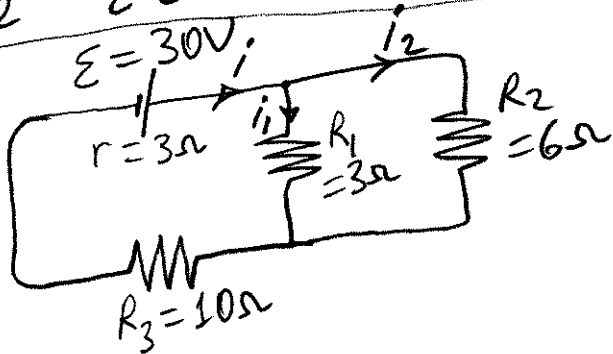
$$P_{\text{tut}} = P_1 + P_2 = 48mW + 24mW = 72mW$$



Üretecin uçları arasındaki potansiyel farkı  $V = ?$

$$R_T = r + R_3 + R_1 \parallel R_2$$

$$= 3\Omega + 10\Omega + 3\Omega \parallel 6\Omega$$


$$= 15\Omega$$


$$i = \frac{\mathcal{E}}{R_T} = \frac{30V}{15\Omega} = 2A$$

$$V = \mathcal{E} - r i = 30V - 3\Omega \times 2A = 24V$$

$$V_a + 8V - 5\Omega \times 3A = V_b$$

$$V_{ab} = V_a - V_b = 15V - 8V = 7V$$

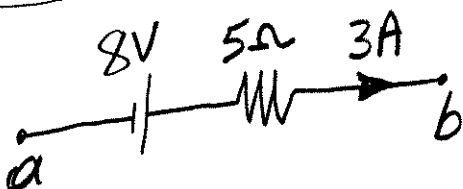

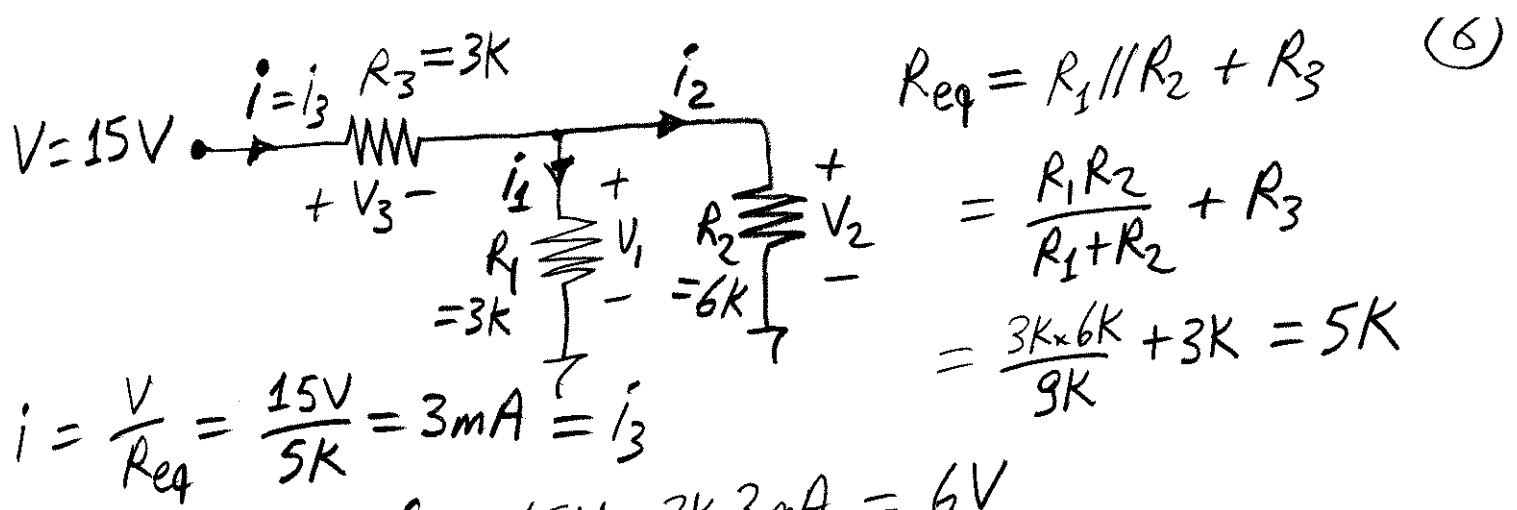

$$R_{eq} = R_1 // R_2 + R_3$$

$$= \frac{R_1 R_2}{R_1 + R_2} + R_3$$

$$= \frac{3k \times 6k}{9k} + 3k = 5k$$

$$i = \frac{V}{R_{eq}} = \frac{15V}{5k} = 3mA = i_3$$

$$V_1 = V_2 = V - R_3 i_3 = 15V - 3k \times 3mA = 6V$$

$$i_1 = \frac{V_1}{R_1} = \frac{6V}{3k} = 2mA$$

$$i_2 = \frac{V_2}{R_2} = \frac{6V}{6k} = 1mA$$

$$i = i_1 + i_2 = 3mA$$


$$P_1 = V_1 i_1 = 6V \times 2mA = 12mW$$

$$P_2 = V_2 i_2 = 6V \times 1mA = 6mW$$

$$P_3 = V_3 i_3 = 9V \times 3mA = 27mW$$

$$P_{port} = Vi = 15V \times 3mA = 45mW$$

$$P_{tot} = P_1 + P_2 + P_3 = 45mW$$

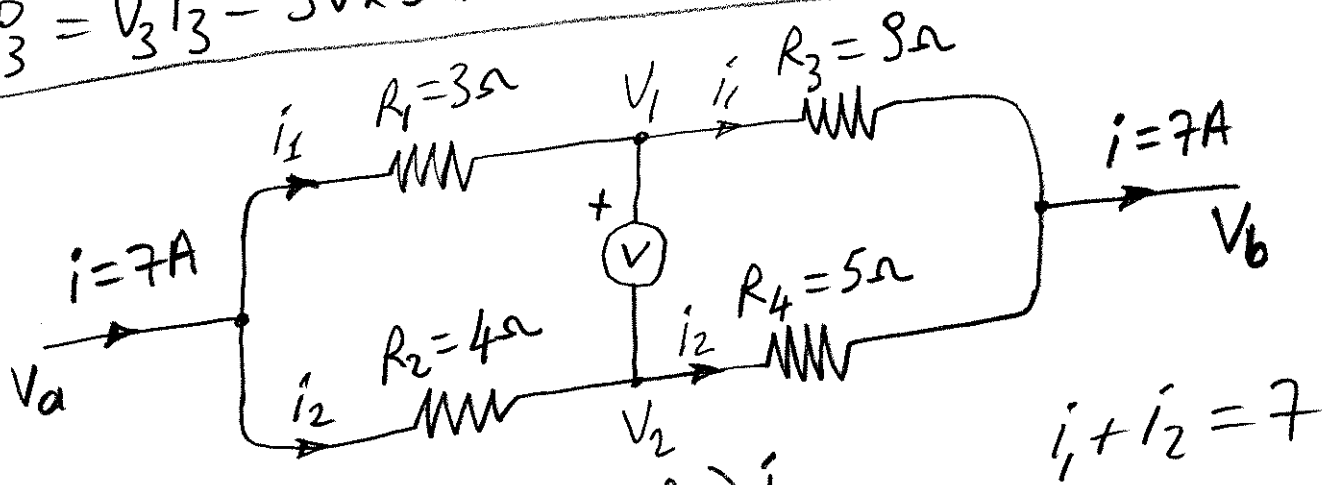

$$V_{ab} = (R_1 + R_3) i_1 = (R_2 + R_4) i_2$$

$$12i_1 = 9i_2 \Rightarrow 4i_1 - 3i_2 = 0$$

$$i_1 + i_2 = 7$$

$$4i_1 - 3i_2 = 0$$

$$3i_1 + 3i_2 = 21$$

$$7i_1 = 21$$

$$i_1 = 3A$$

$$i_2 = 7 - i_1 = 4A$$



$$V_a = V_1 + R_1 i_1 = V_2 + R_2 i_2$$

$$V = V_1 - V_2 = R_2 i_2 - R_1 i_1$$

$$V = 4\Omega \times 4A - 3\Omega \times 3A$$

$$= 16V - 9V$$


$$= 7V$$

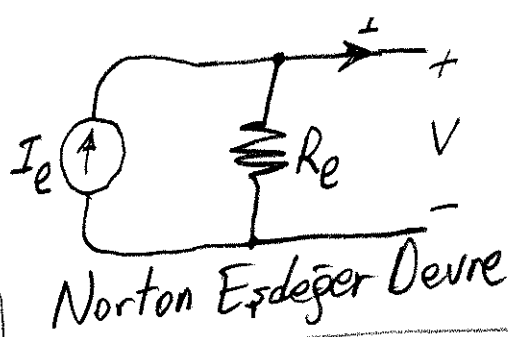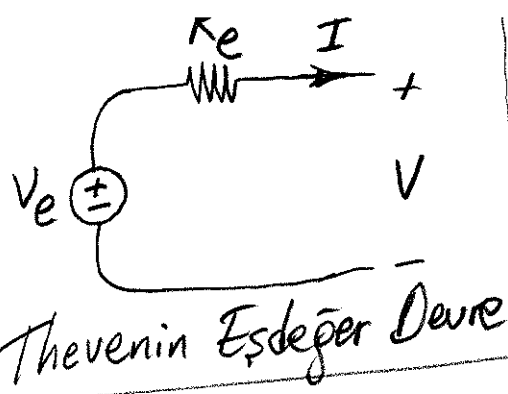


$$V = V_e - R_e I \quad (7)$$

$$= R_e (I_e - I)$$

$$V_e = R_e I_e$$

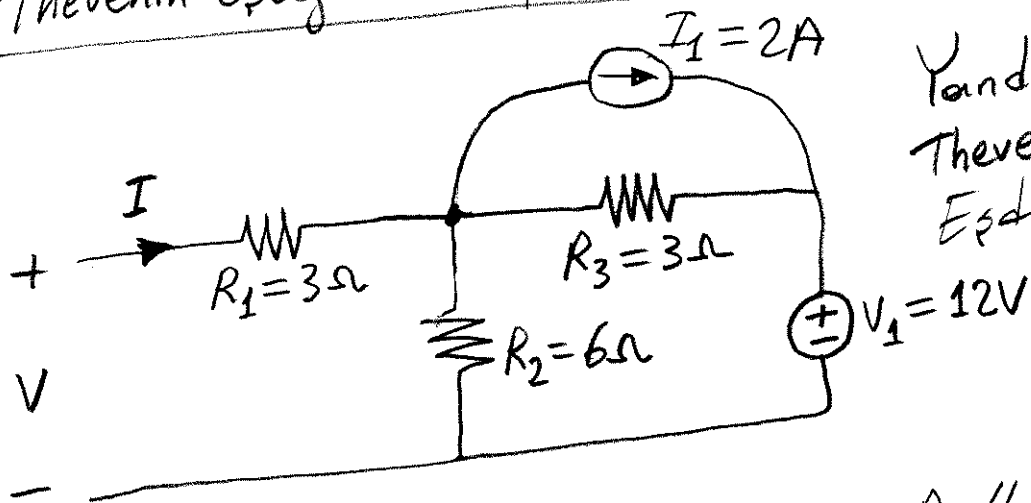

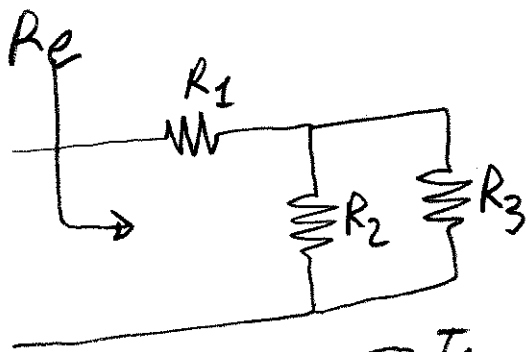
Yanda verilen devrenin Thevenin ve Norton Eşdeğerini bulunuz.



$$R_e = R_1 + R_2 \parallel R_3$$

$$= R_1 + \frac{R_2 R_3}{R_2 + R_3}$$
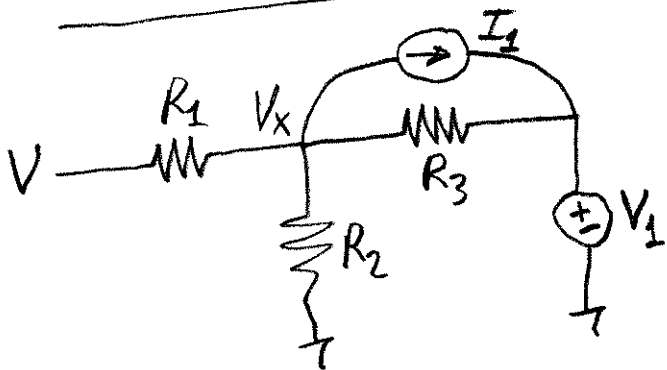
$$= 3\Omega + \frac{6\Omega \times 3\Omega}{9\Omega} = 5\Omega$$





$$I = \frac{V - V_x}{R_1} = \frac{V_x}{R_2} + \frac{V_x - V_1}{R_3} + I_1$$


$$\frac{V - V_x}{3} = \frac{V_x}{6} + \frac{V_x - 12}{3} + 2$$

$$2V - 2V_x = V_x + 2V_x - 24 + 12$$

$$I = \frac{V - V_x}{R_1} = \frac{V - \frac{2V + 12}{5}}{3} = \frac{V - 4}{5} \rightarrow V_e$$

$$V_x = \frac{2V + 12}{5}$$

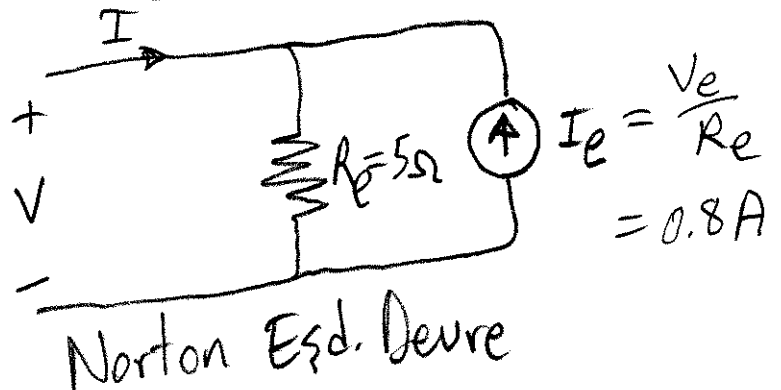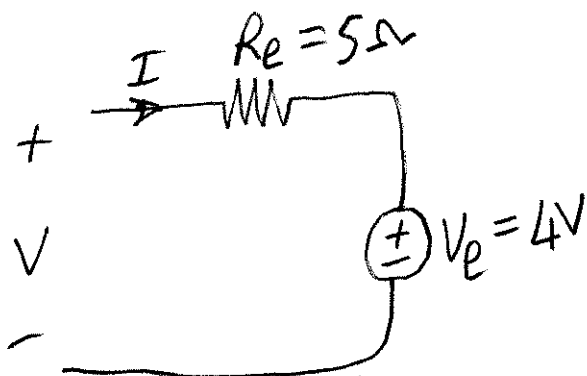

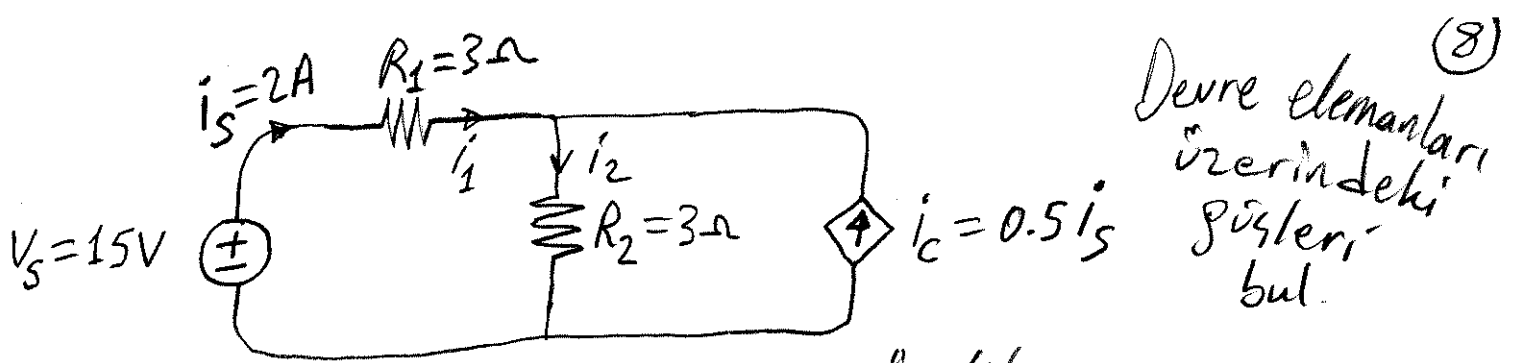

$$P_S = V_S i_S = 15V \times 2A = 30W \text{ Üretilen}$$

$$i_1 = i_S = 2A \quad i_c = 0.5 i_S = 1A \quad i_2 = i_1 + i_c = 3A$$


$$P_1 = R_1 i_1^2 = 3\Omega \times (2A)^2 = 12W \text{ Tüketilen}$$

$$P_2 = R_2 i_2^2 = 3\Omega \times (3A)^2 = 27W \text{ Tüketilen}$$

$$V_c = V_2 = R_2 i_2 = 3\Omega \times 3A = 9V$$

$$P_c = V_c \cdot i_c = 9V \times 1A = 9W \text{ Üretilen}$$
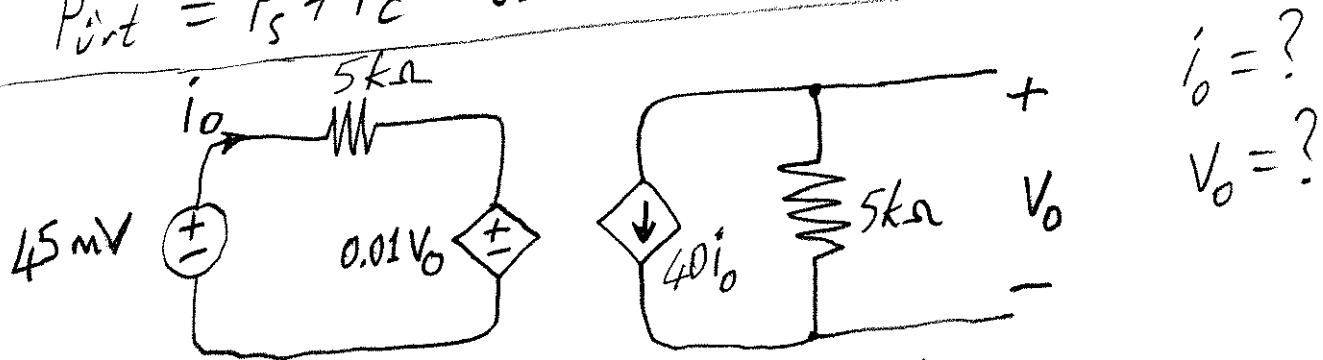
$$P_{\text{int}} = P_S + P_c = 39W \quad P_{\text{tik}} = P_1 + P_2 = 39W$$



$$V_o = -5k\Omega \times 40 i_o = -0.2 \times 10^6 i_o$$

$$45mV - 5k\Omega \times i_o - 0.01 V_o = 0$$

$$45 \times 10^{-3} - 5 \times 10^3 i_o - 10^{-2} V_o = 0$$

$$45 - 5 \times 10^6 i_o - 10 V_o = 0$$

$$45 - 5 \times 10^6 i_o + 2 \times 10^6 i_o = 0$$

$$3 \times 10^6 i_o = 45$$

$$i_o = 15 \mu A$$


$$V_o = -0.2 \times 10^6 i_o$$

$$= -0.2 \times 10^6 \times 15 \times 10^{-6} V$$

$$= -3V$$


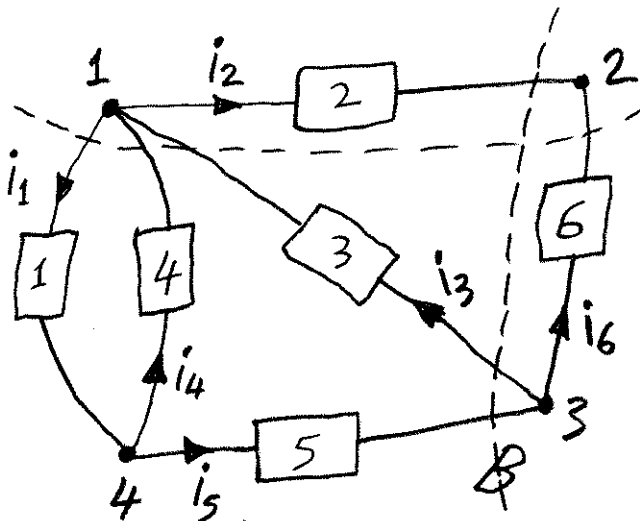
# Kirchhoff'un Akım Yasası (KCL) - Nokta Analiz (9)



Gıkan akım pozitif, giren akım negatif alınır. Her nokta için akımların cebirsel toplamı sıfırdır.

$$① i_1 + i_2 - i_3 - i_4 = 0$$

$$② -i_2 - i_6 = 0$$


$$③ i_3 - i_5 + i_6 = 0$$

$$④ -i_1 + i_4 + i_5 = 0$$

$$① i_1 - i_3 - i_4 - i_6 = 0$$

1 ile 2.denklem birleşir
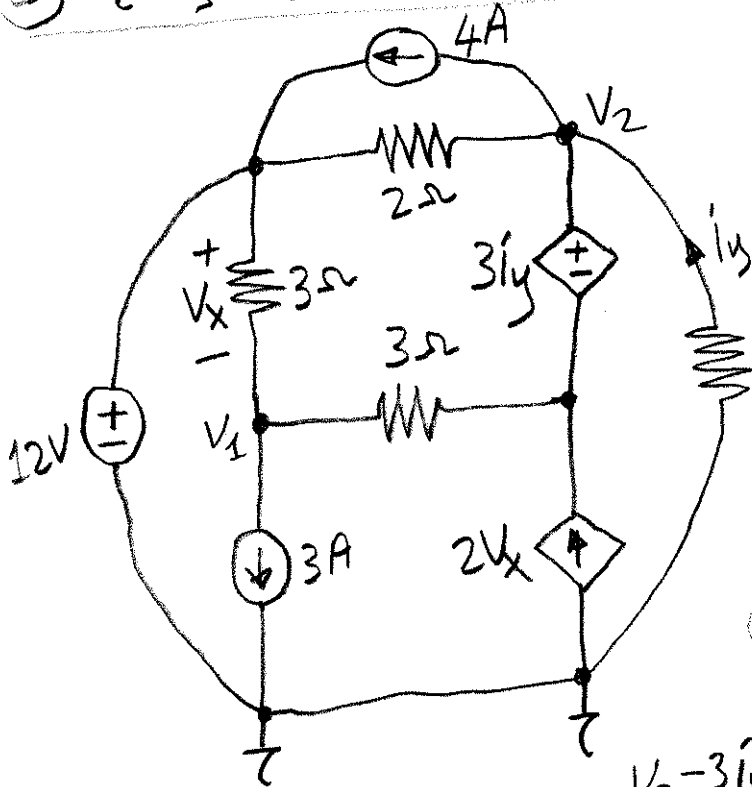
$$③ i_2 - i_3 + i_5 = 0, 2 \text{ ile } 3.\text{denklem birleşir. Eksi ile sarpılır.}$$



$$V_x = ? \quad i_y = ?$$

6 noktadan sadece 2'si alınır.

$$V_1 = 12 - V_x, \quad V_2 = -2i_y$$

$$3 - \frac{V_x}{3} + \frac{V_1 - (V_2 - 3i_y)}{3} = 0$$

$$9 - V_x + V_1 - V_2 + 3i_y = 0$$

$$9 - V_x + 12 - V_x + 2i_y + 3i_y = 0$$

$$2V_x - 5i_y = 21 \quad 1.\text{denklem}$$

$$4 + \frac{V_2 - 12}{2} - i_y - 2V_x + \frac{V_2 - 3i_y - V_1}{3} = 0$$


$$4 + \frac{-2i_y - 12}{2} - i_y - 2V_x + \frac{-2i_y - 3i_y - 12 + V_x}{3} = 0 \quad 2.\text{denklem}$$

$$4 - i_y - 6 - i_y - 2V_x - \frac{5}{3}i_y - 4 + \frac{V_x}{3} = 0 \Rightarrow 5V_x + 11i_y = -18$$

$$\begin{bmatrix} 2 & -5 & 21 \\ 5 & 11 & -18 \end{bmatrix} \sim \begin{bmatrix} 2 & -5 & 21 \\ 9 & 1 & 24 \end{bmatrix} \sim \begin{bmatrix} 47 & 0 & 141 \\ 9 & 1 & 24 \end{bmatrix}$$

$$\sim \begin{bmatrix} 1 & 0 & 3 \\ 9 & 1 & 24 \end{bmatrix} \sim \begin{bmatrix} 1 & 0 & 3 \\ 0 & 1 & -3 \end{bmatrix} \quad V_x = 3V, \quad i_y = -3A$$
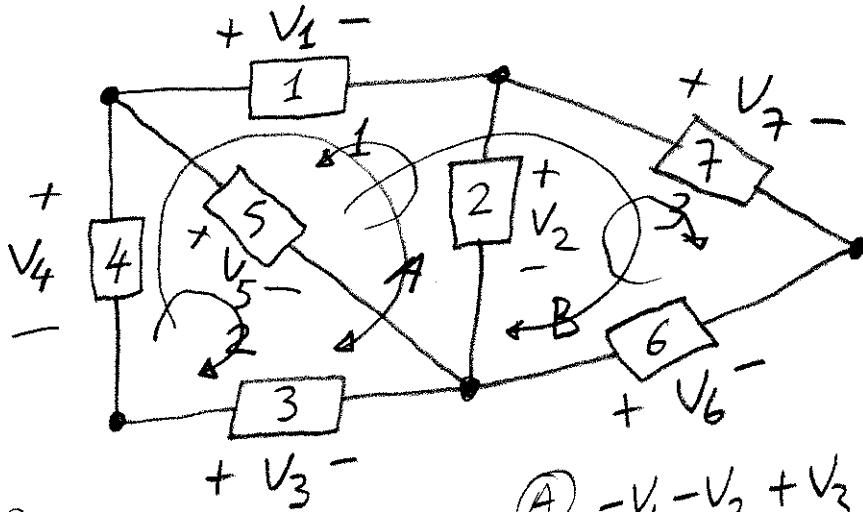
# Kirchhoff'un Gerilim Yasası (KVL) - Mesh Analiz (10)



Bir göz içinde belirli bir yönde alınan tüm gerilimlerin toplamı sıfırdır.

$$\textcircled{1} V_1 + V_2 - V_5 = 0$$

$$\textcircled{2} V_3 + V_4 - V_5 = 0$$

$$\textcircled{3} V_2 + V_6 - V_7 = 0$$

$$\textcircled{A} -V_1 - V_2 + V_3 + V_4 = 0$$

1 ile 2. denklemin birleşir.

$$\textcircled{B} -V_1 + V_5 + V_6 - V_7 = 0$$

1 ile 3. denklemin birleşir.

$$V_x = ? \quad i_y = ?$$

$$I_1 = 3A \quad I_2 = 4A$$


$$I_3 = 2V_x$$

$$I_3 + I_5 = -i_y$$

$$I_5 = -2V_x - i_y$$

$$I_1 - I_4 = V_x/3$$

$$I_4 = 3 - V_x/3$$

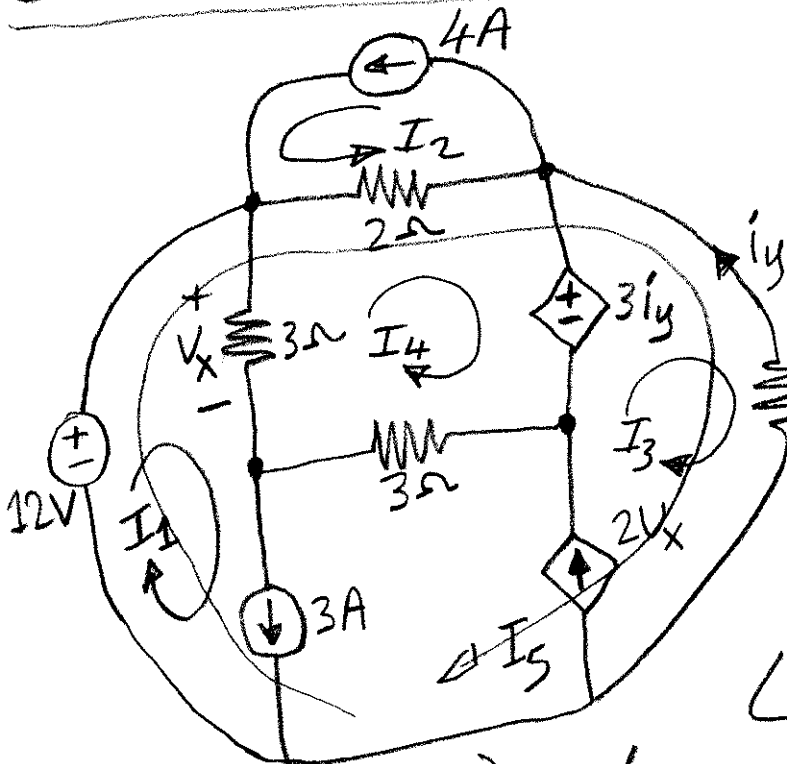

5 gözden sadece 2'si alınır.  
(Akım kaynağı olmayanlar)

$$12 - 2(I_2 + I_4 + I_5) + 2i_y = 0$$


$$12 - 2(4 + 3 - \frac{V_x}{3} - 2V_x - i_y) + 2i_y = 0 \Rightarrow 7V_x + 6i_y = 3$$

$$V_x - 2(I_2 + I_4 + I_5) - 3i_y - 3I_4 = 0 \Rightarrow 20V_x - 3i_y = 69$$

$$\begin{bmatrix} 7 & 6 & 3 \\ 20 & -3 & 69 \end{bmatrix} \sim \begin{bmatrix} 1 & 0 & 3 \\ 0 & 1 & -3 \end{bmatrix} \quad V_x = 3V \quad i_y = -3A$$

# Süper Pozisyon

(11)

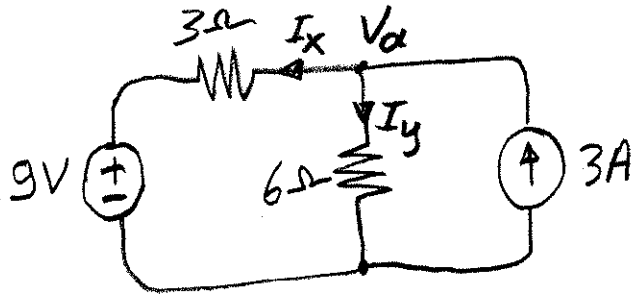


$$\frac{V_a - 9}{3} + \frac{V_a}{6} = 3 \quad \text{6 ile çarp}$$

$$2V_a - 18 + V_a = 18$$


$$3V_a = 36 \Rightarrow V_a = 12V$$

$$I_x = \frac{V_a - 9}{3} = 1A$$

$$I_y = \frac{V_a}{6} = 2A$$

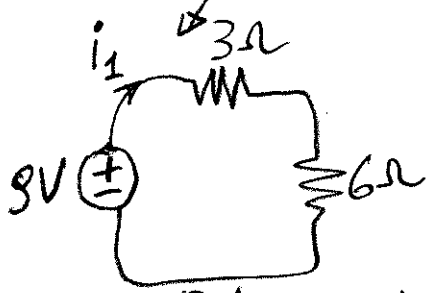
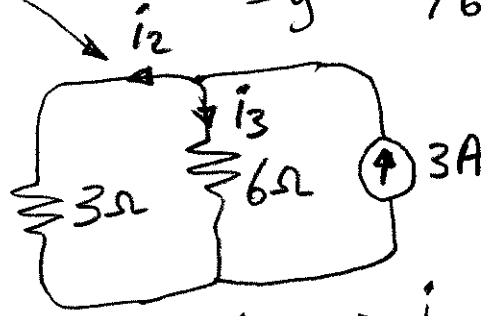
$$i_1 = \frac{9V}{3\Omega + 6\Omega} = 1A$$



$$3i_2 = 6i_3 \Rightarrow i_2 - 2i_3 = 0$$

$$i_2 + i_3 = 3$$

$$i_2 = 2A \quad i_3 = 1A$$

$$I_x = i_2 - i_1 = 2A - 1A = 1A$$

$$I_y = i_1 + i_3 = 1A + 1A = 2A$$

## Dirençin Sıcaklıkla Değişimi

Madde	$\alpha$ ( $1/^\circ C$ )
Bakır	0.0039
Altın	0.0034
Gümüş	0.0038
Silikon	-0.0075
Karbon	-0.0005

$$R_2 = R_1 (1 + \alpha (t_2 - t_1))$$

$\alpha$  : Direnç Sıcaklık Katsayısı  
Cu, Au, Ag elementleri ısıtıldıkça dirençleri artar, Si ve C ise azalır.

Bir telin  $20^\circ C$ 'deki direnci  $5\Omega$ ,  $60^\circ C$ 'deki direnci ise  $6\Omega$  olsun.  $\alpha = ?$

$$R_2 = R_1 (1 + \alpha (t_2 - t_1))$$

$$6 = 5 (1 + 40\alpha)$$

$$\alpha = \frac{1}{200} = 0.005 \text{ } 1/^\circ C$$

$$t_1 = 20^\circ C \quad t_2 = 60^\circ C$$

$$R_1 = 5\Omega \quad R_2 = 6\Omega$$

Bir lambanın direnci  $24^{\circ}\text{C}$ 'de  $250\Omega$ 'dur. Lambanın akkor (12) haline geldiğindeki (yani  $1524^{\circ}\text{C}$ ) direncini bulunuz. Lambadaki telin direnç sıcaklık katsayısı  $0.004\text{ }^{\circ}\text{C}^{-1}$  olsun.

$$t_1 = 24^{\circ}\text{C} \quad t_2 = 1524^{\circ}\text{C}$$

$$R_1 = 250\Omega \quad R_2 = ?$$

$$\alpha = 0.004\text{ }^{\circ}\text{C}^{-1}$$

$$R_2 = R_1 (1 + \alpha(t_2 - t_1)) = 250\Omega (1 + 0.004 \times 1500) = 1750\Omega$$

Direnci  $20\Omega$  olan bir ısıtıcı  $220\text{V}$ 'luk bir gerilime bağlanmıştır. Isıtıcıdan geçen akımı, ısıtıcının gücünü, ısıtıcının 5 dakikada vereceği ısı enerjisini Joule ve Cal cinsinden bulunuz.

$$I = \frac{V}{R} = \frac{220\text{V}}{20\Omega} = 11\text{A}$$

$$W = P \cdot t = 2420\text{W} \times 5 \times 60\text{sn}$$

$$= 726000\text{J} = 726\text{kJ}$$

$$P = VI = 220\text{V} \times 11\text{A}$$


$$= 2420\text{W} = 2.42\text{kW}$$

$$1\text{Joule} \Rightarrow 0.24\text{Cal}$$

$$W = 726000\text{J} \times 0.24\text{Cal/J}$$

$$= 174240\text{Cal} = 174.24\text{kCal}$$

Maksimum Güç Aktarımı

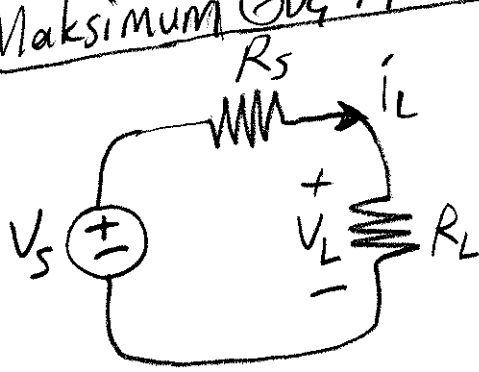

$$I_L = \frac{V_s}{R_s + R_L}$$

$$P_L = R_L I_L^2 = \frac{R_L V_s^2}{(R_s + R_L)^2}$$

$\frac{dP_L}{dR_L} = 0$  olunca max. güç aktarımı olur.

$$\frac{dP_L}{dR_L} = \frac{V_s^2 (R_s + R_L)^2 - R_L V_s^2 \cdot 2(R_s + R_L)}{(R_s + R_L)^4}$$

$$= \frac{V_s^2 (R_s + R_L) - 2R_L V_s^2}{(R_s + R_L)^3} = \frac{(R_s - R_L) V_s^2}{(R_s + R_L)^3} = 0$$

$R_s = R_L$  olunca max. güç aktarımı olur.




$$P_L = R_L I_L^2$$

$$P_T = R_T I_L^2 = 2R_L I_L^2 = 2P_L$$

$$R_T = R_s + R_L = 2R_L$$

$$P_L = P_T / 2$$

1kWh  $\rightarrow$  864 kCal

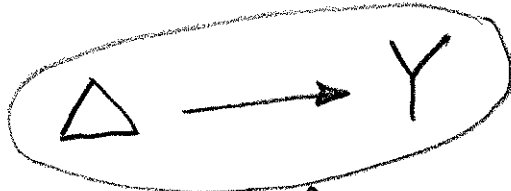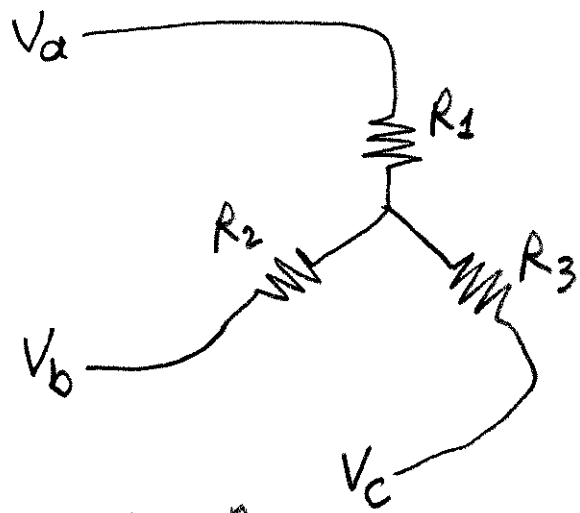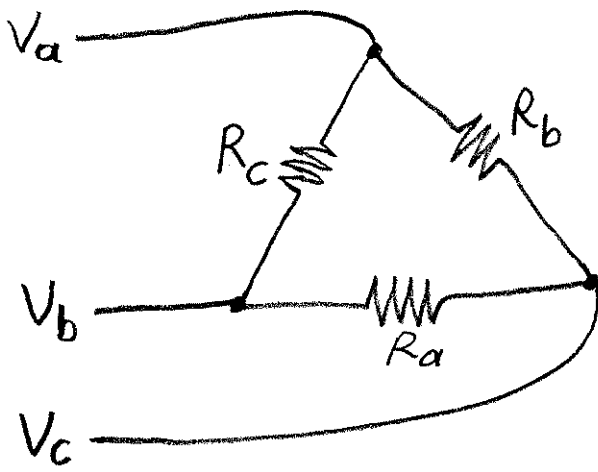


$$R_{\Delta} = R_a + R_b + R_c$$

$$R_1 = \frac{R_b R_c}{R_{\Delta}}$$

$$R_2 = \frac{R_c R_a}{R_{\Delta}}$$

$$R_3 = \frac{R_a R_b}{R_{\Delta}}$$

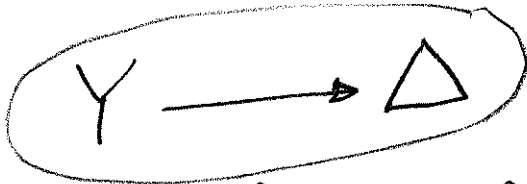


$$R_Y = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_3}$$

$$R_a = R_Y / R_1$$

$$R_b = R_Y / R_2$$

$$R_c = R_Y / R_3$$

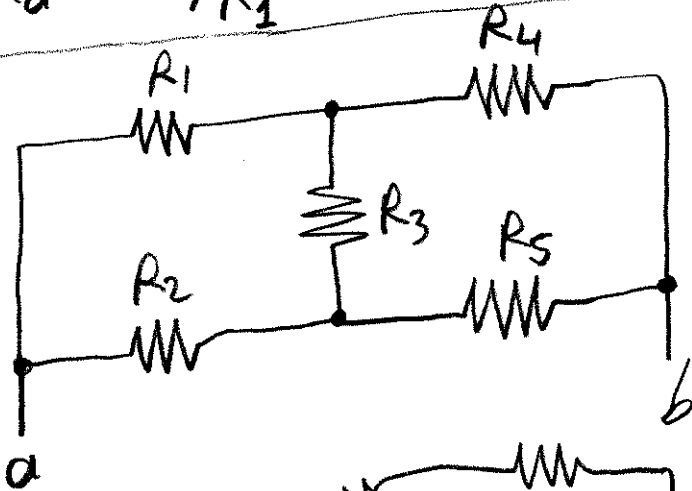

$$\begin{aligned} R_1 &= 36\Omega \\ R_2 &= 60\Omega \\ R_3 &= 48\Omega \end{aligned}$$

$$\begin{aligned} R_4 &= 9\Omega \\ R_5 &= 22\Omega \end{aligned}$$


$$R_{ab} = ?$$

$$\begin{aligned} R_{\Delta} &= R_1 + R_2 + R_3 \\ &= 36\Omega + 60\Omega + 48\Omega \\ &= 144\Omega \end{aligned}$$

$$R_6 = \frac{R_1 R_2}{R_{\Delta}} = \frac{36\Omega \times 60\Omega}{144\Omega} = 15\Omega$$

$$R_7 = \frac{R_1 R_3}{R_{\Delta}} = \frac{36\Omega \times 48\Omega}{144\Omega} = 12\Omega$$
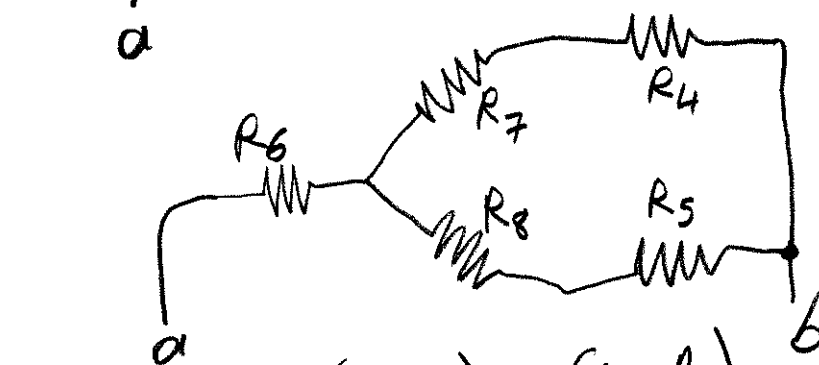
$$R_8 = \frac{R_2 R_3}{R_{\Delta}} = \frac{60\Omega \times 48\Omega}{144\Omega} = 20\Omega$$




$$R_{ab} = R_6 + (R_4 + R_7) \parallel (R_5 + R_8)$$

$$= 15\Omega + 21\Omega \parallel 42\Omega$$

$$= 15\Omega + 14\Omega = 29\Omega$$

# Simetrik Devreler

(14)

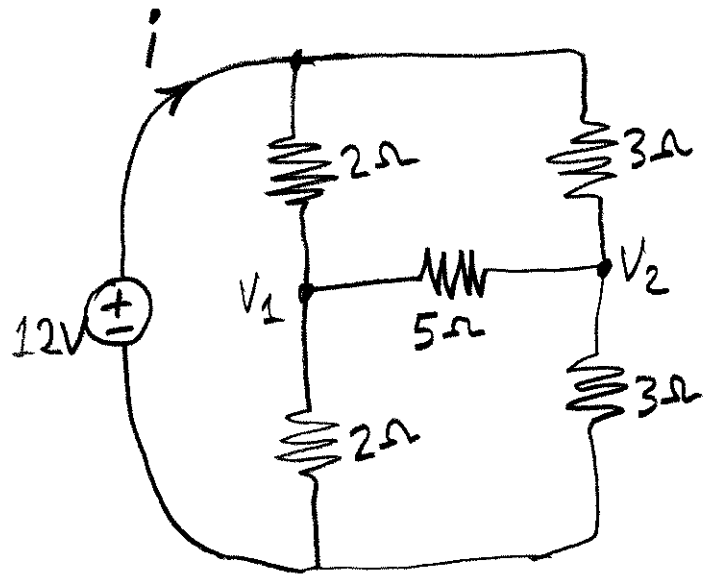

$$\frac{V_1 - V_2}{5} + \frac{V_1}{2} + \frac{V_1 - 12}{2} = 0$$


$$6V_1 - V_2 = 30 \quad \text{1. denklemin}$$

$$\frac{V_2 - V_1}{5} + \frac{V_2}{3} + \frac{V_2 - 12}{3} = 0$$

$$-3V_1 + 13V_2 = 60 \quad \text{2. denklemin}$$



$$V_1 = V_2 = 6V$$

5Ω üzerinden akım geçmez.

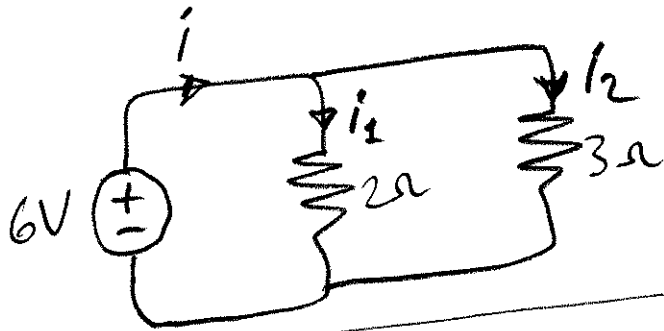

$$i_1 = \frac{6V}{2\Omega} = 3A \quad i = i_1 + i_2$$

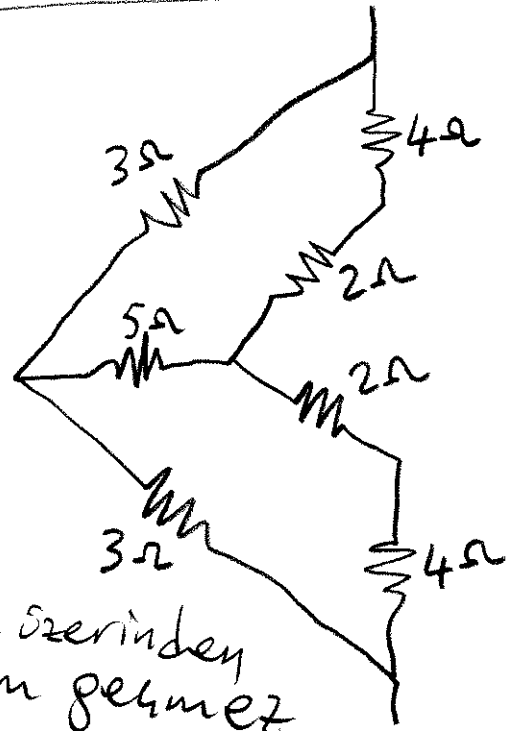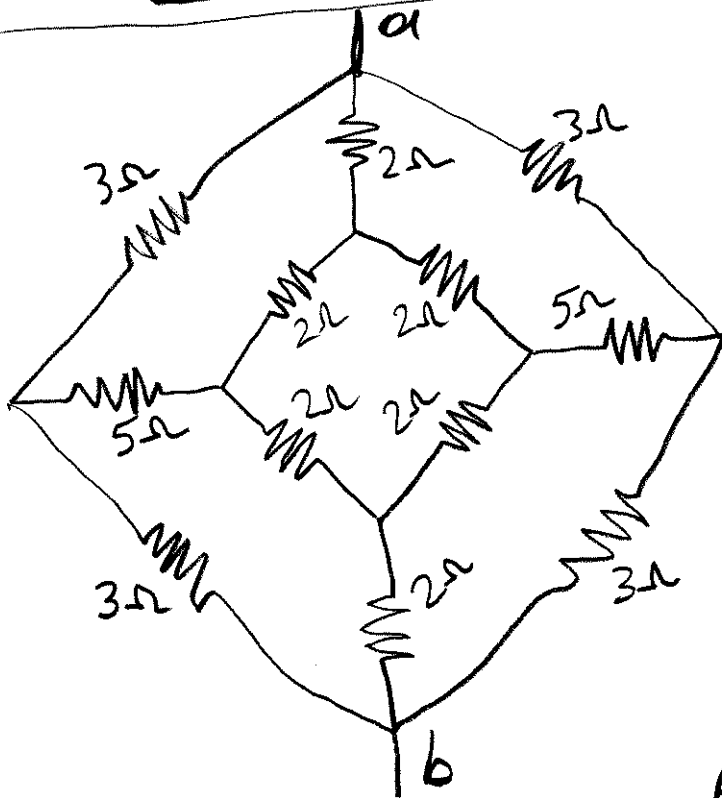
$$i_2 = \frac{6V}{3\Omega} = 2A \quad = 3A + 2A = 5A$$




5Ω üzerinden akım geçmez

$$R' = 2R'' = 4\Omega$$

$$R_T = R'/2 = 2\Omega$$

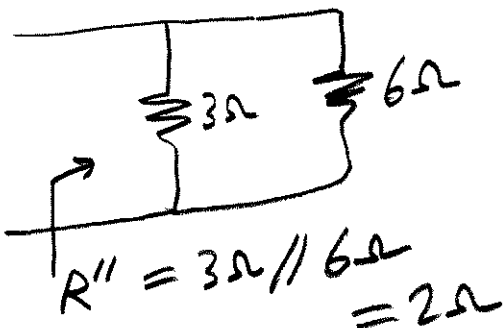

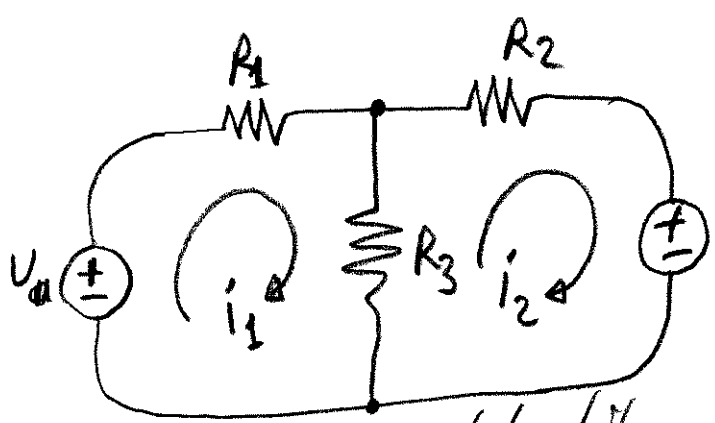

$$R_1 = 2\Omega \quad R_2 = 5\Omega \quad R_3 = 5\Omega \quad (1)$$

$$V_1 = 25V \quad V_2 = 9V$$

Devre elemanları üzerindeki akımları, voltajları ve güçleri bulunuz.

Üretilen ve tüketilen güçleri bulunuz.

$$(R_1 + R_3)i_1 - R_3i_2 = V_a \Rightarrow 7i_1 - 5i_2 = 25$$

$$R_3i_1 - (R_2 + R_3)i_2 = V_b \Rightarrow 5i_1 - 8i_2 = 9$$

$$\begin{bmatrix} 7 & -5 & 25 \\ 5 & -8 & 9 \end{bmatrix} \sim \begin{bmatrix} 1 & 0 & 5 \\ 0 & 1 & 2 \end{bmatrix} \quad \begin{matrix} i_1 = 5A \\ i_2 = 2A \end{matrix}$$

$$i_3 = i_1 - i_2 = 5A - 2A = 3A$$

$$V_1 = R_1 i_1 = 2\Omega \times 5A = 10V$$

$$V_2 = R_2 i_2 = 5\Omega \times 2A = 10V$$


$$V_3 = R_3 i_3 = 5\Omega \times 3A = 15V$$

$$P_{\text{totk}} = P_1 + P_2 + P_3 = 50W + 12W + 45W = 107W$$

$$P_a = V_a i_1 = 25V \times 5A = 125W$$

$$P_b = V_b i_2 = 9V \times 2A = 18W$$
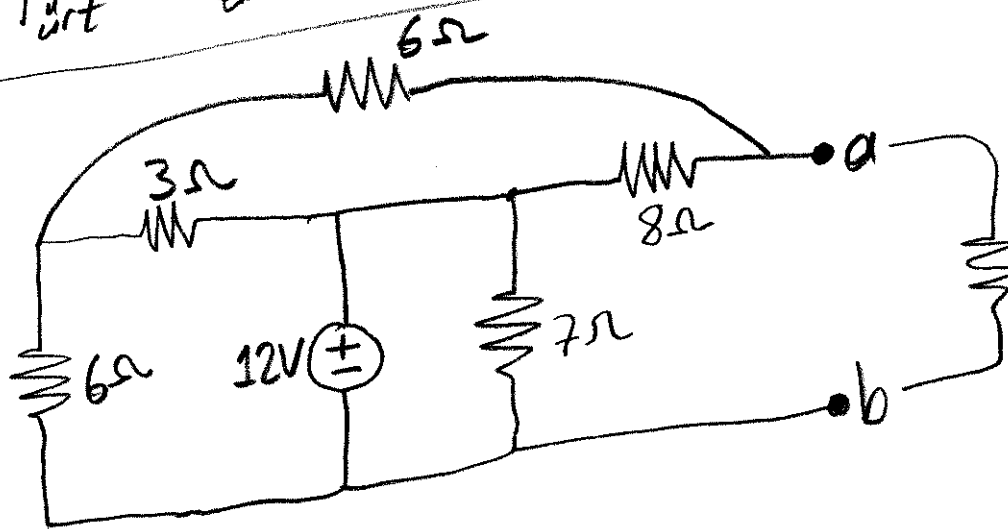
$$P_{\text{üret}} = P_a - P_b = 125W - 18W = 107W$$




a) \$R\_L\$ direncinin bağlandığı devrenin thevenin ve norton eşdeğer devresini bulunuz.

b)  $R_L = 16\Omega$  ise  $V_L$  ve  $I_L$  bulunuz.

(16)

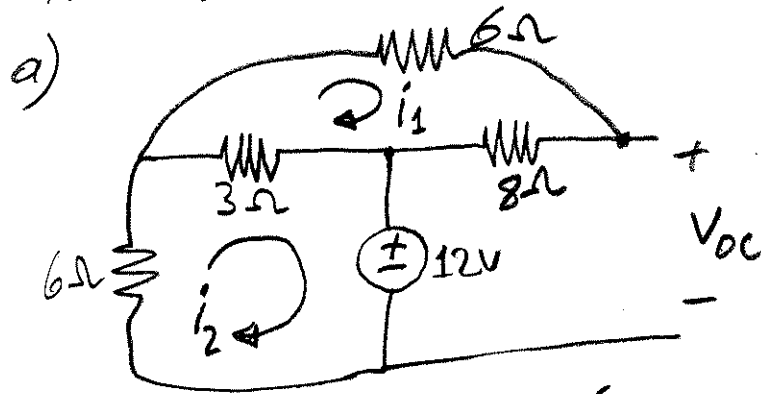c)  $R_L$  lineer değilse yani  $i_L = \begin{cases} V_L^2/2 & V_L \geq 0 \\ 0 & V_L < 0 \end{cases}$  ise  $V_L$  ve  $I_L$  bulunuz.




$$\begin{aligned} 17i_1 - 3i_2 &= 0 \\ -3i_1 + 9i_2 &= -12 \end{aligned}$$


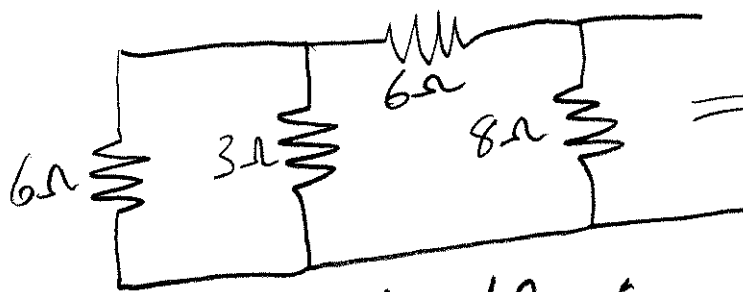
1. denklemin 3 katını 2. denkleme ekle

$$48i_1 = -12 \Rightarrow i_1 = -0.25A$$

$$V_{oc} = 12V + 8\Omega \times i_1 = 12V + 8\Omega \times (-0.25A) = 10V = V_e$$


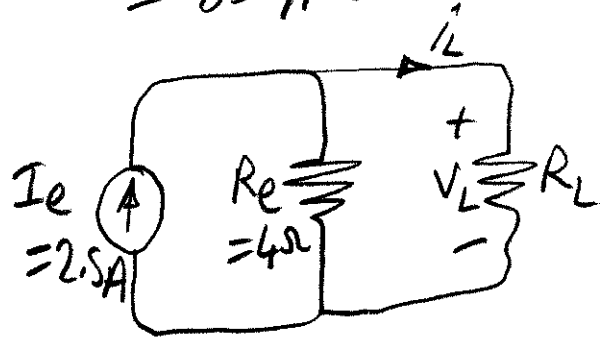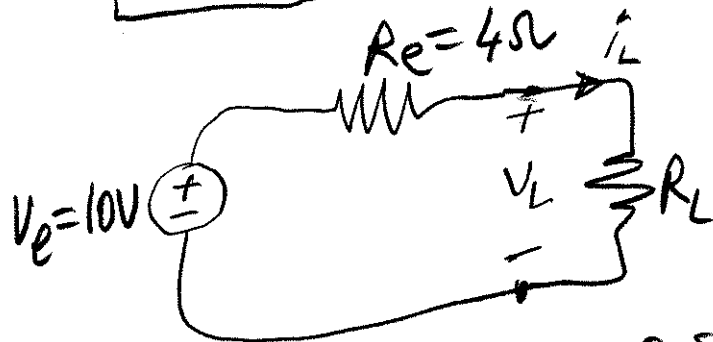
$$\begin{aligned} R_e &= (6\Omega // 3\Omega + 6\Omega) // 8\Omega \\ &= 8\Omega // 8\Omega = 4\Omega \end{aligned}$$



$$I_e = V_e / R_e = 10V / 4\Omega = 2.5A$$

b)  $R_L$  lineer

$$i_L = \frac{V_e}{R_e + R_L} = \frac{10V}{4\Omega + 16\Omega} = \frac{10V}{20\Omega} = 0.5A$$

$$\begin{aligned} V_L &= R_L i_L \\ &= 16\Omega \times 0.5A \\ &= 8V \end{aligned}$$

c)

$$V_e = R_e i_L + V_L$$

$$10V = 4\Omega \times 0.5V_L^2 + V_L$$

$$2V_L^2 + V_L - 10 = 0$$

$$(V_L - 2)(2V_L + 5) = 0$$

$$V_L = 2V$$


$$V_L = \cancel{5/2V}$$

$$i_L = 0.5V_L^2 = 2A$$

$$R_L = V_L / i_L = \frac{2V}{2A} = 1\Omega$$



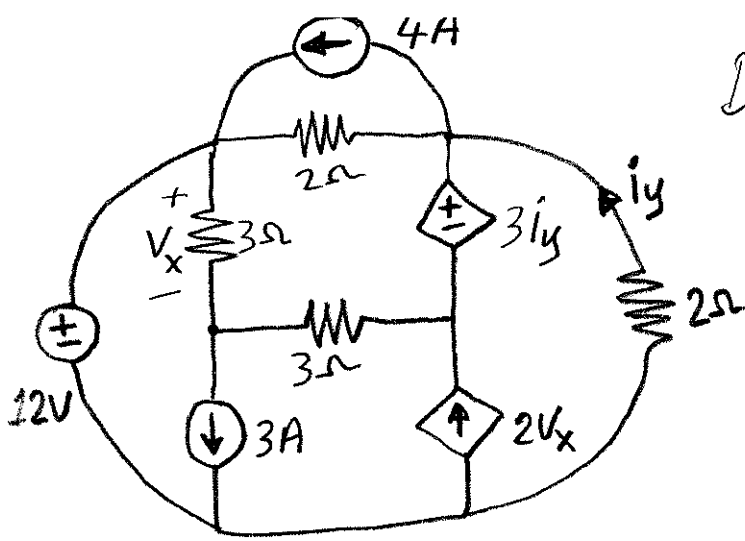Devrenin Thevenin eşdeğerini (17) bulup  $i_y$  akımını hesaplayınız.





$$\frac{V_y}{2} - i_y - 2V_x - \frac{V_x}{3} = 0$$

$$3V_y - 6i_y - 14V_x = 0 \quad \begin{matrix} 1. \text{denklem} \\ 2. \text{denklem} \end{matrix}$$

$$V_y - 3i_y + 2V_x = 0$$
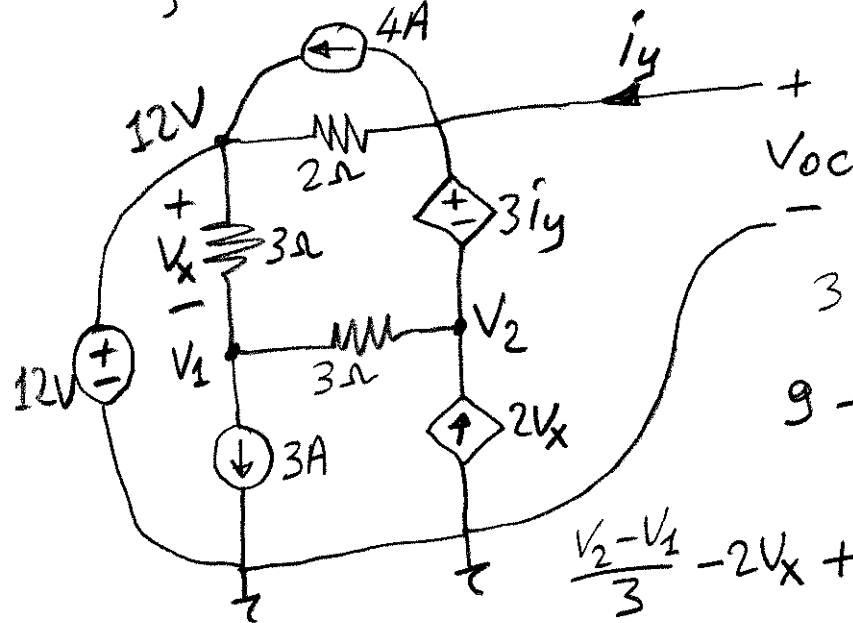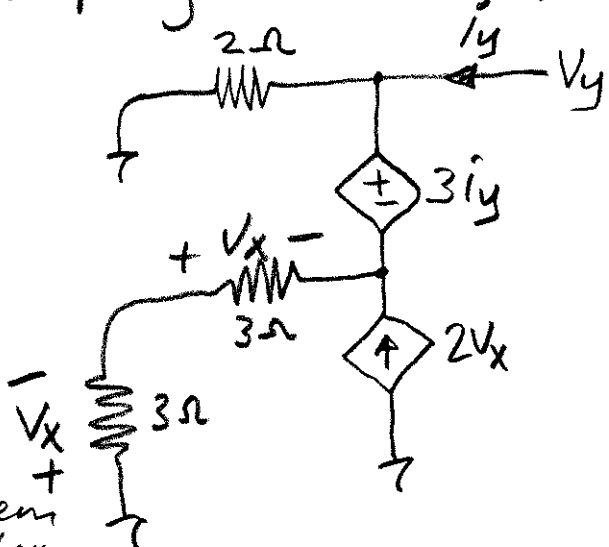
$$V_y = 18V_x, \quad i_y = \frac{20}{3}V_x \Rightarrow R_e = \frac{V_y}{i_y} = \frac{18V_x}{\frac{20}{3}V_x} = 2.7 \Omega$$



$$V_1 = 12 - V_x$$

$$i_y = 0 \Rightarrow V_2 = V_{oc}$$

$$3 - \frac{V_x}{3} + \frac{V_1 - V_2}{3} = 0$$


$$9 - V_x + 12 - V_x - V_{oc} = 0$$

$$2V_x + V_{oc} = 21 \quad 1. \text{denklem}$$

$$\frac{V_2 - V_1}{3} - 2V_x + 4 + \frac{V_{oc} - 12}{2} = 0$$

$$\frac{V_{oc} - 12 + V_x}{3} - 2V_x + 4 + \frac{V_{oc}}{2} - 6 = 0 \Rightarrow 5V_{oc} - 10V_x = 36 \quad 2. \text{denklem}$$
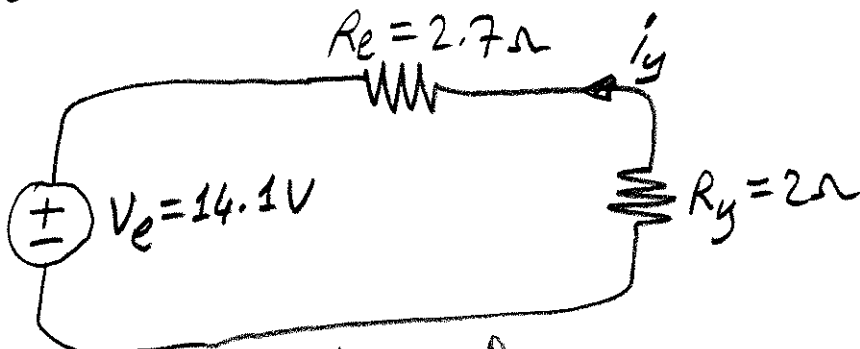
$$\text{Denklemler çözdükçe } V_{oc} = 14.1V = V_e$$





Thevenin Eşdeğer Devre

$$i_y = - \frac{V_e}{R_e + R_y} = - \frac{14.1V}{2.7\Omega + 2\Omega}$$

$$= - \frac{14.1V}{4.7\Omega} = -3A$$

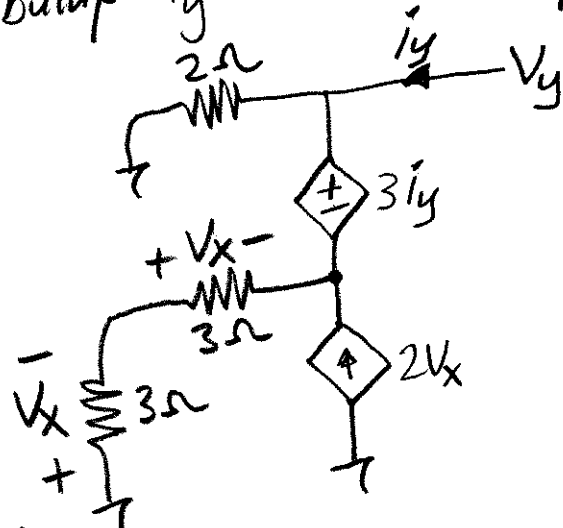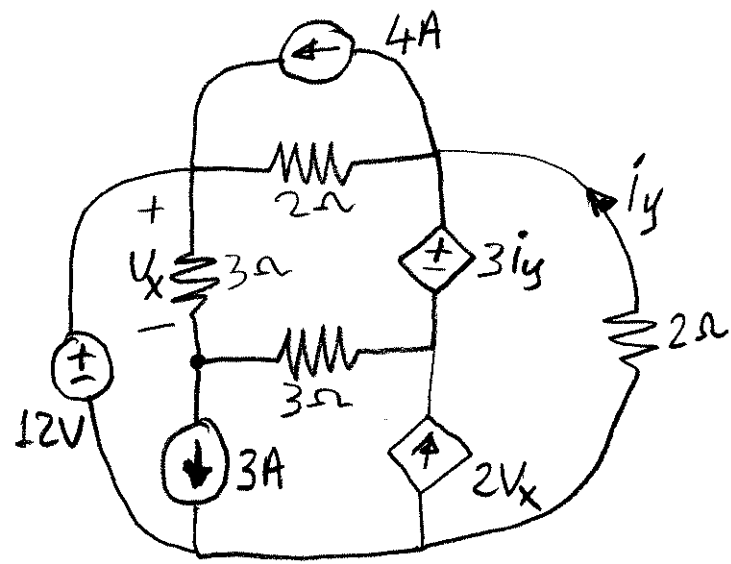Devrenin Norton eşdeğerini bulup  $i_y$  akımını hesaplayınız. (18)




$$\frac{V_y}{2} - i_y - 2V_x - \frac{V_x}{3} = 0$$

$$3V_y - 6i_y - 14V_x = 0 \quad \text{1. denklemin}$$

$$V_y - 3i_y + 2V_x = 0 \quad \text{2. denklemin}$$
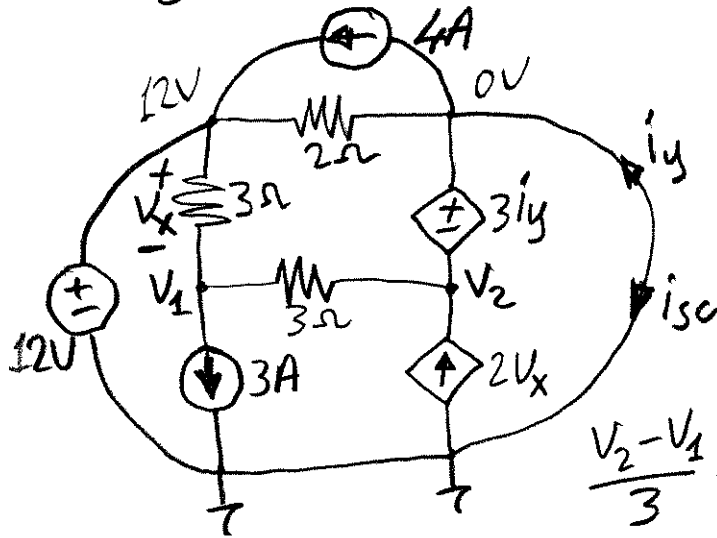
$$V_y = 18V_x, i_y = \frac{20}{3}V_x \Rightarrow R_e = \frac{V_y}{i_y} = \frac{18V_x}{\frac{20}{3}V_x} = 2.7 \Omega$$



$$V_1 = 12 - V_x, V_2 = -3i_y$$

$$3 - \frac{V_x}{3} + \frac{V_1 - V_2}{3} = 0$$


$$9 - V_x + 12 - V_x + 3i_y = 0$$

$$2V_x - 3i_y = 21 \quad \text{1. denklemin}$$

$$\frac{V_2 - V_1}{3} - 2V_x - i_y + 4 - \frac{12}{2} = 0$$

$$\frac{-3i_y - 12 + V_x}{3} - 2V_x - i_y - 2 = 0 \Rightarrow 5V_x + 6i_y = -18 \quad \text{2. denklemin}$$
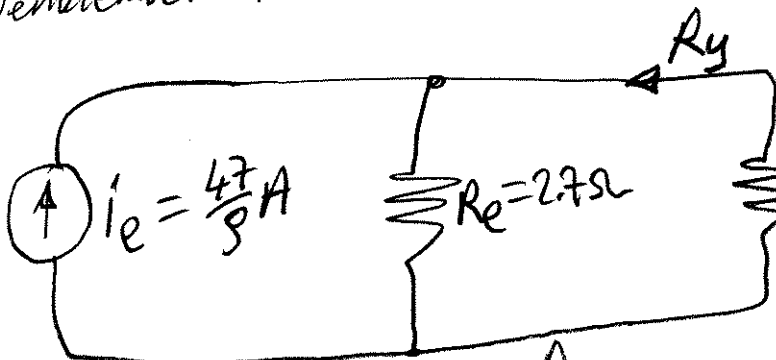
$$\text{Denklemler \&Ouml;2\&Ouml;l\u00fcrse } V_x = \frac{8}{3}V, i_y = -\frac{47}{8}A \Rightarrow i_{sc} = -i_y = \frac{47}{8}A$$




Norton Eşdeğer Devre

$$R_e(i_e + i_y) + R_y i_y = 0$$

$$R_e i_e = -(R_e + R_y) i_y$$

$$i_y = -\frac{R_e i_e}{R_e + R_y}$$
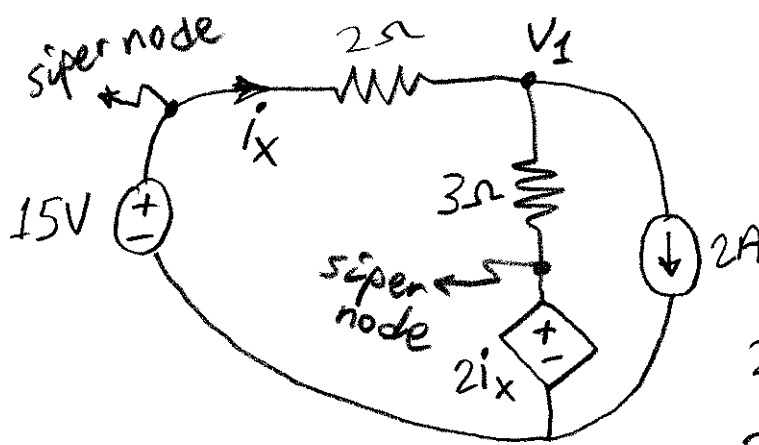
$$i_y = -\frac{2.7}{4.7} \frac{47}{8} A = -3A$$




$$V_1 = 15 - 2i_x \quad (19)$$

$$2 - i_x + \frac{V_1 - 2i_x}{3} = 0$$

$$2 - i_x + \frac{15 - 2i_x - 2i_x}{3} = 0$$

$$21 - 7i_x = 0 \Rightarrow i_x = 3A$$

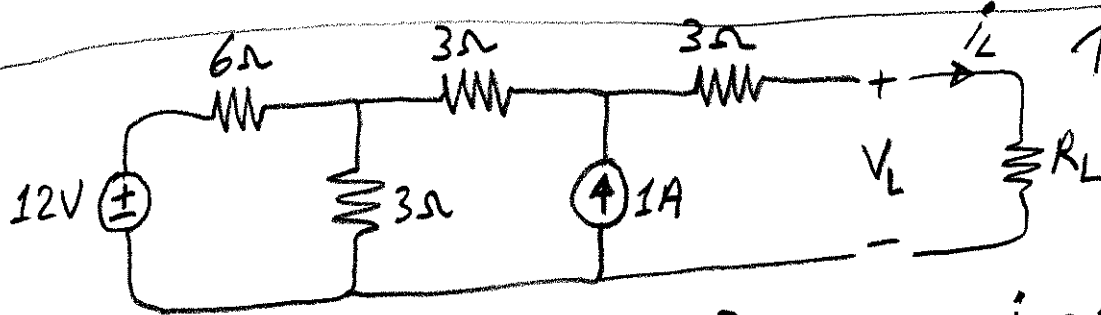


Thevenin ve Norton eşdeğerini bulup  $R_L = 10\Omega$  için  $V_L = ?$


$$i_2 = 1A \quad \text{in } V_L = ?$$

$$9i_1 + 3i_2 = 12$$


$$i_2 = \frac{12 - 3i_1}{3} = 1A$$

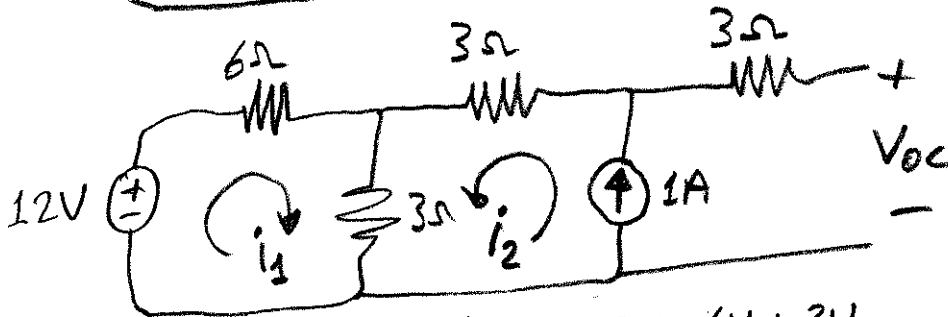
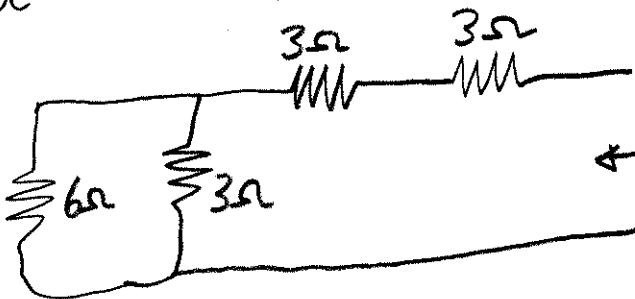
$$V_{oc} = 12 - 6i_1 + 3i_2 = 12V - 6V + 3V = 9V = V_e$$



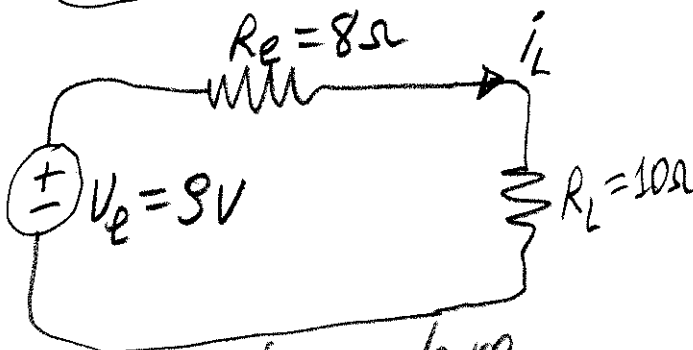
$$\begin{aligned} R_e &= 6\Omega // 3\Omega + 3\Omega + 3\Omega \\ &= 2\Omega + 3\Omega + 3\Omega \\ &= 8\Omega \end{aligned}$$




Thevenin Eşdeğer devre

$$i_L = \frac{V_e}{R_e + R_L} = \frac{9V}{8\Omega + 10\Omega} = \frac{9V}{18\Omega} = 0.5A$$


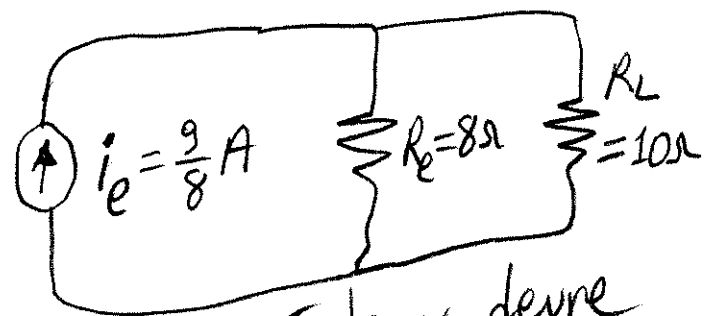
$$V_L = R_L i_L = 10\Omega \times 0.5A = 5V$$



Norton Eşdeğer devre

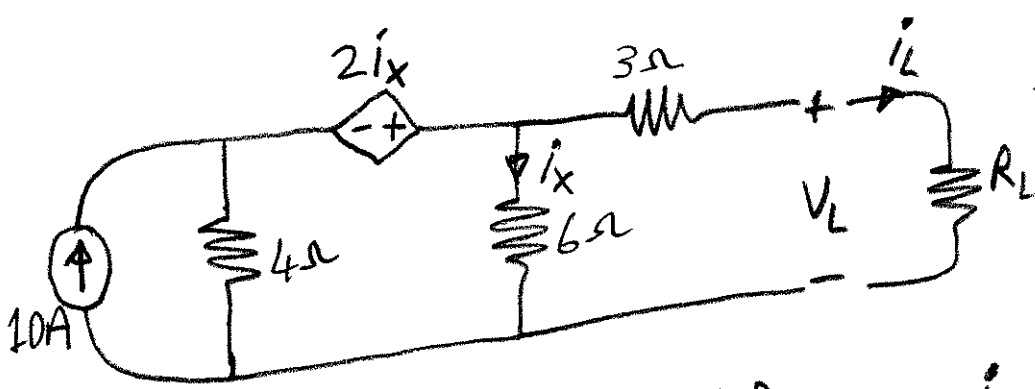

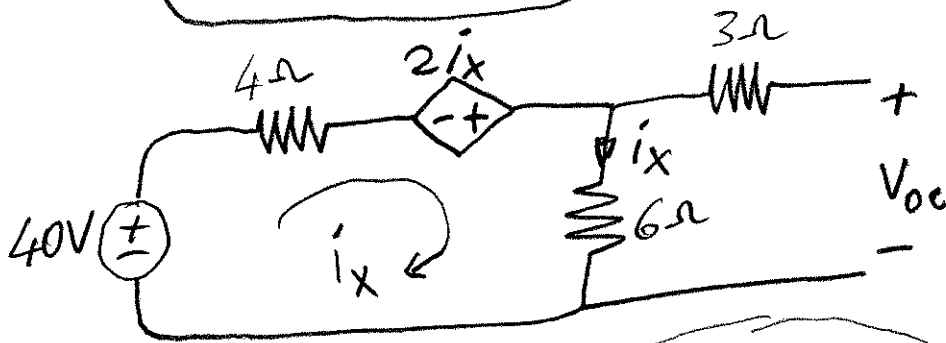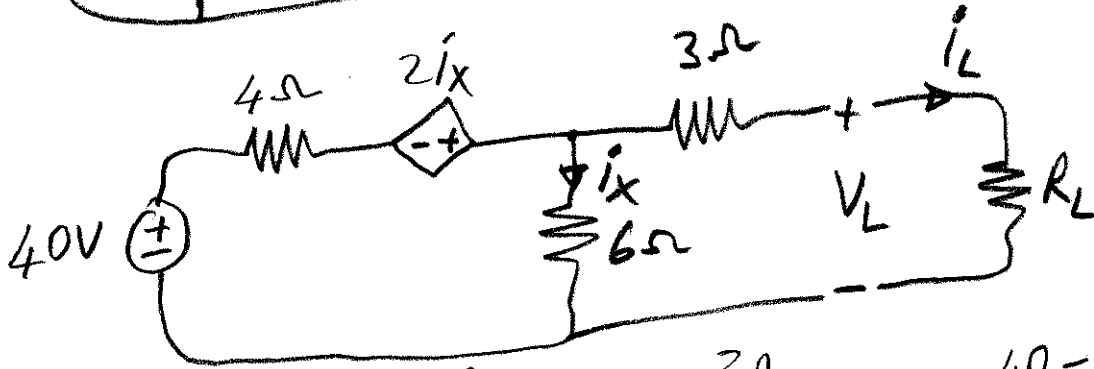
Thevenin ve Norton  
Eşdeğerini bulup  
 $R_L = 4\Omega$  için  
 $V_L = ?$



$$40 - 10i_x + 2i_x = 0$$

$$8i_x = 40 \Rightarrow i_x = 5A$$

$$V_{oc} = 6i_x = 30V$$

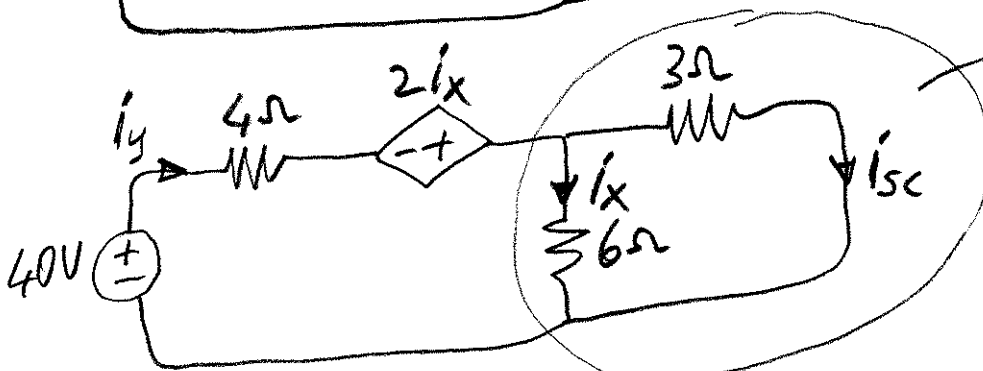

$$3\Omega // 6\Omega = 2\Omega$$

$$6i_x = 3i_{sc}$$


$$i_{sc} = 2i_x$$

$$i_y = i_x + i_{sc} = 3i_x$$


$$40 - 4i_y + 2i_x - 6i_x = 0$$

$$40 - 12i_x + 2i_x - 6i_x = 0 \Rightarrow i_x = 2.5A \Rightarrow i_{sc} = 2i_x = 5A$$
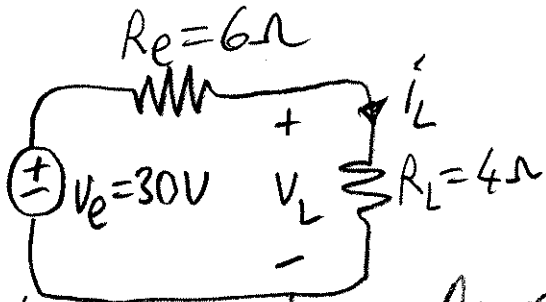
$$V_e = V_{oc} = 30V, i_e = i_{sc} = 5A, R_e = \frac{V_e}{i_e} = \frac{30V}{5A} = 6\Omega$$




Thevenin Eşdeğer Devre

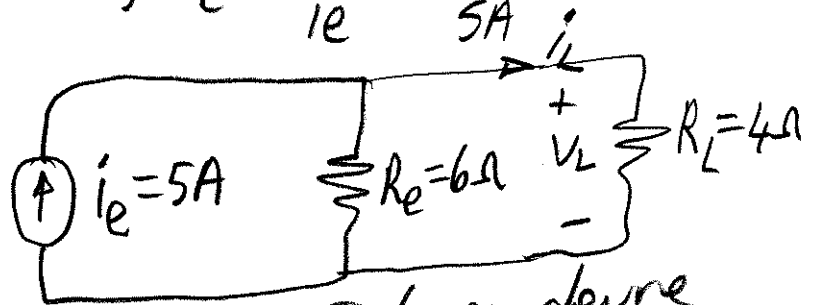

Norton Eşdeğer devre

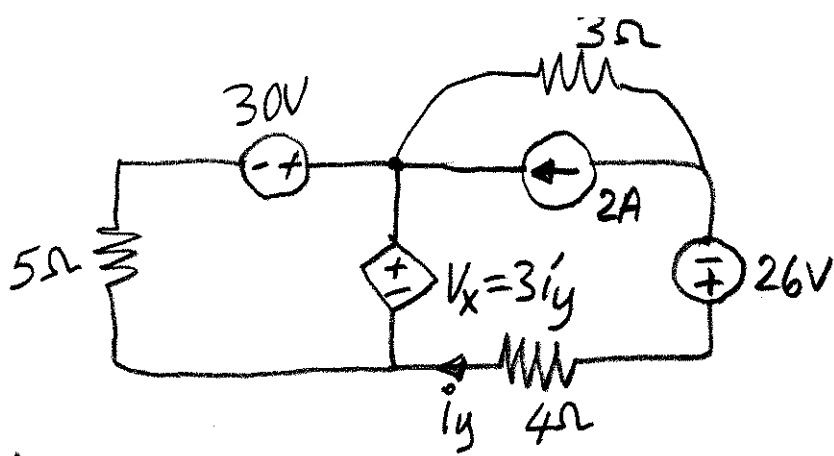
$$i_L = \frac{V_e}{R_e + R_L} = \frac{30V}{6\Omega + 4\Omega} = \frac{30V}{10\Omega} = 3A, V_L = R_L i_L = 12V$$



$$i_y = ?, V_x = ?, P_x = ? \quad (21)$$

a) Mesh Analiz (KVL) ile

b) Node Analiz (KCL) ile

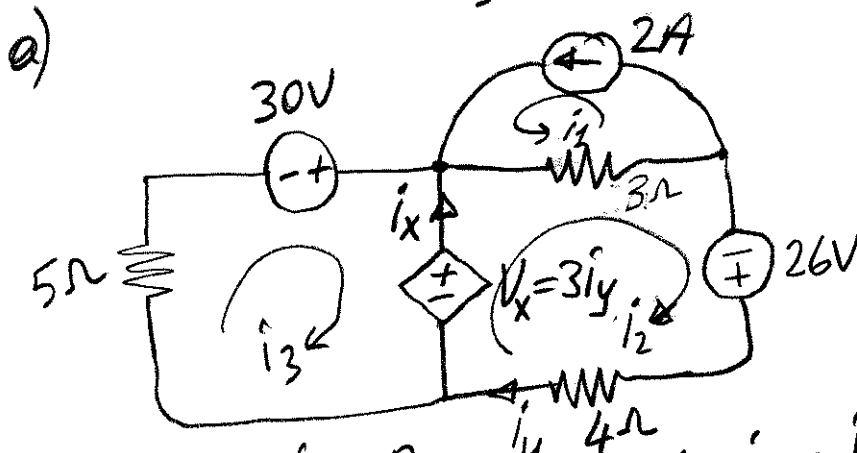

$$i_1 = 2A, \quad i_2 = i_y$$

$$V_x - 3i_1 - 7i_2 + 26 = 0$$

$$3i_y - 6 - 7i_y + 26 = 0$$


$$i_y = 5A \Rightarrow V_x = 15V$$

$$30 - V_x - 5i_3 = 0$$

$$i_3 = \frac{30 - V_x}{5} = 3A$$

$$i_x = i_2 - i_3 = i_y - i_3 = 5A - 3A = 2A$$
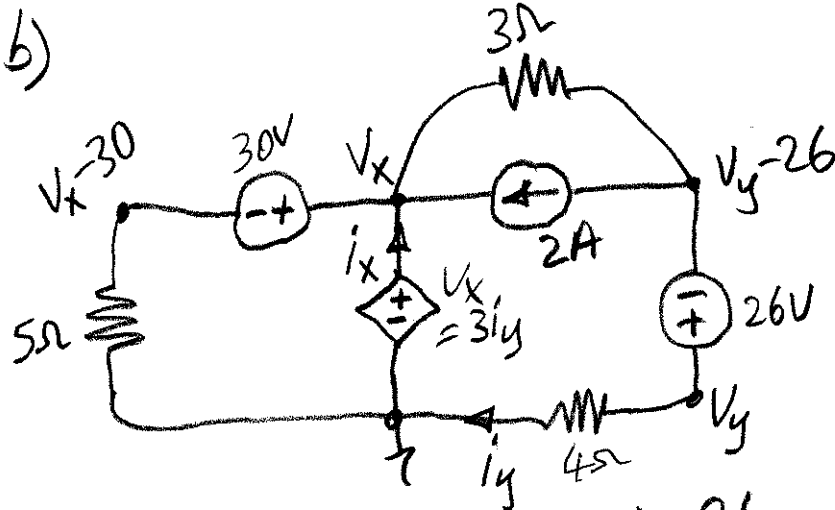
$$P_x = V_x i_x = 15V \times 2A = 30W \text{ üretici konumunda}$$



$$V_x = 3i_y, \quad V_y = 4i_y$$

$$i_x = i_y + \frac{V_x - 30}{5}$$

$$= 1.6i_y - 6$$


$$\frac{V_x - 30}{5} - i_x - 2 + \frac{V_x - V_y + 26}{3} = 0$$

$$\frac{3i_y - 30}{5} - 1.6i_y + 6 - 2 + \frac{3i_y - 4i_y + 26}{3} = 0 \Rightarrow i_y = 5A$$

$$V_x = 3i_y = 3\Omega \times 5A = 15V$$

$$i_x = 1.6i_y - 6 = 1.6 \times 5A - 6A = 8A - 6A = 2A$$

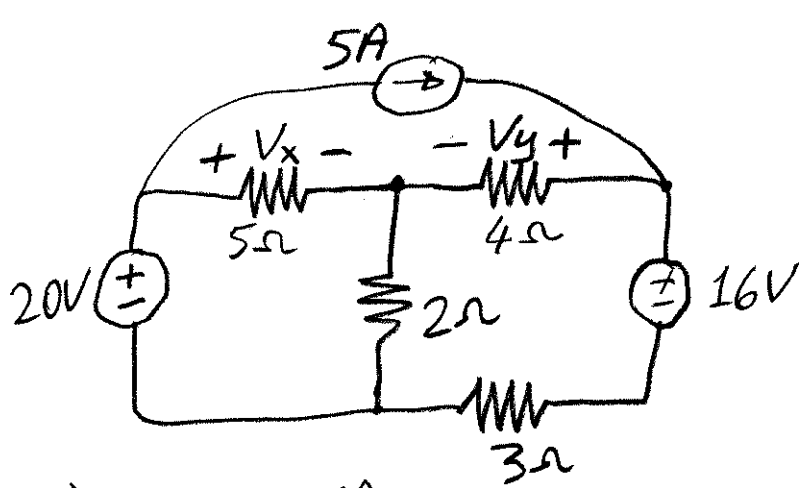
$$P_x = V_x i_x = 15V \times 2A = 30W \text{ üretici konumunda}$$



$$V_x = ? \quad V_y = ?$$

a) Nodal Analiz (KCL) ile

b) Mesh Analiz (KVL) ile

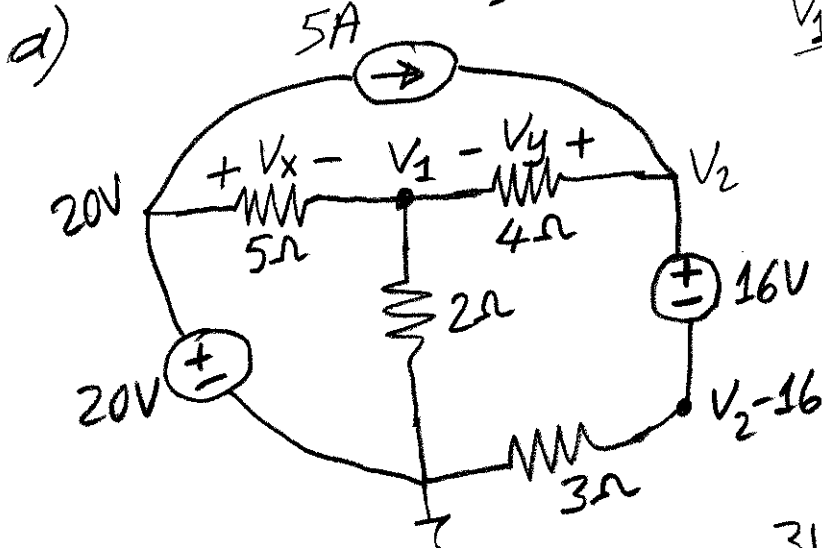

$$\frac{V_1 - 20}{5} + \frac{V_1}{2} + \frac{V_1 - V_2}{4} = 0$$

20 ile carp.

$$4V_1 - 80 + 10V_1 + 5V_1 - 5V_2 = 0$$

$$19V_1 - 5V_2 = 80 \quad 1. \text{ denklemin}$$

$$\frac{V_2 - V_1}{4} - 5 + \frac{V_2 - 16}{3} = 0$$

$$3V_2 - 3V_1 - 60 + 4V_2 - 64 = 0$$


$$7V_2 - 3V_1 = 124 \quad 2. \text{ denklemin}$$

denklemler a22line

$$V_1 = 10V, \quad V_2 = 22V$$

$$V_x = 20 - V_1 = 10V$$

$$V_y = V_2 - V_1 = 12V$$

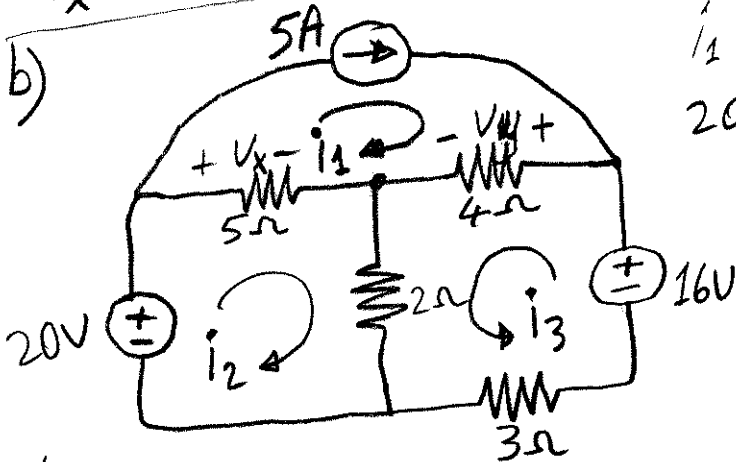

$$i_1 = 5A$$

$$20 + 5i_1 - 7i_2 - 2i_3 = 0$$

$$7i_2 + 2i_3 = 45 \quad 1. \text{ denklemin}$$

$$16 - 4i_1 - 2i_2 - 9i_3 = 0$$


$$2i_2 + 9i_3 = -4 \quad 2. \text{ denklemin}$$

denklemler a22line

$$i_2 = 7A, \quad i_3 = -2A$$

$$V_x = 5\Omega (i_2 - i_1) = 5\Omega (7A - 5A) = 5\Omega \times 2A = 10V$$
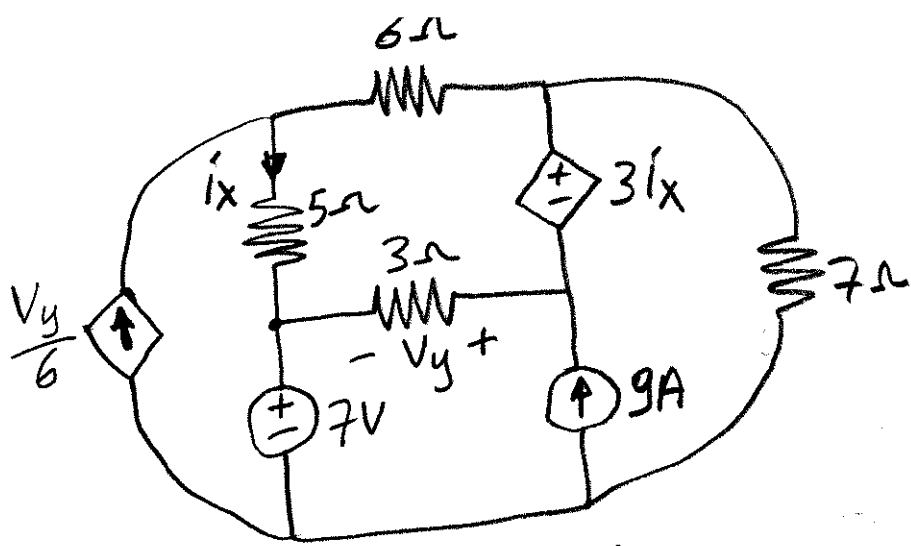
$$V_y = 4\Omega (i_1 + i_3) = 4\Omega (5A - 2A) = 4\Omega \times 3A = 12V$$




$$i_x = ? \quad V_y = ?$$

a) Nodal Analiz ile

b) Mesh Analiz ile

a)

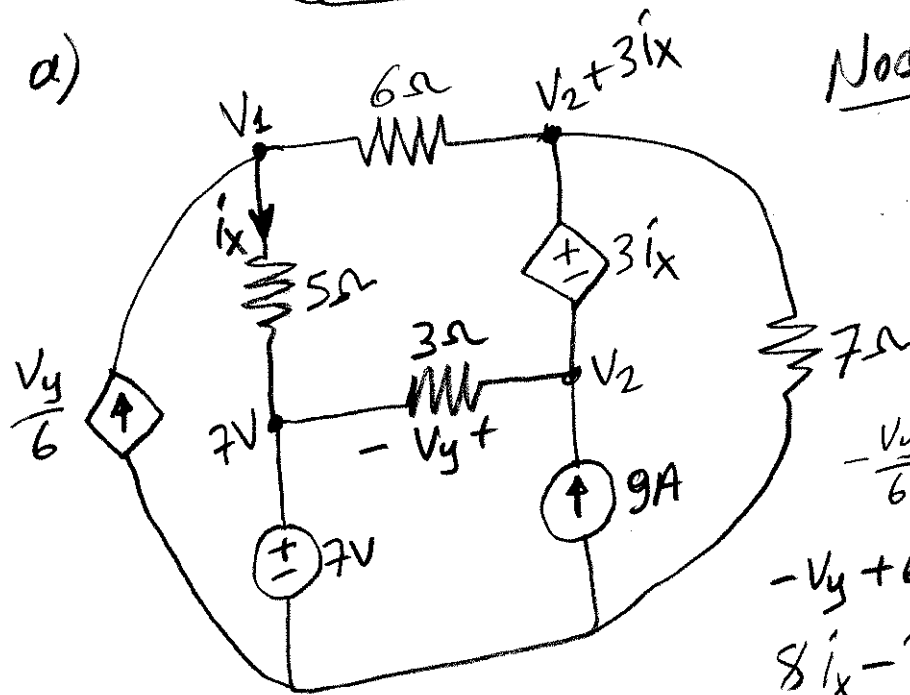

Nodal Analiz

$$V_1 = 7 + 5i_x$$

$$V_2 = 7 + V_y$$

$$-\frac{V_y}{6} + i_x + \frac{V_1 - V_2 - 3i_x}{6} = 0$$

$$-V_y + 6i_x + 7 + 5i_x - 7 - V_y - 3i_x = 0$$

$$8i_x - 2V_y = 0 \Rightarrow V_y = 4i_x$$

$$\frac{V_y}{3} - 9 + \frac{V_2 + 3i_x}{7} + \frac{V_2 + 3i_x - V_1}{6} = 0$$

$$\frac{V_y}{3} - 9 + \frac{7 + V_y + 3i_x}{7} + \frac{7 + V_y + 3i_x - 7 - 5i_x}{6} = 0$$

$$\frac{V_y}{3} + \frac{V_y + 3i_x}{7} + \frac{V_y - 2i_x}{6} = 8$$


$$\frac{4i_x}{3} + \frac{4i_x + 3i_x}{7} + \frac{4i_x - 2i_x}{6} = 8$$

$$\frac{4}{3}i_x + i_x + \frac{i_x}{3} = 8 \Rightarrow \frac{8i_x}{3} = 8 \Rightarrow i_x = 3A$$

$$V_y = 4i_x = 4\Omega \times 3A = 12V$$

b)

(24)

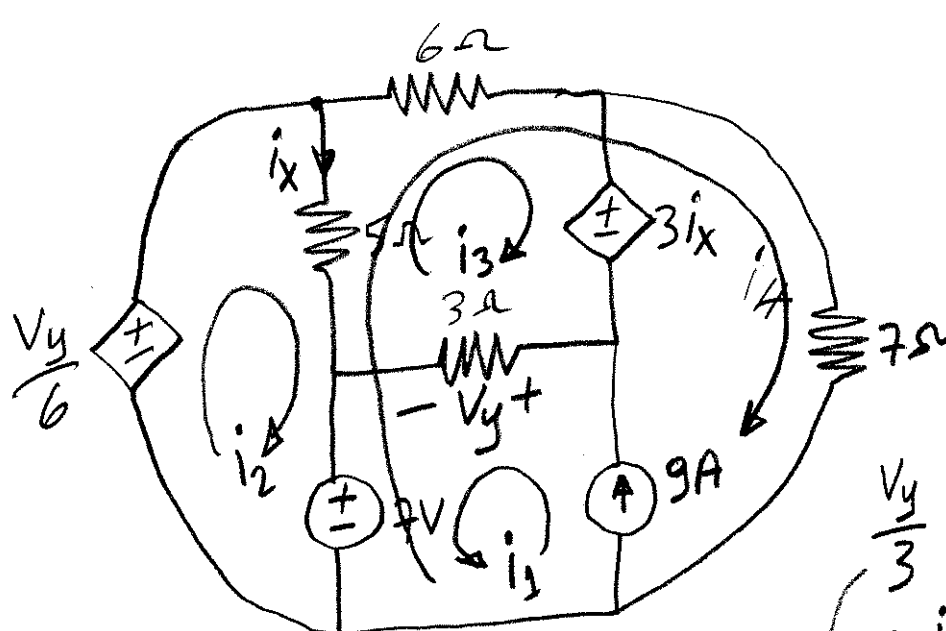Mesh Analysis

$$i_1 = 9A$$

$$i_2 = V_y/6$$

$$\frac{V_y}{3} = i_1 + i_3$$

$$\rightarrow i_3 = \frac{V_y}{3} - 9$$

$$i_x = i_2 - i_3 - i_4$$

$$\rightarrow i_4 = i_2 - i_3 - i_x = \frac{V_y}{6} - \left(\frac{V_y}{3} - 9\right) - i_x = 9 - i_x - \frac{V_y}{6}$$

$$3i_x + 6(i_3 + i_4) - 5i_x + V_y = 0$$

$$3i_x + 6\left(\frac{V_y}{3} - 9 + 9 - i_x - \frac{V_y}{6}\right) - 5i_x + V_y = 0$$

$$3i_x + 2V_y - 6i_x - V_y - 5i_x + V_y = 0$$

$$2V_y - 8i_x = 0 \Rightarrow V_y = 4i_x$$

$$7 + 5i_x - 6i_3 - 13i_4 = 0$$

$$7 + 5i_x - 6\left(\frac{V_y}{3} - 9\right) - 13\left(9 - i_x - \frac{V_y}{6}\right) = 0$$


$$7 + 5i_x - 2V_y + 54 - 117 + 13i_x + \frac{13}{6}V_y = 0$$

$$18i_x + \frac{V_y}{6} = 56$$

$$18i_x + \frac{4i_x}{6} = 56 \Rightarrow \frac{56}{3}i_x = 56 \Rightarrow i_x = 3A$$


$$V_x = 4i_x = 4\Omega \times 3A = 12V$$



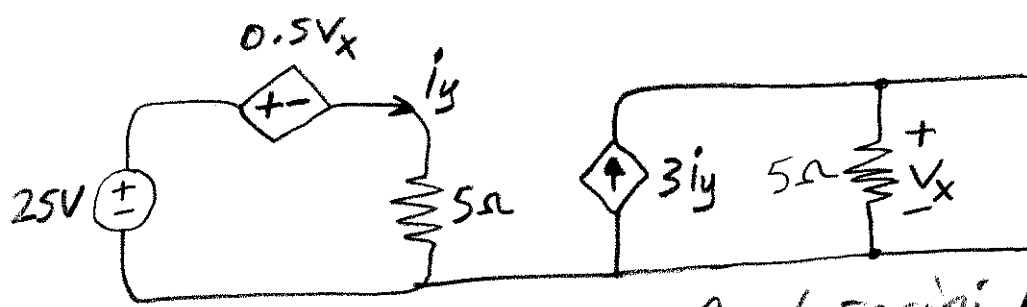

Devrenin Thévenin eşdeğerini bulup  $R_L$  direnci bağlayınız.
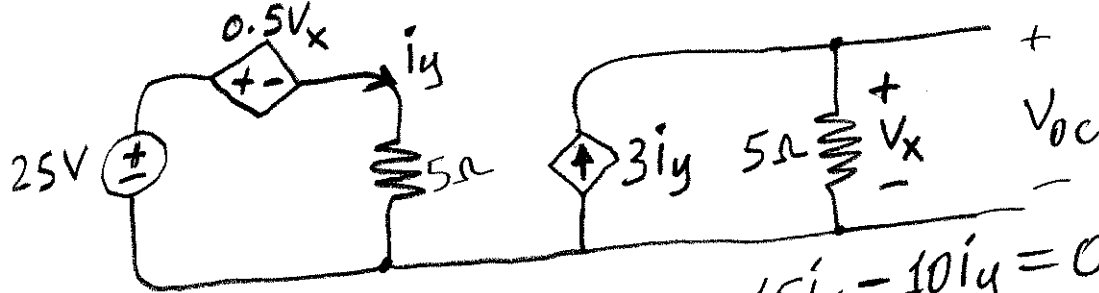
$$V_L = i_L^2 + 4i_L + 3 \text{ için } R_L \text{ değerini bulunuz.}$$




$$V_x = 15i_y$$

$$25 - 0.5V_x - 5i_y = 0$$

$$50 - V_x - 10i_y = 0$$

$$50 - 15i_y - 10i_y = 0$$

$$i_y = 2A, V_{oc} = V_x = 15i_y = 30V$$

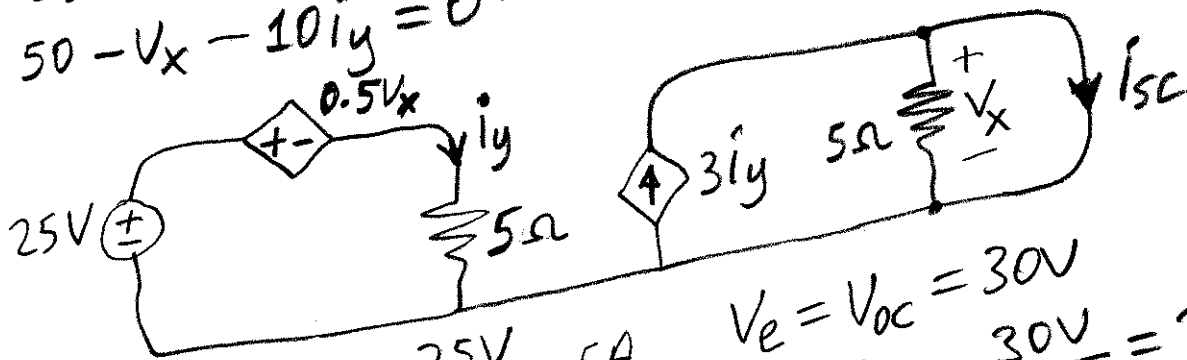


$$V_x = 0 \Rightarrow i_y = \frac{25V}{5\Omega} = 5A$$

$$i_{sc} = 3i_y = 15A = i_e$$

$$R_e = 2\Omega$$

$$V_e = V_{oc} = 30V$$
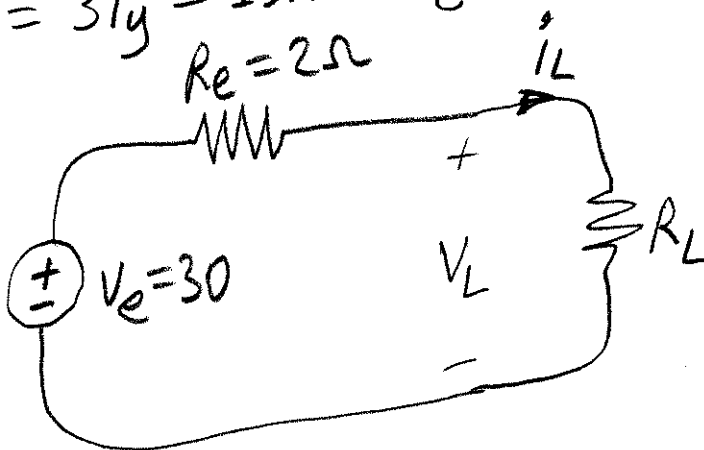
$$R_e = \frac{V_e}{i_e} = \frac{30V}{15A} = 2\Omega$$



$$V_L = i_L^2 + 4i_L + 3$$

$$= 9 + 12 + 3 = 24V$$

$$R_L = \frac{V_L}{i_L} = \frac{24V}{3A} = 8\Omega$$

$$V_e - R_e i_L - V_L = 0$$

$$30 - 2i_L - i_L^2 - 4i_L - 3 = 0$$

$$i_L^2 + 6i_L - 27 = 0$$

$$(i_L - 3)(i_L + 9) = 0$$

$$i_L = 3A \quad i_L = -9A$$


$$i_L > 0 \text{ olmalı}$$

(26)


$$R_1 = 20\Omega$$

$$R_2 = 12\Omega$$

$$R_3 = 15\Omega$$

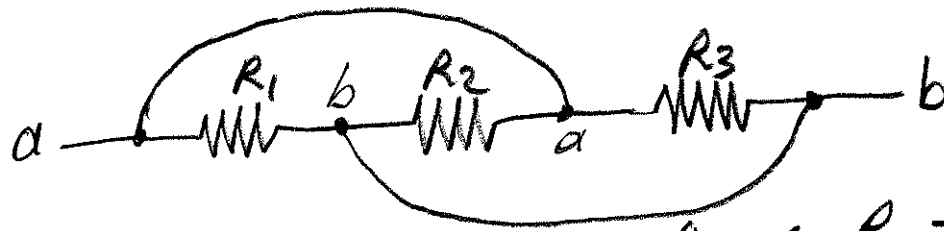


ab uçları arasındaki direnç  $R_T = ?$

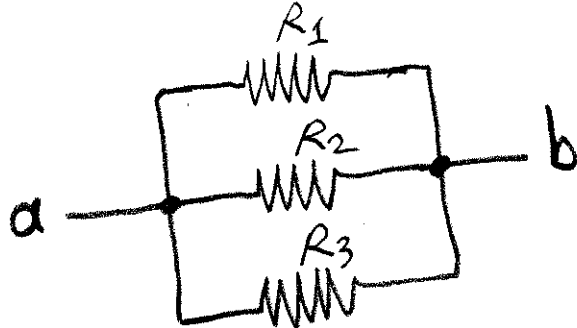

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$R_T = \frac{R_1 R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

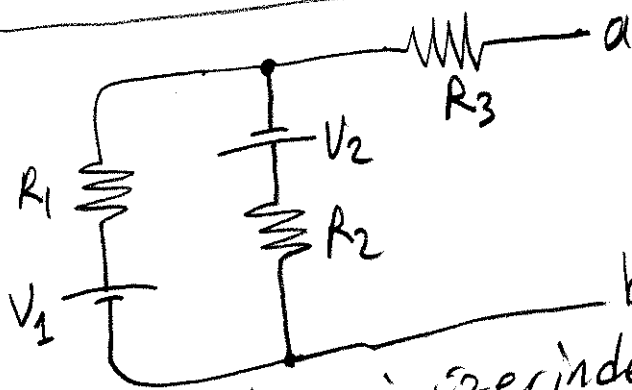
$$R_T = \frac{20 \times 12 \times 15}{20 \times 12 + 20 \times 15 + 12 \times 15} \Omega = \frac{3600}{240 + 300 + 180} \Omega = 5\Omega$$



$$R_1 = 3\Omega, R_2 = 6\Omega, R_3 = 3\Omega$$


$$V_1 = 15V, V_2 = 12V$$

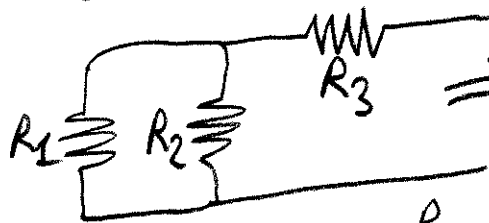Devrenin Thevenin eşdeğerini bulup uçlarına  $R_L$  direnci bağla.  $R_L$  direnci üzerinden geçen akım  $i_L = 0.5A$  ise  $R_L$  ve  $V_L$  değerlerini hesapla.



$$R_e = R_1 // R_2 + R_3 = 3\Omega // 6\Omega + 3\Omega$$

$$= 2\Omega + 3\Omega = 5\Omega$$

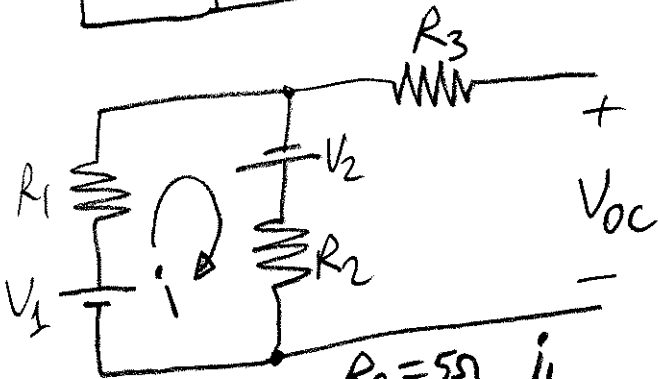


$$i = \frac{V_1 + V_2}{R_1 + R_2} = \frac{15V + 12V}{3\Omega + 6\Omega}$$

$$= \frac{27V}{9\Omega} = 3A$$



$$V_{oc} = V_1 - R_1 i = 15V - 3\Omega \times 3A = 6V$$

$$i_L = \frac{V_e}{R_e + R_L} = \frac{6V}{5\Omega + R_L} = 0.5A$$
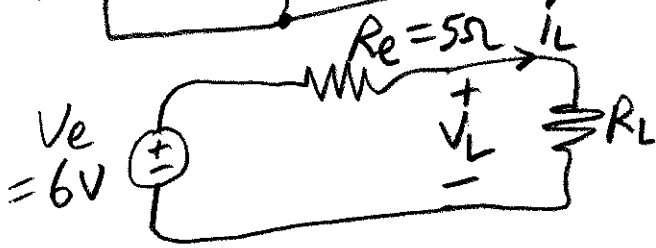
$$R_L = 7\Omega \quad V_L = R_L i_L = 3.5V$$



# Opamp : Operational Amplifier

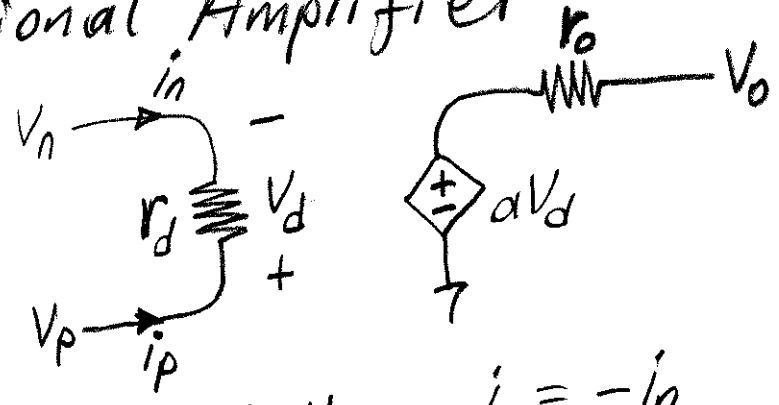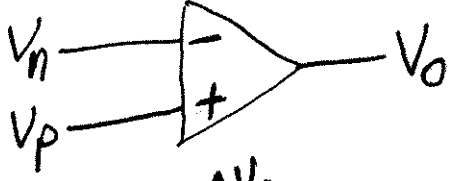


$$V_d = V_p - V_n, \quad i_p = -i_n$$

Opamp  $\pm 15V$  ile beslenirse saturasyon voltajları

$$V_H \approx 15V - 2V = 13V$$

$$V_L \approx -15V + 2V = -13V$$

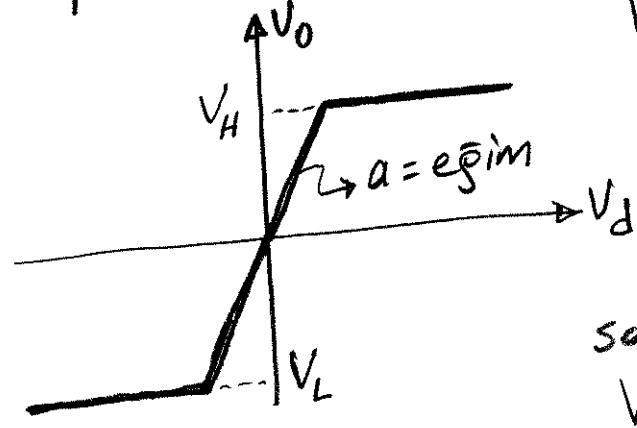

$$a = 200\,000 \text{ için}$$

$$\frac{13V}{a} \approx 65 \mu V$$

Artı ve çıkışa verilmez. Verilirse osilasyon yapar. Yani; kararlı durum oluşur.

## ideal Opamp

$$r_d \rightarrow \infty$$



$$r_o \rightarrow 0$$

$$a \rightarrow \infty$$

$r_d$  sonsuz ise üzerinden akım geçmez.  $i_p = -i_n = 0$  olur.  
Yani  $V_p = V_n$  olur.

$a$  sonsuz ve  $r_o$  sıfır ise  $V_d = \frac{V_o}{a} = 0$

## Voltaj Takip Edici

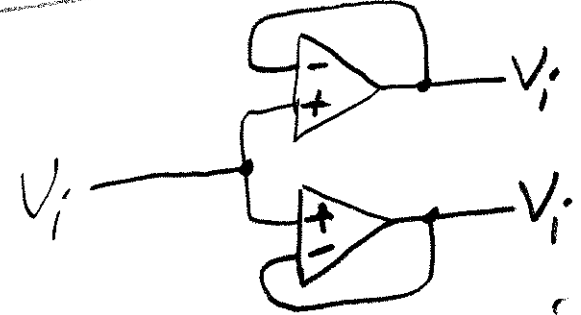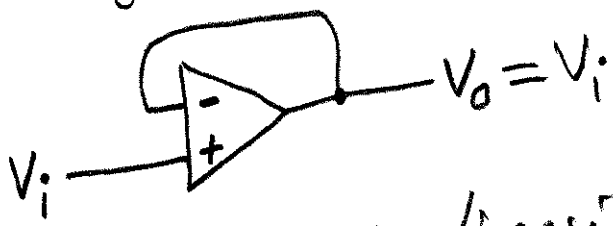


$$R_i = \infty \text{ Giriş direnci}$$

$$R_o = 0 \text{ Çıkış direnci}$$


$$A = 1 \text{ Yükseltme Oranı}$$

Kaynağın iç direnci varsa iç direncini sıfıra çekerek ideal kaynak oluşturur.


## Eviren Devre

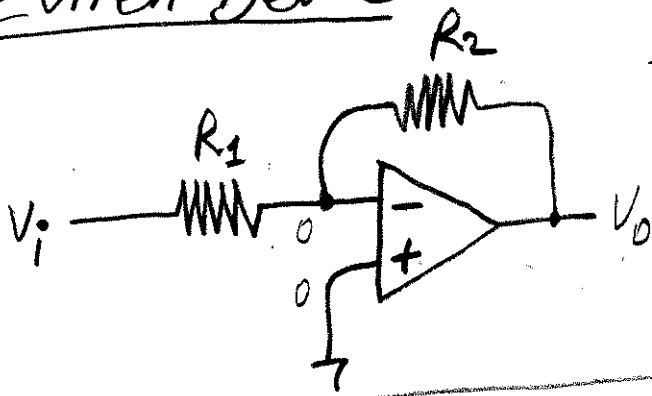
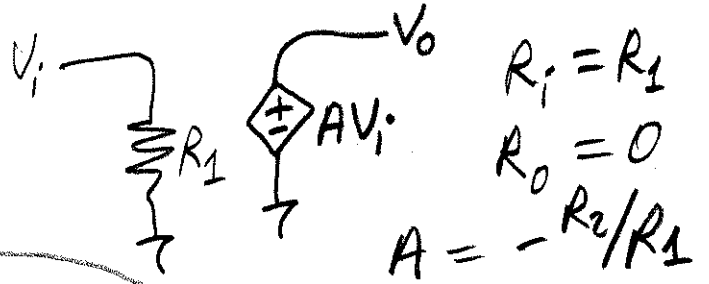
$$\frac{V_i}{R_1} + \frac{V_o}{R_2} = 0 \Rightarrow V_o = -\frac{R_2}{R_1} V_i \quad (28)$$





## Evirmeyen Opamp

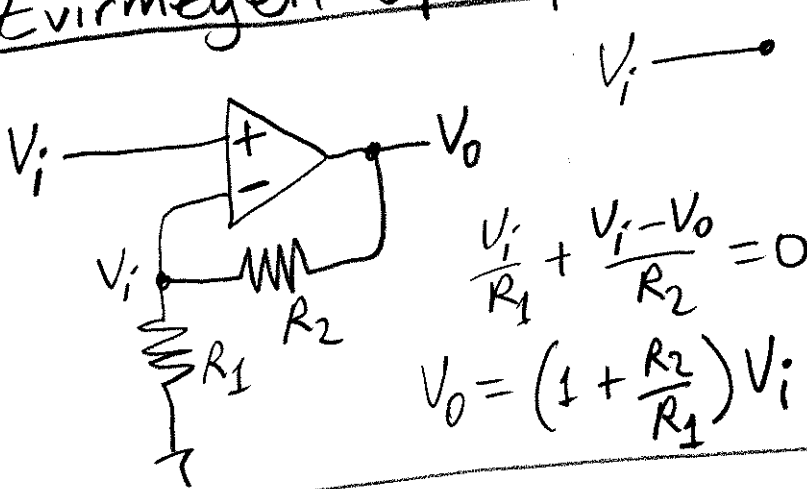

$$\frac{V_i}{R_1} + \frac{V_i - V_o}{R_2} = 0$$
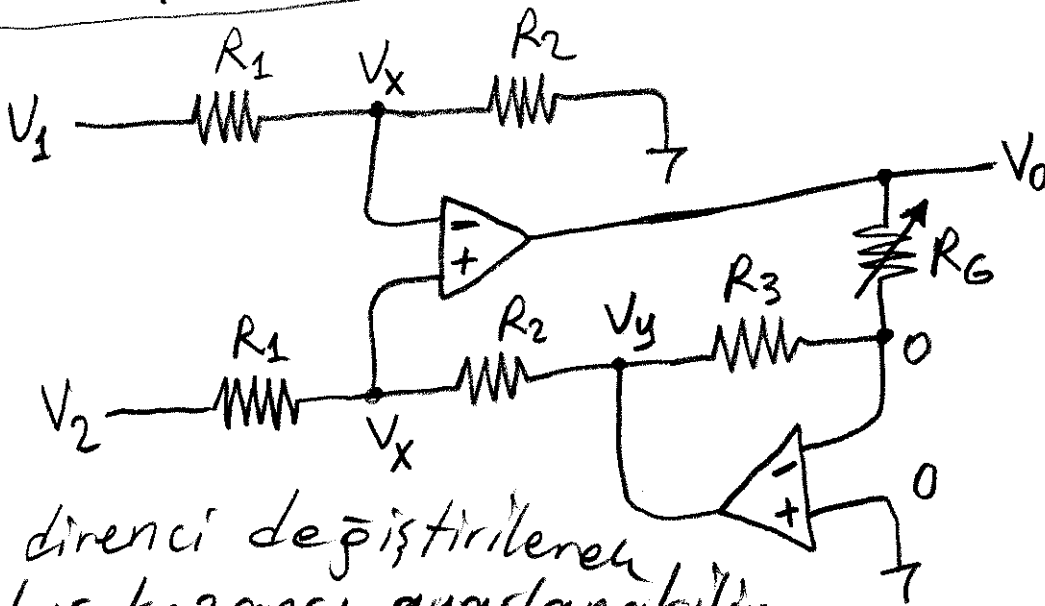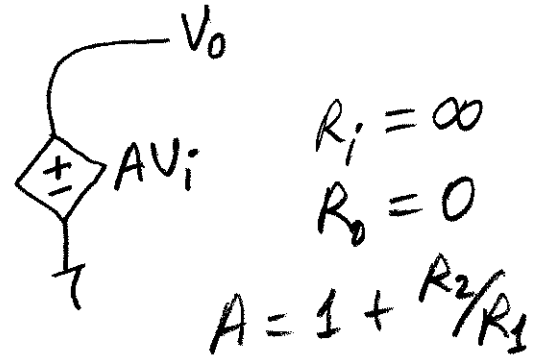
$$V_o = \left(1 + \frac{R_2}{R_1}\right) V_i$$



Görün ki 3 nokta alınır.

$R_6$  direnci değiştirilerek çıkış kazancı ayarlanabilir.

$$\frac{V_x - V_1}{R_1} + \frac{V_x}{R_2} = 0 \Rightarrow V_x = \frac{R_2}{R_1 + R_2} V_1$$


$$\frac{V_x - V_2}{R_1} + \frac{V_x - V_y}{R_2} = 0 \Rightarrow V_y = \left(1 + \frac{R_2}{R_1}\right) V_x - \frac{R_2}{R_1} V_2 = \frac{R_2}{R_1} (V_1 - V_2)$$

$$\frac{V_y}{R_3} + \frac{V_o}{R_6} = 0 \Rightarrow V_o = -\frac{R_6}{R_3} V_y = \left(\frac{R_2 R_6}{R_1 R_3}\right) (V_2 - V_1)$$

Aradaki farkı yükseltir.  $\rightarrow$  Kazanç

## Eviren Toplayıcı Devre

(29)

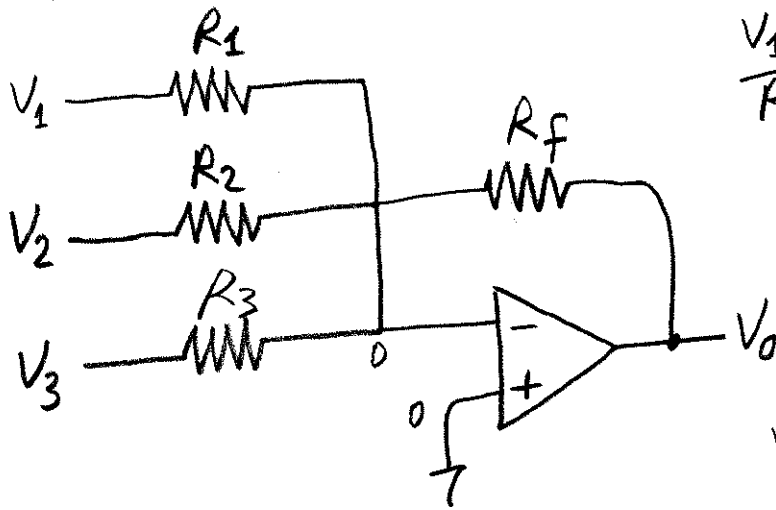


$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \frac{V_0}{R_f} = 0$$

$$V_0 = -R_f \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

$R_1 = R_2 = R_3 = R$  alınırsa

$$V_0 = -\frac{R_f}{R} (V_1 + V_2 + V_3)$$

## Evirmeyen Toplayıcı Devre

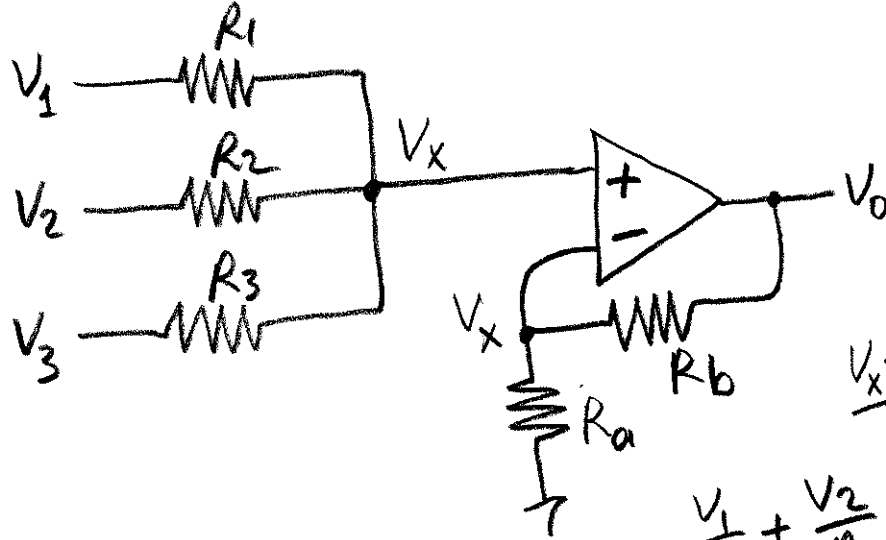

$$\frac{V_x}{R_a} + \frac{V_x - V_0}{R_b} = 0$$

$$V_0 = \left( 1 + \frac{R_b}{R_a} \right) V_x$$

$$\frac{V_x - V_1}{R_1} + \frac{V_x - V_2}{R_2} + \frac{V_x - V_3}{R_3} = 0$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = V_x \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$


$$V_x = \frac{R_1 R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3} \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

$$V_0 = \left( 1 + \frac{R_b}{R_a} \right) V_x = \left( 1 + \frac{R_b}{R_a} \right) \frac{R_1 R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3} \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

$R_1 = R_2 = R_3 = R$  alınırsa

$$V_0 = \left( 1 + \frac{R_b}{R_a} \right) \frac{R^3}{3R^2} \frac{1}{R} (V_1 + V_2 + V_3)$$

$$V_0 = \left( 1 + \frac{R_b}{R_a} \right) \frac{V_1 + V_2 + V_3}{3}$$

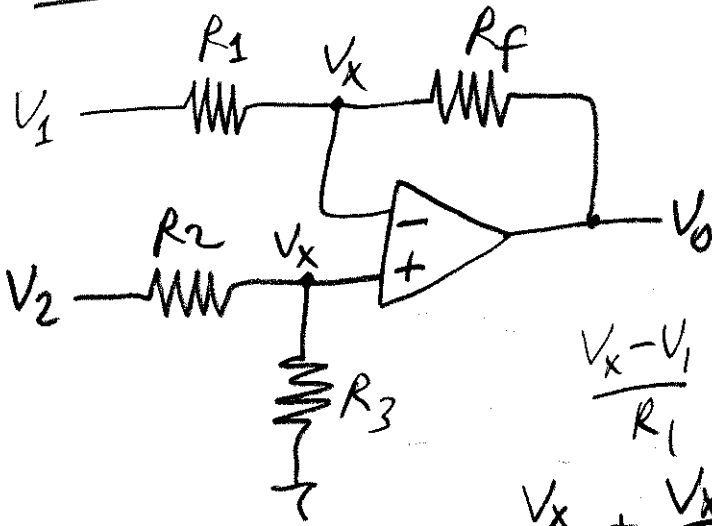Gıkarcı Devre

$$\frac{V_x - V_2}{R_2} + \frac{V_x}{R_3} = 0$$

$$V_x = \frac{R_3}{R_2 + R_3} V_2$$


$$\frac{V_x - V_1}{R_1} + \frac{V_x - V_0}{R_f} = 0$$

$$\frac{V_x}{R_1} + \frac{V_x}{R_f} = \frac{V_1}{R_1} + \frac{V_0}{R_f}$$

$$\frac{V_1}{R_1} + \frac{V_0}{R_f} = \left( \frac{1}{R_1} + \frac{1}{R_f} \right) V_x = \left( \frac{1}{R_1} + \frac{1}{R_f} \right) \frac{R_3}{R_2 + R_3} V_2$$

$$V_0 = \left( 1 + \frac{R_f}{R_1} \right) \frac{R_3}{R_2 + R_3} V_2 - \frac{R_f}{R_1} V_1$$

$$\frac{R_f}{R_1} = \frac{R_3}{R_1} = K \text{ olursa } V_0 = \frac{R_f}{R_1} (V_2 - V_1)$$

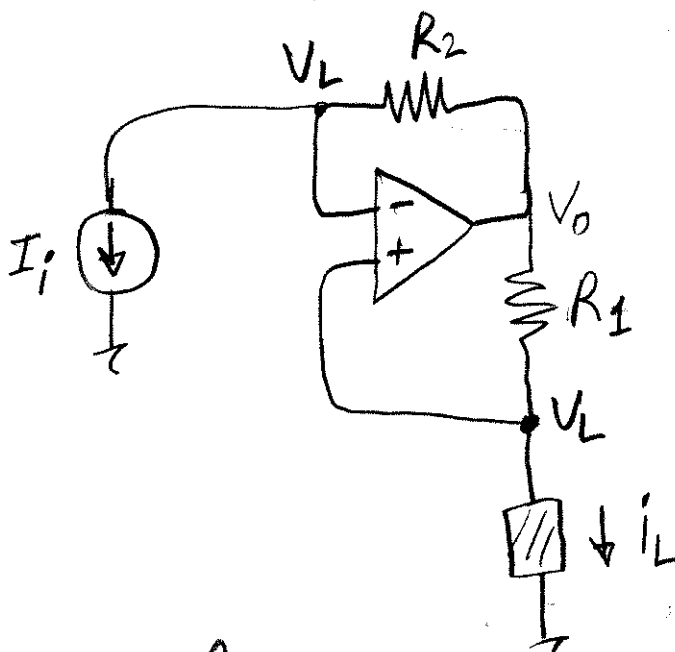Akım Yükselticiler

$$I_i + \frac{V_L - V_0}{R_2} = 0$$

$$V_L = V_0 - R_2 I_i$$

$$I_L + \frac{V_L - V_0}{R_1} = 0$$


$$I_L = \frac{V_0 - V_L}{R_1}$$

$$I_L = \frac{V_0 - (V_0 - R_2 I_i)}{R_1}$$

$$K = \frac{R_2}{R_1} \text{ kararsız ise}$$

$$I_L = K I_i \text{ olur.}$$

$$I_L = \frac{R_2}{R_1} I_i$$

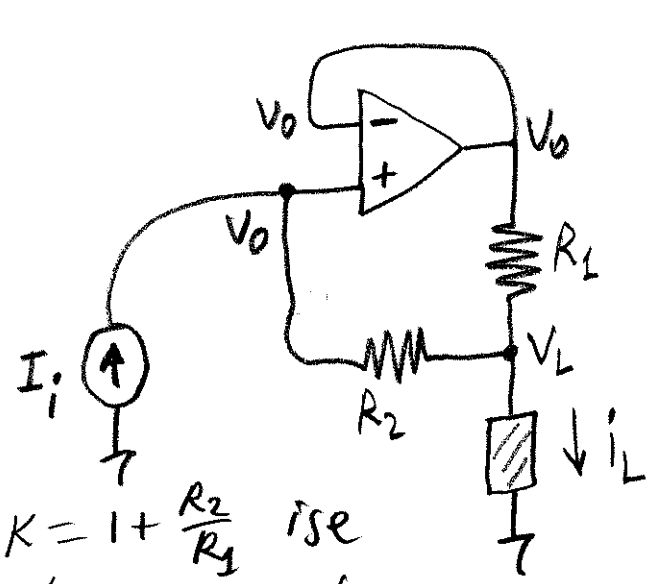

$$I_i = \frac{V_o - V_L}{R_2} \Rightarrow V_L = V_o - R_2 I_i$$


$$I_L = I_i + \frac{V_o - V_L}{R_1}$$

$$I_L = I_i + \frac{V_o - (V_o - R_2 I_i)}{R_1}$$

$$I_L = \left(1 + \frac{R_2}{R_1}\right) I_i$$

$K = 1 + \frac{R_2}{R_1}$  ise  
 $I_L = K I_i$  olur.

### İki Opampli Çıkartıcı Devre

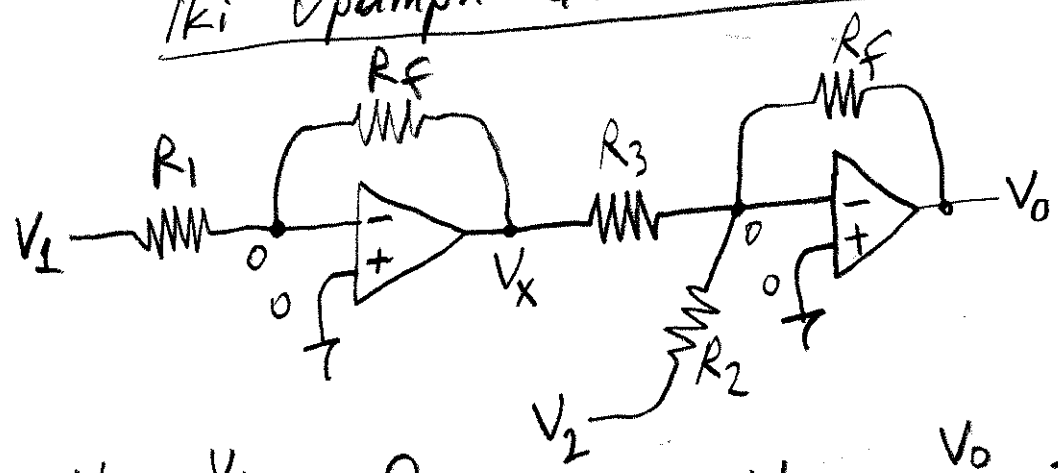

2 nokta seçilir.

$$\frac{V_1}{R_1} + \frac{V_x}{R_F} = 0$$

$$V_x = -\frac{R_F}{R_1} V_1$$

$$\frac{V_x}{R_3} + \frac{V_2}{R_2} + \frac{V_o}{R_F} = 0$$


$$V_o = -\frac{R_F}{R_3} V_x - \frac{R_F}{R_2} V_2$$

$$V_o = -\frac{R_F}{R_3} \left(-\frac{R_F}{R_1} V_1\right) - \frac{R_F}{R_2} V_2$$

$$= \frac{R_F^2}{R_1 R_3} V_1 - \frac{R_F}{R_2} V_2$$

$R_1 = R_2 = R_3 = R_F = R$  alınırsa

$$V_o = V_1 - V_2 \text{ olur.}$$

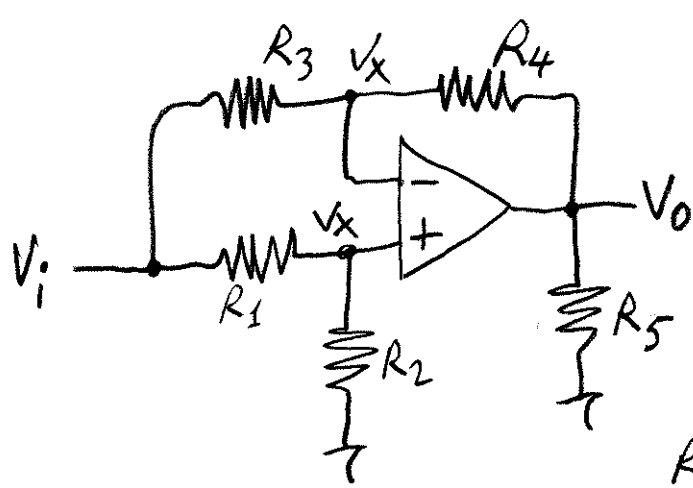

Yandaki ideal opamp'lı (32)  
devre için  
 $A=?$   $R_i=?$   $R_o=?$   
en sade halde bulunuz.

$$\frac{V_x - V_i}{R_1} + \frac{V_x}{R_2} = 0 \Rightarrow V_x = \frac{R_2}{R_1 + R_2} V_i$$

$$\frac{V_x - V_o}{R_3} + \frac{V_x - V_o}{R_4} = 0 \Rightarrow V_x = \frac{R_3}{R_3 + R_4} V_o + \frac{R_4}{R_3 + R_4} V_i$$

$$V_x = V_x \Rightarrow \frac{R_2}{R_1 + R_2} V_i = \frac{R_3}{R_3 + R_4} V_o + \frac{R_4}{R_3 + R_4} V_i$$

$$\frac{R_3}{R_3 + R_4} V_o = \left( \frac{R_2}{R_1 + R_2} - \frac{R_4}{R_3 + R_4} \right) V_i$$

$$V_o = \left( \frac{R_3 + R_4}{R_3} \frac{R_2}{R_1 + R_2} - \frac{R_4}{R_3} \right) V_i = \frac{R_2 R_3 - R_1 R_4}{(R_1 + R_2) R_3} V_i$$

$$A = \frac{R_2 R_3 - R_1 R_4}{(R_1 + R_2) R_3} \quad V_o = A V_i$$

$$I_i = \frac{V_i}{R_1 + R_2} + \frac{V_i - V_x}{R_3} = \frac{V_i}{R_1 + R_2} + \frac{V_i - \frac{R_2}{R_1 + R_2} V_i}{R_3}$$

$$= \left( \frac{1}{R_1 + R_2} + \frac{1}{R_3} - \frac{R_2}{(R_1 + R_2) R_3} \right) V_i$$


$$R_i = \frac{V_i}{I_i} = \frac{1}{\frac{1}{R_1 + R_2} + \frac{1}{R_3} - \frac{R_2}{(R_1 + R_2) R_3}} = \frac{(R_1 + R_2) R_3}{R_1 + R_3}$$

$$R_o = 0$$



# Voltaġ-Akım Dönüştürücü

(33)

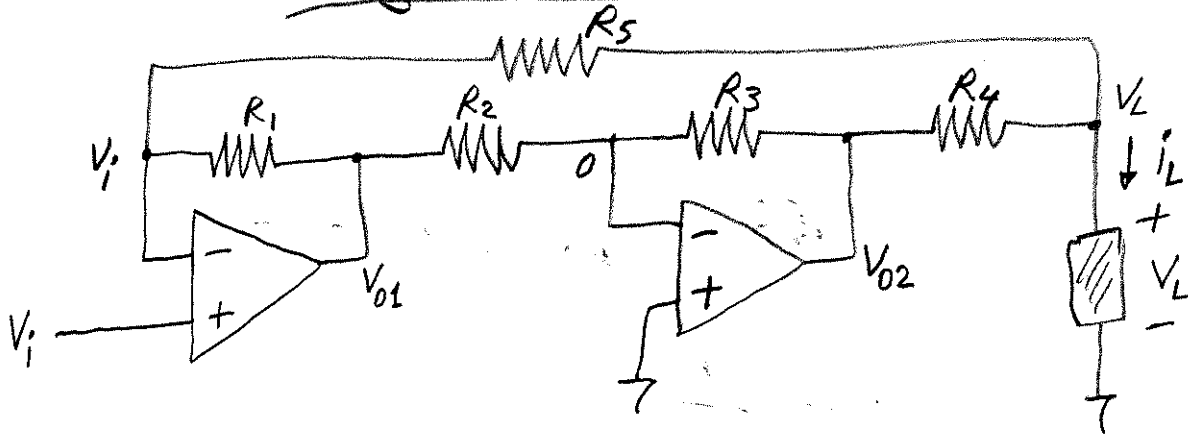

$$\frac{V_L - V_i}{R_5} + \frac{V_{01} - V_i}{R_1} = 0 \rightarrow V_{01} = \left(1 + \frac{R_1}{R_5}\right) V_i - \frac{R_1}{R_5} V_L$$

$$\frac{V_{01}}{R_2} + \frac{V_{02}}{R_3} = 0 \rightarrow V_{02} = -\frac{R_3}{R_2} V_{01} = \frac{R_1 R_3}{R_2 R_5} V_L - \left(1 + \frac{R_1}{R_5}\right) \frac{R_3}{R_2} V_i$$

$$i_L = \frac{V_{02} - V_L}{R_4} + \frac{V_i - V_L}{R_5} = \frac{V_i}{R_5} + \frac{V_{02}}{R_4} - \frac{V_L}{R_4} - \frac{V_L}{R_5}$$

$$= \frac{V_i}{R_5} + \frac{R_1 R_3}{R_2 R_4 R_5} V_L - \left(1 + \frac{R_1}{R_5}\right) \frac{R_3}{R_2 R_4} V_i - \frac{V_L}{R_4} - \frac{V_L}{R_5}$$

$$= \left(\frac{1}{R_5} - \left(1 + \frac{R_1}{R_5}\right) \frac{R_3}{R_2 R_4}\right) V_i + \left(\frac{R_1 R_3}{R_2 R_4 R_5} - \frac{1}{R_4} - \frac{1}{R_5}\right) V_L$$

$$\left(\frac{R_2 R_4 - R_3 R_5 - R_1 R_3}{R_2 R_4 R_5}\right) V_i - \left(\frac{R_1 R_3 - R_2 R_5 - R_2 R_4}{R_2 R_4 R_5}\right) V_L$$



$R_1 = R_2 = R_3 = R_4 + R_5 = R$  olsun

$$i_L = \left(\frac{R R_4 - R R_5 - R \cdot R}{R R_4 R_5}\right) V_i - \left(\frac{R \cdot R - R R_5 - R R_4}{R R_4 R_5}\right) V_L$$

$$= \frac{R_4 - R_5 - R}{R_4 R_5} V_i - \frac{R - (R_4 + R_5)}{R_4 R_5} V_L \rightarrow 0$$

$$= \frac{R - R_5 - R_5 - R}{R_4 R_5} V_i = -\frac{2}{R_4} V_i \quad (\text{sabit akım})$$

Norton eşdeğer devresi (34)

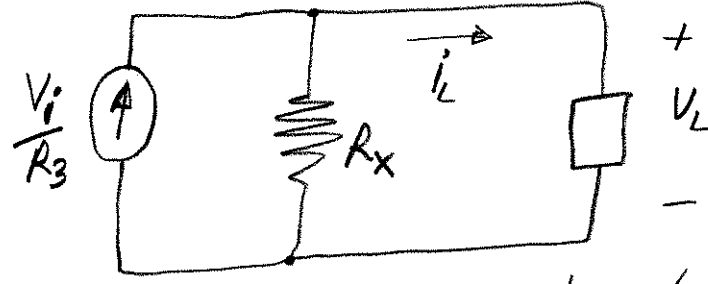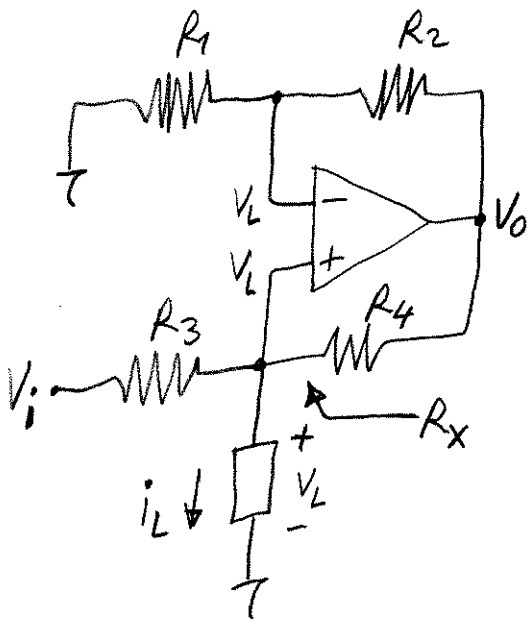

Asağıdaki denklem bu şekle getirilip  $R_x$  bulunur.

$$\frac{V_L}{R_1} + \frac{V_L - V_0}{R_2} = 0 \rightarrow V_0 = \left(1 + \frac{R_2}{R_1}\right) \cdot V_L$$

$$i_L = \frac{V_i - V_L}{R_3} + \frac{V_0 - V_L}{R_4} = \frac{V_i - V_L}{R_3} + \frac{\left(1 + \frac{R_2}{R_1}\right) V_L - V_L}{R_4}$$

$$= \frac{V_i}{R_3} - \frac{V_L}{R_3} + \frac{R_2}{R_1 R_4} V_L = \frac{V_i}{R_3} - \left(\frac{1}{R_3} - \frac{R_2}{R_1 R_4}\right) V_L$$

$$= \frac{V_i}{R_3} - \left(\frac{R_1 R_4 - R_2 R_3}{R_1 R_3 R_4}\right) V_L = \frac{V_i}{R_3} - \frac{V_L}{\frac{R_1 R_3 R_4}{R_1 R_4 - R_2 R_3}}$$



$$R_x = \frac{R_1 R_3 R_4}{R_1 R_4 - R_2 R_3} = \frac{R_4}{\frac{R_4}{R_3} - \frac{R_2}{R_1}}$$

$$\frac{R_4}{R_3} = \frac{R_2}{R_1} = k \text{ ise } R_x = \frac{R_4}{k - k} = \frac{R_4}{0} = \infty$$

Bu durumdan  $\rightarrow$  olur

$$i_L = \frac{V_i}{R_3} - \frac{V_L}{R_x} \Rightarrow i_L = \frac{V_i}{R_3}$$

# Kapasitör (C)

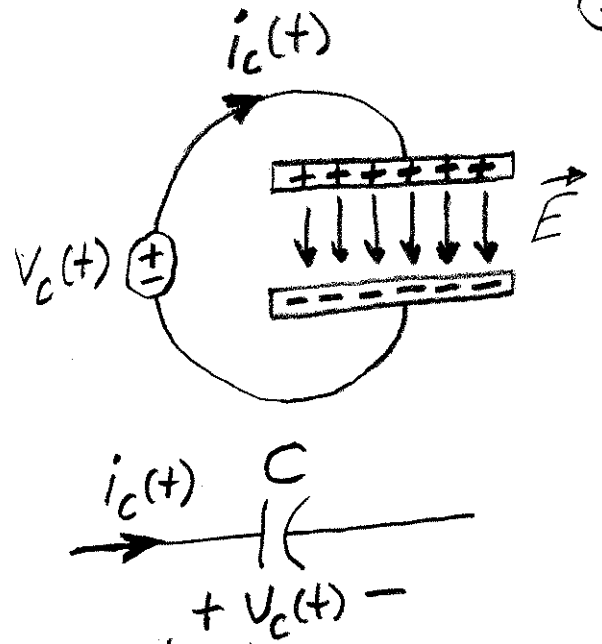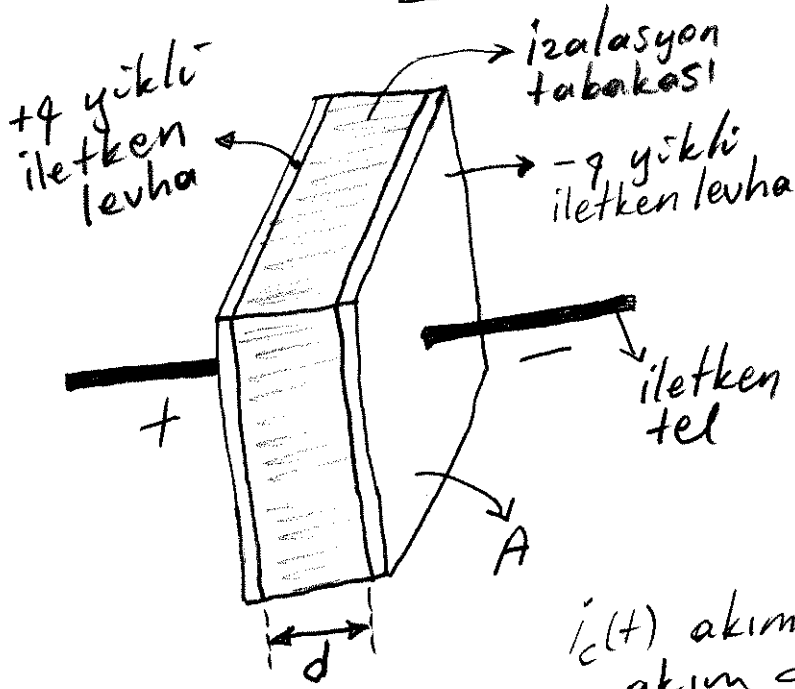

$i_C(t)$  akımı kapasitörden geçen akım değildir.

$d$ : levhalar arasındaki uzaklık veya izalasyon tabakasının kalınlığı

$A$ : Levhalardan birinin yüzey alanı

$\epsilon_0 = 8.85 \times 10^{-12} \text{ F/m}$   
Boşluğun veya havanın dielektrik katsayısı

izalasyon tabakası ince plastik bir yaprak olabildiği gibi arada boşlukta olabilir.

$\epsilon_r$ : Plakalar arasındaki yalıtıcının bağıl dielektrik katsayısı  
Boşluk için 1, Hava için  $\sim 1$ , Silikon için 12 alınır.

$$C = \epsilon \cdot \frac{A}{d} = \epsilon_r \epsilon_0 \frac{A}{d} = \epsilon_r C_0$$

Kapasitörün (veya Kondansatörün) şarj depolama kapasitesi, kapasitans olarak adlandırılır. Semboli  $C$ 'dir. Birimi ise Farad (F)'dir.

Kapasitör, enerjiyi elektrik alanında depolayan devre elemanıdır. Elektrik alan varsa kapasitif etki vardır. Potansiyel farkının değişmesi yüklerin değişmesiyle olur.

Kapasitörler, yüksek frekansta kısa devre özelliği gösterirler. Dolayısıyla tiz denilen yüksek frekansları geçirirler. Üzerlerindeki voltaj artıyorsa tüketici, azalıyorsa üretici konumundadırlar. Kapasitörler, radyo alıcılarında frekans ayarında, güç kaynaklarında filtre olarak, ateşleme sistemlerinde kıvılcımı yok etmede, elektronik flaş üniteleri gibi pek çok yerde kullanılır.

$$q(t) = C V(t) \Rightarrow C = \frac{q(t)}{V(t)}, \quad 1 \text{ Farad} = \frac{1 \text{ Coulomb}}{1 \text{ Volt}} \quad (36)$$

$$i_c(t) = \frac{dq(t)}{dt} = C \frac{dV_c(t)}{dt}$$


$$V_c(t) = \frac{1}{C} \int_{-\infty}^t i_c(z) dz = V_c(t_0) + \frac{1}{C} \int_{t_0}^t i_c(z) dz$$

$$P_c(t) = \frac{dw_c(t)}{dt} = \frac{dw_c(t)}{dq(t)} \frac{dq(t)}{dt} = V_c(t) \cdot i_c(t)$$

$$= V_c(t) \cdot C \frac{dV_c(t)}{dt} = \frac{d}{dt} \left( \frac{1}{2} C V_c^2(t) \right)$$

$$W_c(t) = \frac{1}{2} C V_c^2(t) = \frac{q^2(t)}{2C} = \frac{q(t) V_c(t)}{2}$$

### Kapasitörlerin Seri Bağlanması

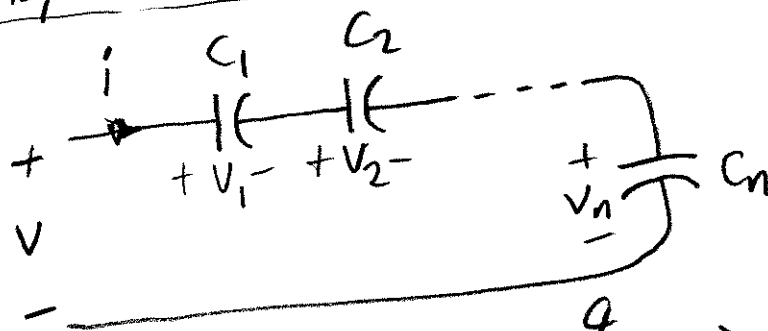


$$q = q_1 = q_2 = \dots = q_n$$

$$i = i_1 = i_2 = \dots = i_n$$

$$V = V_1 + V_2 + \dots + V_n$$

$$\frac{q}{C_e} = \frac{q}{C_1} + \frac{q}{C_2} + \dots + \frac{q}{C_n} \Rightarrow \frac{1}{C_e} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$$

### Kapasitörlerin Paralel Bağlanması

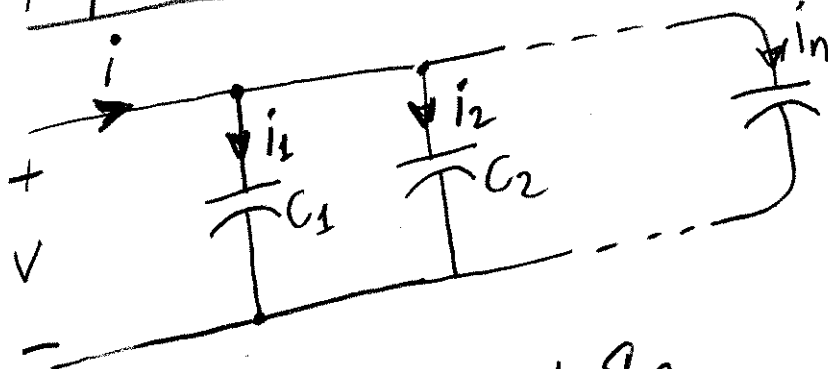

$$q = q_1 + q_2 + \dots + q_n$$

$$i = i_1 + i_2 + \dots + i_n$$


$$V = V_1 = V_2 = \dots = V_n$$

$$q = q_1 + q_2 + \dots + q_n$$


$$C_e V = C_1 V + C_2 V + \dots + C_n V \Rightarrow C_e = C_1 + C_2 + \dots + C_n$$

# İndüktör (L)

(37)

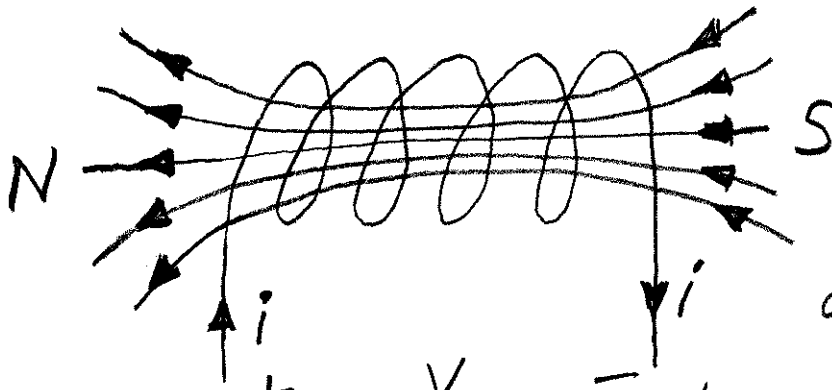

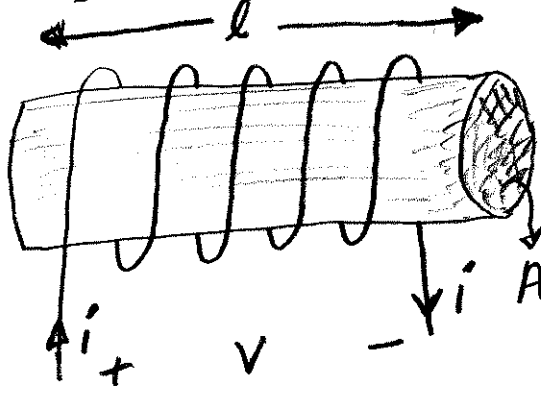akım manyetik alan oluşturduğu gibi tersi de doğrudur.



iletken bir telden akım geçince etrafında manyetik alan oluşur. İletken tel bobin haline getirilirse oluşan manyetik alan düz bir mıknatısınkine benzer. Bobinden geçen

İndüktör (Endüktans, Bobin) in Sembolü L, Birimi Henry (H) dir.

n : Sarım sayısı  
A : Yüzey alanı  
l : Uzunluk

$$L = \mu \frac{n^2 A}{l} = \mu_r \mu_0 \frac{n^2 A}{l} = \mu_r L_0$$

$$\mu_0 = 4\pi \times 10^{-7}$$

Boşluğun manyetik alan geçirgenliği


$\mu_r$  : Bağıl manyetik alan geçirgenlik katsayısı

Boşluk için 1, Hava için  $\sim 1$ , Demir nüvesi için 400 alınır.

Bobin enerjisi manyetik alanda depolayan devre elemanıdır. Pratikte bobin emaye telden sarılarak elde edilir. Bu teli azda olsa bir direnci vardır. İdeal bobinin iç direnci sıfır alınır.

Bobinde manyetik alan oluşturmak için zamana ihtiyaç vardır. Bobinden geçen akım kesildiğinde manyetik alan birden yok olmaz. Manyetik alanın yok olması için yine zamana ihtiyaç vardır.

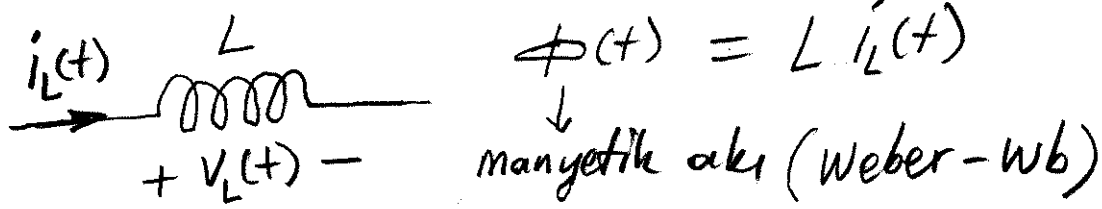Bobin üzerinden geçen akıma tepki gösterir. Geçen akım DC ise uçları arasındaki gerilim sıfırdır. AC bir akımda frekans artması endüktans gerilimini artırır. Yüksek frekansta akım devre, düşük frekansta kısa devre olur. Bass denilen düşük frekansları geçirir. Endüktans enerji çekiyorsa tüketici konumunda, enerji veriyorsa üretici konumundadır.



$$V_L(t) = \frac{d\Phi(t)}{dt} = L \frac{di_L(t)}{dt}$$


$$i_L(t) = \frac{1}{L} \int_{-\infty}^t V_L(z) dz = i_L(t_0) + \frac{1}{L} \int_{t_0}^t V_L(z) dz$$

$$P_L(t) = \frac{dW_L}{dt} = V_L(t) i_L(t) = L \frac{di_L}{dt} \cdot i_L(t) = \frac{d}{dt} \left( \frac{1}{2} L i_L^2(t) \right)$$

$$W_L(t) = \frac{1}{2} L i_L^2(t) = \frac{\Phi^2(t)}{2L} = \frac{\Phi(t) \cdot i_L(t)}{2}$$

Bir bobindeki akım değişim hızı 1A/sn ve bu değişime karşı koyan endüksiyon peritimi 1V ise bobinin endüktansı 1H'dir.

### İndüktörlerin Seri Bağlanması

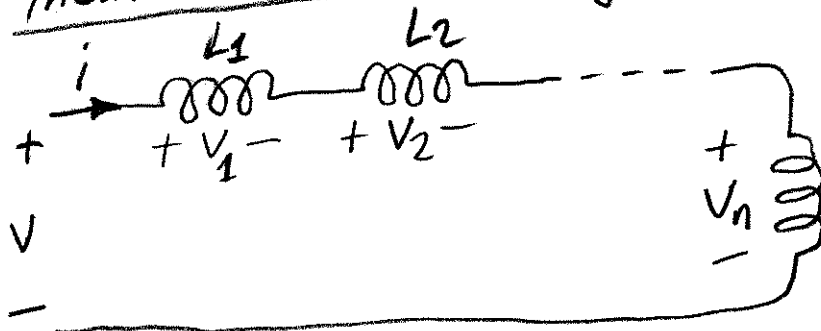

$$\Phi = \Phi_1 + \Phi_2 + \dots + \Phi_n$$


$$V = V_1 + V_2 + \dots + V_n$$

$$i = i_1 = i_2 = \dots = i_n$$

$$\Phi = \Phi_1 + \Phi_2 + \dots + \Phi_n$$

$$L_e i = L_1 i + L_2 i + \dots + L_n i \Rightarrow L_e = L_1 + L_2 + \dots + L_n$$

### İndüktörlerin Paralel Bağlanması

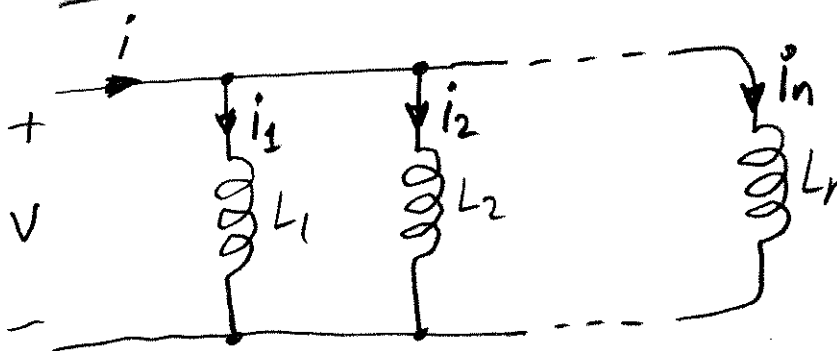

$$\Phi = \Phi_1 = \Phi_2 = \dots = \Phi_n$$

$$V = V_1 = V_2 = \dots = V_n$$

$$i = i_1 + i_2 + \dots + i_n$$

$$i = i_1 + i_2 + \dots + i_n$$

$$\frac{\Phi}{L_e} = \frac{\Phi}{L_1} + \frac{\Phi}{L_2} + \dots + \frac{\Phi}{L_n} \Rightarrow \frac{1}{L_e} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n}$$

5  $\mu\text{F}$ 'lık bir kapasitörün uçlarına 12V'luk bir gerilim uygulanıyor. Plakalarda biriken yükü bulunuz. Kapasitörde depolanan enerjiyi bulunuz. (39)

$$C = 5 \mu\text{F} \quad q = CV_c = 5 \mu\text{F} \times 12\text{V} = 60 \mu\text{C}$$

$$V_c = 12\text{V} \quad W = \frac{1}{2} CV_c^2 = \frac{1}{2} \times 5 \mu\text{F} \times (12\text{V})^2 = 0.36 \text{ mJ}$$

Bir kapasitörde plakalar arası 3mm, plakaların yüzey alanı 15  $\text{cm}^2$  olsun. Plakalar arasındaki yalıtken malzemenin bağıl dielektrik katsayısı 4 olsun.

- a) Kapasitörün kapasitesi nedir?  
b) Yalıtken malzemenin dayanabileceği max. elektrik alanı 10<sup>5</sup> ise kapasitörün taşıyabileceği max. voltaj ve yük nedir?

a)  $\epsilon_r = 4$ ,  $d = 3\text{mm} = 3 \times 10^{-3} \text{ m}$ ,  $A = 15\text{cm}^2 = 15 \times 10^{-4} \text{ m}^2$

$$C = \epsilon \frac{A}{d} = \epsilon_r \epsilon_0 \frac{A}{d}$$
$$= 4 \times 8.85 \times 10^{-12} \frac{15 \times 10^{-4}}{3 \times 10^{-3}} \text{ F} = 17.7 \text{ pF}$$

b)  $V = E \cdot d = 10^5 \frac{\text{V}}{\text{m}} \times 3 \times 10^{-3} \text{ m} = 300 \text{ V}$

$$Q = CV = 17.7 \text{ pF} \times 300 \text{ V} = 5.31 \text{ nC}$$

500 sarımlı bir bobinin uzunluğu 6cm, kullanılan telin kesit alanı 12  $\text{cm}^2$ 'dir.

a) Bobin nüveliz ise Endüktansı

b) Bobin nüveli ise Endüktansı. ( $\mu_r = 250$  olsun)

$$n = 500, \quad l = 6\text{cm} = 6 \times 10^{-2} \text{ m}, \quad A = 12\text{cm}^2 = 12 \times 10^{-4} \text{ m}^2$$

a)  $L_0 = \mu_0 \frac{n^2 A}{l} = 4\pi \times 10^{-7} \frac{500^2 \times 12 \times 10^{-4}}{6 \times 10^{-2}} \text{ F}$

$$= 4\pi \times 10^{-7} \frac{25 \times 12 \times 100}{6} \text{ F} = 6.28 \text{ mF}$$

b)  $L = \mu_r L_0 = 250 \times 6.28 \text{ mF} = 1.57 \text{ F}$



Bir bobinden geçen akım 0.25 sn'de 2A'den 5A'ye (40) çıktığında üzerinde 6V'luk endüksiyon gerilimi oluşuyor. Bobinin endüktansını bulunuz.

$$\Delta t = 0.25 \text{ sn}$$

$$\Delta I = 5A - 2A = 3A$$



$$V = L \frac{\Delta I}{\Delta t} \Rightarrow L = V \cdot \frac{\Delta t}{\Delta I}$$
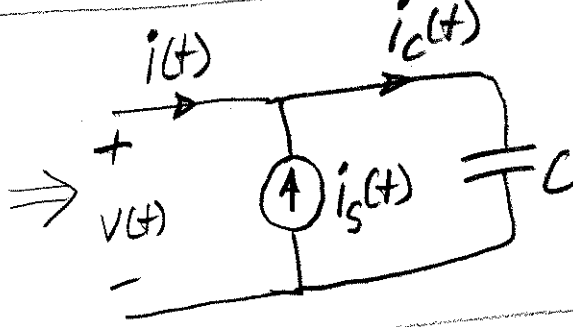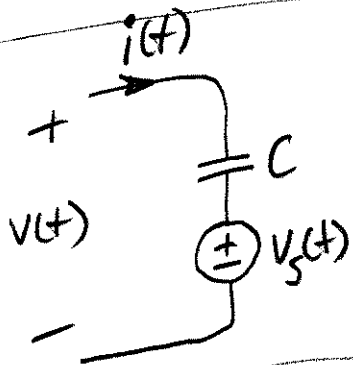
$$L = 6V \frac{0.25 \text{ sn}}{3A} = 0.5 \text{ H}$$







$$i_s(t) = C \frac{dV_s(t)}{dt}$$
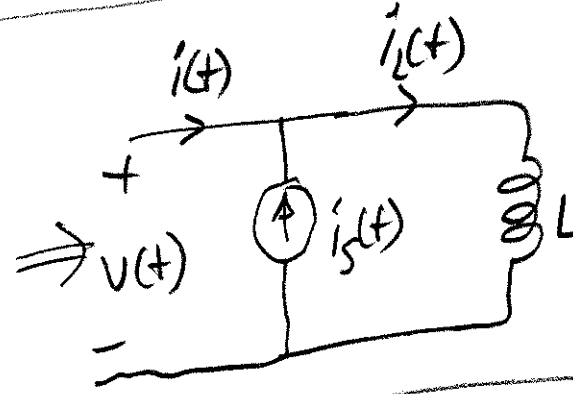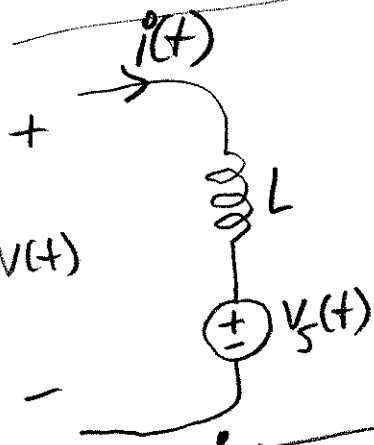
$$V_s(t) = \frac{1}{C} \int_{-\infty}^t i_s(z) dz$$



$$V_s(t) = L \frac{di_s(t)}{dt}$$
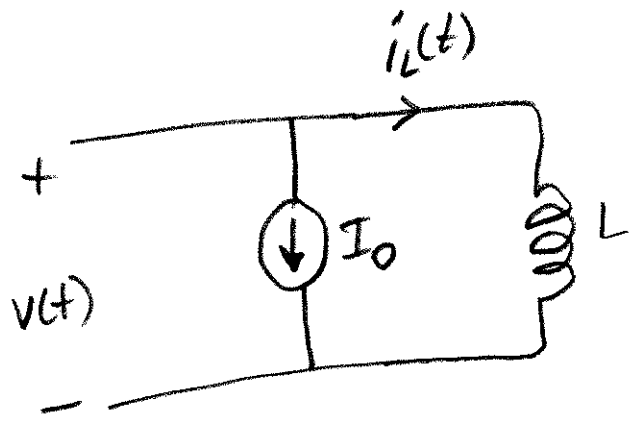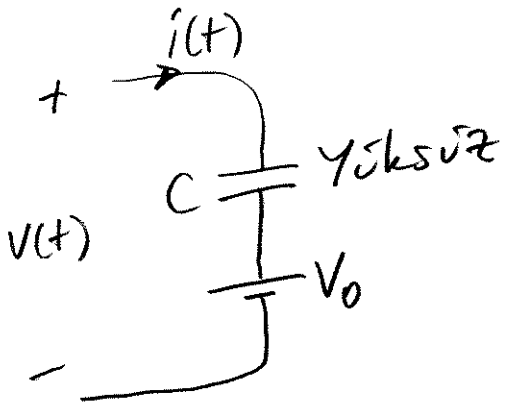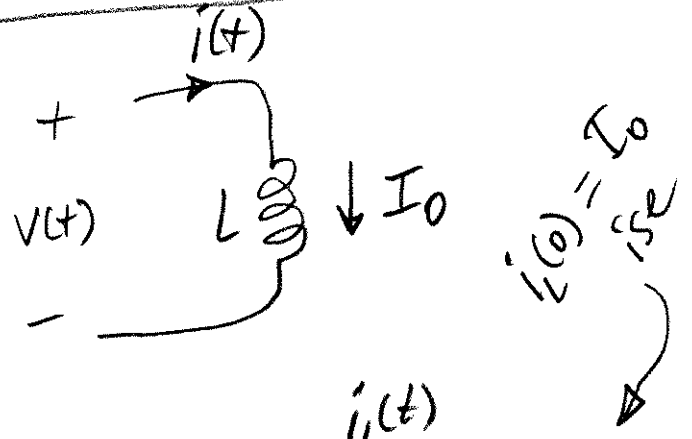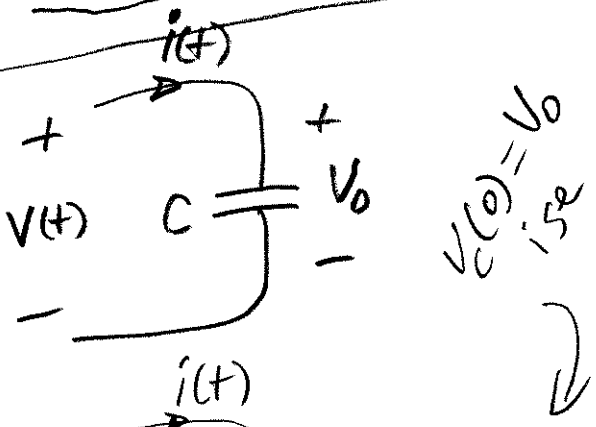
$$i_s(t) = \frac{1}{L} \int_{-\infty}^t V_s(z) dz$$



$$V_c(0) = 0$$

$$i_L(0) = 0$$





# Dalga Formları

(41)

① Sabit Fonksiyon  $f(t) = A$

② Sinüzoidal Fonksiyon  $f(t) = A \cdot \sin(\omega t + \alpha)$ ,  $\omega = 2\pi f = 2\pi/T$

③ Birim Dürtü Fonksiyonu

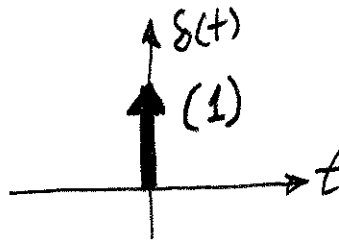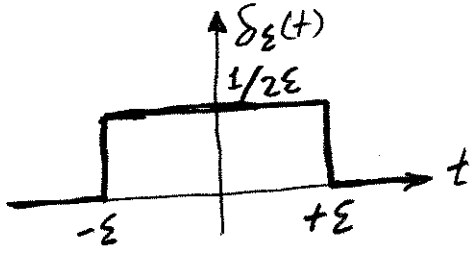

$$\int_{-\infty}^{\infty} \delta_{\epsilon}(t) dt = \int_{-\epsilon}^{\epsilon} \delta_{\epsilon}(t) dt = 1$$

$$\int_{-\infty}^{\infty} \delta(t) dt = \int_{0^-}^{0^+} \delta(t) dt = 1$$

$\epsilon \rightarrow 0$  için  $\delta_{\epsilon}(t) \rightarrow \delta(t)$  olur.



$\delta(-t) = \delta(t)$  çift fonksiyon

$$\delta(at) = \delta(t)/|a|$$

$$\int_{-\infty}^{\infty} x(t) \delta(t) dt = \int_{-\infty}^{\infty} x(0) \cdot \delta(t) dt = x(0) \int_{-\infty}^{\infty} \delta(t) dt = x(0)$$

$$x(t) = \int_{-\infty}^{\infty} x(z) \delta(t-z) dz = x(t) * \delta(t)$$

④ Birim Basamak Fonksiyonu

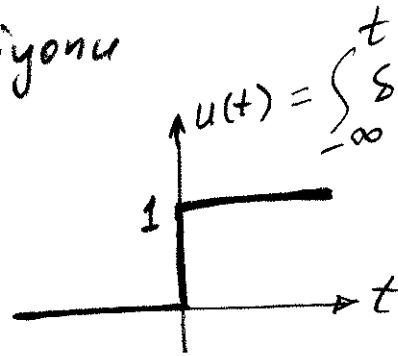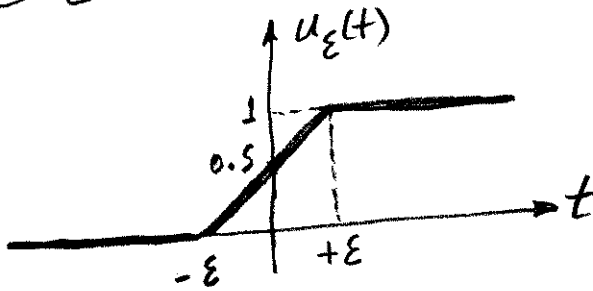


$$u(t) = \int_{-\infty}^t \delta(z) dz = \begin{cases} 1 & t > 0 \\ 0 & t < 0 \\ 1/2 & t = 0 \end{cases}$$

$\epsilon \rightarrow 0$  için  $u_{\epsilon}(t) \rightarrow u(t)$  olur.



$$u(0^-) = 0, u(0^+) = 1 \quad \delta(t) = \frac{du(t)}{dt} = u'(t)$$


⑤ Birim Rampa Fonksiyonu

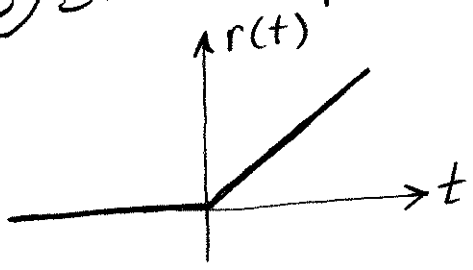


$$r(t) = \int_{-\infty}^t u(z) dz = t u(t) = \begin{cases} t, & t \geq 0 \\ 0, & t < 0 \end{cases}$$

$$u(t) = r'(t) = \frac{dr(t)}{dt}$$

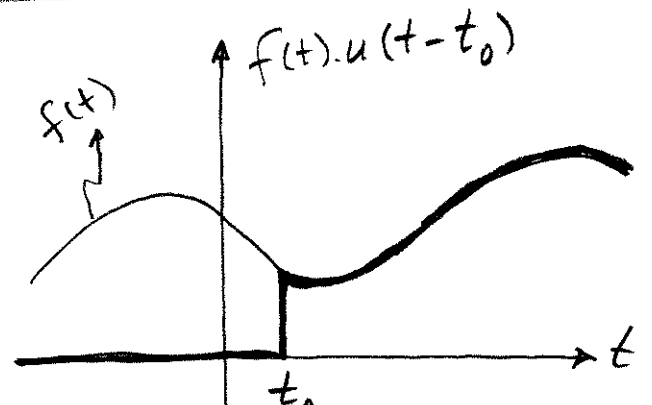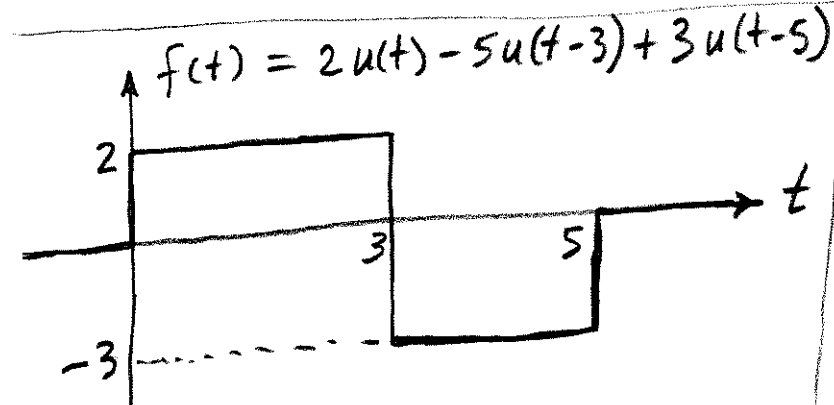


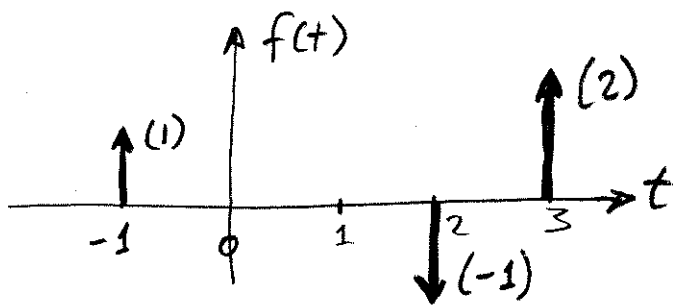
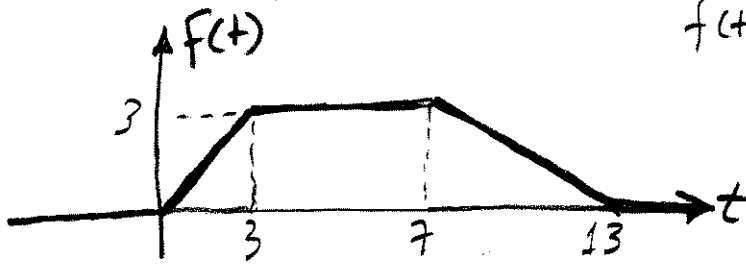
$$f(t) = \delta(t+1) - \delta(t-2) + 2\delta(t-3)$$



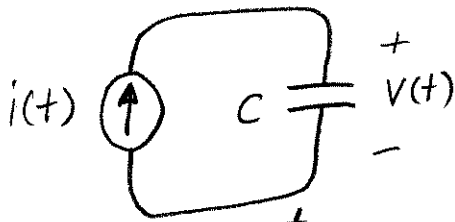
$$f(t) = r(t) - r(t-3) - 0.5r(t-7) + 0.5r(t-13)$$



$i(t) = 3u(t) - 5u(t-2) + 2u(t-5)$   
 $C = 3F$  ise  $v(t)$ ,  $p(t)$  bulunuz.  
 Ve grafiklerini çiziniz.

$$v(t) = \frac{1}{C} \int_{-\infty}^t i(z) dz = \int_{-\infty}^t u(z) dz - \frac{5}{3} \int_{-\infty}^t u(z-2) dz + \frac{2}{3} \int_{-\infty}^t u(z-5) dz$$
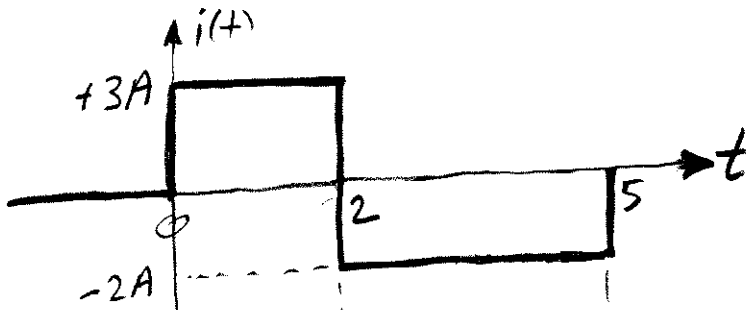
$$= r(t) - \frac{5}{3} r(t-2) + \frac{2}{3} r(t-5)$$



$$p(t) = v(t) \cdot i(t)$$

$$= 3r(t) - 3r(t-2)$$



$$- 10u(t-2)$$


$$+ \frac{4}{3} r(t-2)$$

$$- \frac{4}{3} r(t-5)$$

$$r(t) = 3r(t) - \frac{5}{3} r(t-2)$$

$$- 10u(t-2) - \frac{4}{3} r(t-5)$$

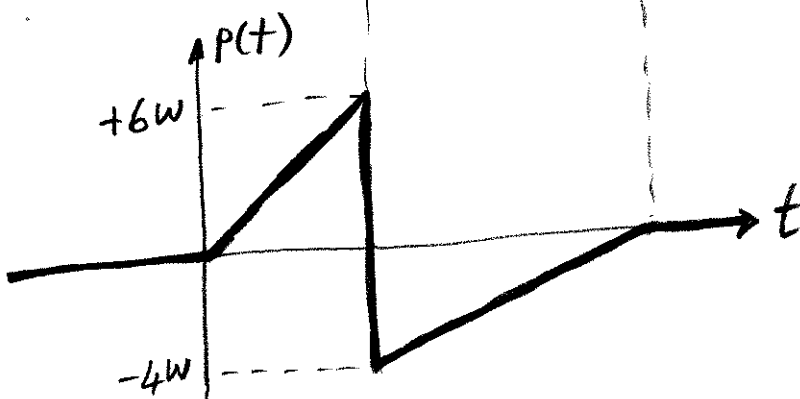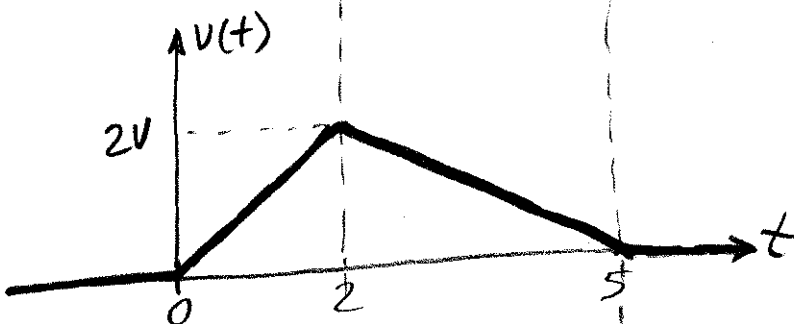

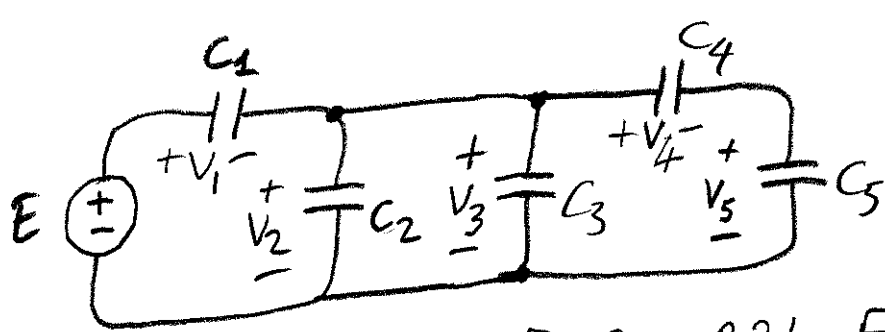

Herbir kapasitör üzerindeki yük ve voltajları bulunuz. (43)

$$E = 24V, C_1 = 0.3mF, C_2 = 0.24mF, C_3 = 0.18mF$$

$$C_4 = 0.3mF, C_5 = 0.45mF$$

$$C_e = C_1 \text{ } \$ \text{ } (C_2 + C_3 + C_4 \text{ } \$ \text{ } C_5)$$

$$= 0.3mF \text{ } \$ \text{ } (0.24mF + 0.18mF + 0.3mF \text{ } \$ \text{ } 0.45mF)$$

$$= 0.3mF \text{ } \$ \text{ } (0.42mF + \frac{0.3 \times 0.45}{0.75} mF)$$

$$= 0.3mF \text{ } \$ \text{ } (0.42mF + 0.18mF)$$

$$= 0.3mF \text{ } \$ \text{ } 0.6mF = \frac{0.3 \times 0.6}{0.9} mF = 0.2mF$$

$$Q = C_e E = 0.2mF \times 24V = 4.8mC$$

$$Q_1 = Q = 4.8mC \quad V_1 = \frac{Q_1}{C_1} = \frac{4.8mC}{0.3mF} = 16V$$

$$V_2 = V_3 = E - V_1 = 24V - 16V = 8V$$

$$Q_2 = C_2 V_2 = 0.24mF \times 8V = 1.92mC$$


$$Q_3 = C_3 V_3 = 0.18mF \times 8V = 1.44mC$$

$$Q_4 = Q_5 = (C_4 \text{ } \$ \text{ } C_5) V_3 = (0.3mF \text{ } \$ \text{ } 0.45mF) \times 8V$$

$$= 0.18mF \times 8V = 1.44mC$$

$$V_4 = \frac{Q_4}{C_4} = \frac{1.44mC}{0.3mF} = 4.8V$$
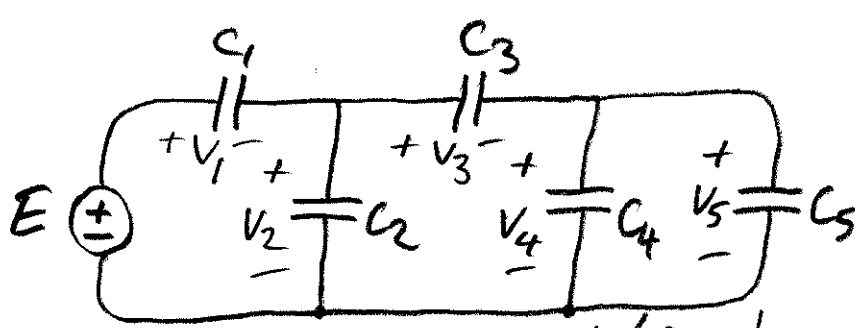
$$V_5 = \frac{Q_5}{C_5} = \frac{1.44mC}{0.45mF} = 3.2V$$



$$E = 25V, C_1 = 30\text{mF} \quad (44)$$

$$C_2 = 24\text{mF}, C_3 = 30\text{mF}$$

$$C_4 = 20\text{mF}, C_5 = 50\text{mF}$$

Herbir kapasitor üzerindeki yük ve voltajları bulunuz.

$$\begin{aligned} C_e &= C_1 \parallel (C_2 + C_3 \parallel (C_4 + C_5)) \\ &= 30\text{mF} \parallel (24\text{mF} + 30\text{mF} \parallel (20\text{mF} + 50\text{mF})) \\ &= 30\text{mF} \parallel (24\text{mF} + 30\text{mF} \parallel 70\text{mF}) \\ &= 30\text{mF} \parallel (24\text{mF} + 21\text{mF}) \\ &= 30\text{mF} \parallel 45\text{mF} = 18\text{mF} \end{aligned}$$

$$Q = C_e E = 18\text{mF} \times 25V = 450\text{mC}$$

$$Q_1 = Q = 450\text{mC} \quad V_1 = \frac{Q_1}{C_1} = \frac{450\text{mC}}{30\text{mF}} = 15V$$

$$V_2 = E - V_1 = 25V - 15V = 10V$$

$$Q_2 = C_2 V_2 = 24\text{mF} \times 10V = 240\text{mC}$$


$$Q_3 = Q_1 - Q_2 = 450\text{mC} - 240\text{mC} = 210\text{mC}$$

$$V_3 = \frac{Q_3}{C_3} = \frac{210\text{mC}}{30\text{mF}} = 7V$$

$$V_4 = V_5 = V_2 - V_3 = 10V - 7V = 3V$$

$$Q_4 = C_4 V_4 = 20\text{mF} \times 3V = 60\text{mC}$$
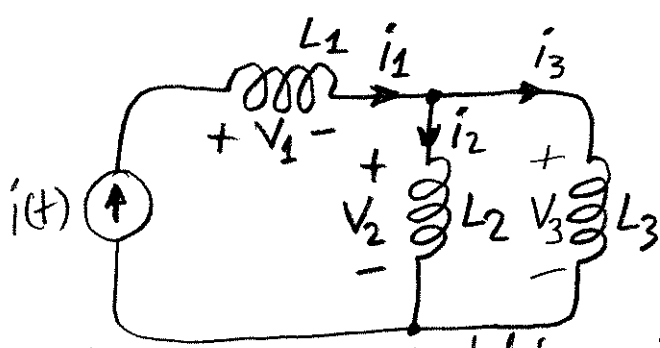
$$Q_5 = C_5 V_5 = 50\text{mF} \times 3V = 150\text{mC}$$



$$L_1 = 12H, L_2 = 10H, L_3 = 15H$$

$$i(t) = (5 - 3e^{-2t})u(t)$$

Eşdeğer endüktansı, toplam manyetik akıyı bulunuz.

Herbir bobin üzerindeki manyetik akıyı, akımı ve voltajı bulunuz.  $t = 0^+$  ve  $t = \infty$  anlarındaki bobinler üzerindeki voltaj ve akımları bulunuz.

$$L_e = 12H + 10H // 15H = 12H + 6H = 18H$$

$$\Phi(t) = L_e i(t) = (90 - 54e^{-2t})u(t)$$

$$i_1(t) = i(t) = (5 - 3e^{-2t})u(t)$$

$$\Phi_1(t) = L_1 i_1(t) = (60 - 36e^{-2t})u(t)$$

$$V_1(t) = \frac{d\Phi_1(t)}{dt} = 72e^{-2t}u(t) + \cancel{24\delta(t)}$$

$$\Phi_2(t) = \Phi_3(t) = \Phi(t) - \Phi_1(t) = (30 - 18e^{-2t})u(t)$$

$$V_2(t) = V_3(t) = \frac{d\Phi_2}{dt} = 36e^{-2t}u(t) + \cancel{12\delta(t)}$$


$$i_2(t) = \frac{\Phi_2(t)}{L_2} = (3 - 1.8e^{-2t})u(t)$$

$$i_3(t) = \frac{\Phi_3(t)}{L_3} = (2 - 1.2e^{-2t})u(t)$$

$i(\infty)$   
 $v(\infty)$

$$i_1(0^+) = 2A, i_2(0^+) = 1.2A, i_3(0^+) = 0.8A$$
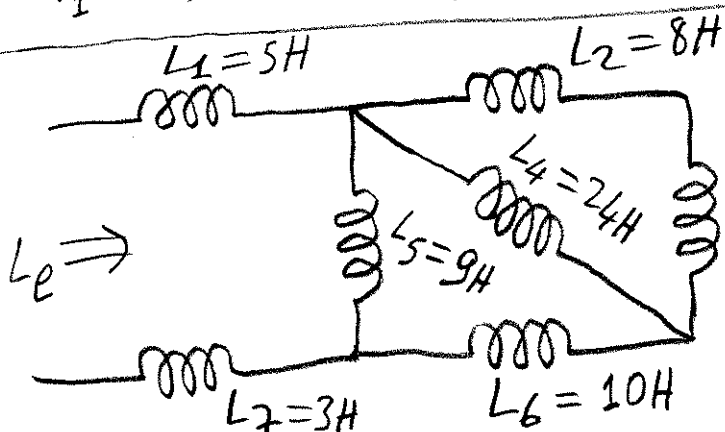
$$V_1(0^+) = 72V, V_2(0^+) = V_3(0^+) = 36V$$




$$L_e = L_1 + L_x + L_7$$

$$L_x = L_5 // (L_6 + L_4 // (L_2 + L_3))$$

$$L_x = 9 // (10 + 24 // 12)H = 6H$$

$$L_e = 5H + 6H + 3H = 14H$$

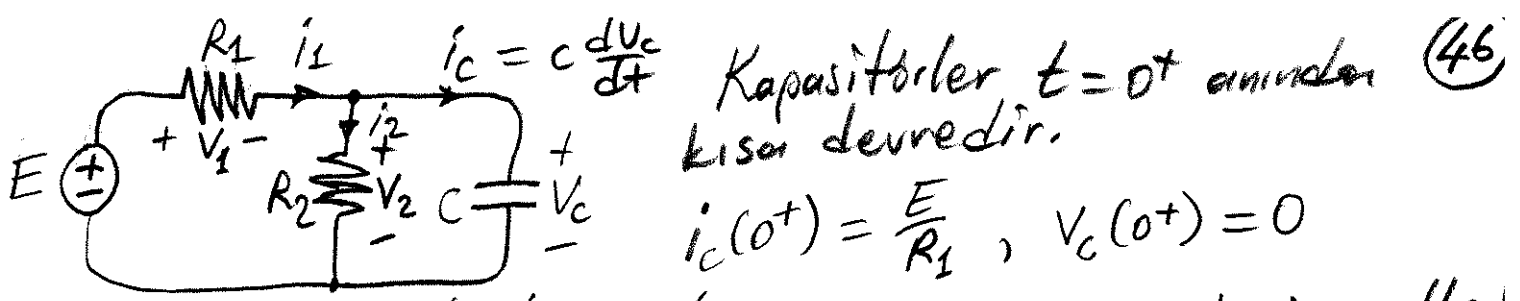

Kapasitörler  $t = 0^+$  anında kısa devredir. (46)


$$i_c(0^+) = \frac{E}{R_1}, \quad V_c(0^+) = 0$$

$t \rightarrow \infty$  iken açık devre olur.

$$i_c(\infty) = 0, \quad V_c(\infty) = V_2(\infty) = \frac{R_2 E}{R_1 + R_2}$$

Kapasitörün yaklaşık dolma süresi  $5\tau$  alınır.
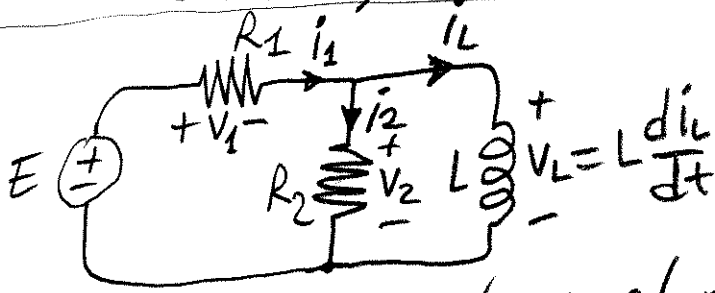
$$\tau = (R_1 \parallel R_2) \cdot C \text{ zaman sabitesi}$$



İndüktör  $t = 0^+$  anında açık devredir.


$$i_L(0^+) = 0, \quad V_L(0^+) = \frac{R_2 E}{R_1 + R_2}$$

$t \rightarrow \infty$  iken kısa devre olur.

$$i_L(\infty) = E/R_1, \quad V_L(\infty) = 0$$

$$\tau = \frac{L}{R_1 \parallel R_2} \text{ zaman sabitesi}$$

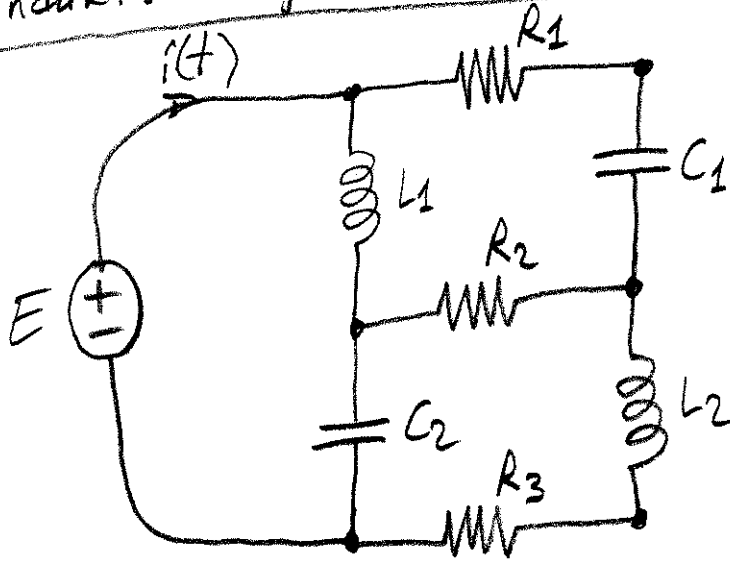İndüktörün yaklaşık kısa devre olma süresi  $5\tau$  alınır.



$t = 0^+$  anında kapasitörler kısa devre, bobinler açık devredir.

$$i(0^+) = i_{C1}(0^+) = i_{C2}(0^+)$$

$$= \frac{E}{R_1 + R_2}$$

$$i_{L1}(0^+) = i_{L2}(0^+) = 0$$

$$V_{C1}(0^+) = V_{C2}(0^+) = 0$$

$$V_{L1}(0^+) = E, \quad V_{L2}(0^+) = R_2 i(0^+) = \frac{R_2 E}{R_1 + R_2}$$

$t \rightarrow \infty$  iken kapasitörler açık devre, bobinler kısa devre olur.

$$i(\infty) = i_{L1}(\infty) = i_{L2}(\infty) = \frac{E}{R_2 + R_3}$$

$$V_{L1}(\infty) = V_{L2}(\infty) = 0$$


$$V_{C1}(\infty) = R_2 i(\infty) = \frac{R_2 E}{R_2 + R_3}$$

$$V_{C2}(\infty) = E$$

$$i_{C1}(\infty) = i_{C2}(\infty) = 0$$

# Birinci Mertebeden Devreler

(47)

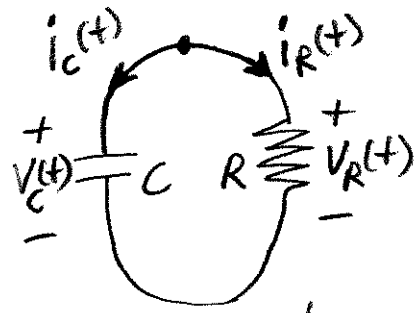

$$V_C(t) = V_R(t)$$

$$i_C(t) + i_R(t) = 0$$

$$C \frac{dV_C}{dt} + \frac{V_C}{R} = 0$$

$V_C(0^+) = V_0$  olsun


$\tau = RC$  Zaman Sabitesi

52 ise Durulma Zamanıdır.  
52'lik sürede kapasitörün boşaldığı (veya sabit bir voltaj) olduğu kabul edilir.

$$V_C(t) = A e^{-t/RC} u(t)$$


$$V_C(0^+) = A = V_0$$

$$V_C(t) = V_0 e^{-t/RC} u(t)$$

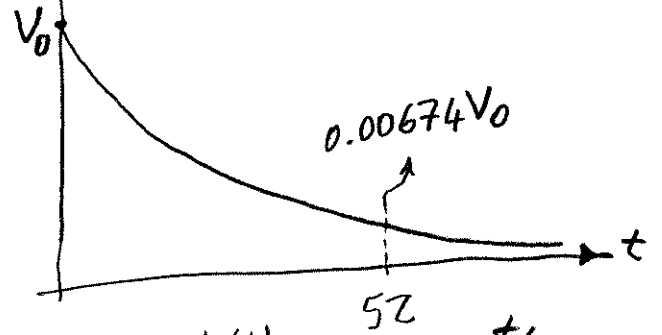

$$\frac{dV_C}{dt} + \frac{1}{RC} V_C = 0$$
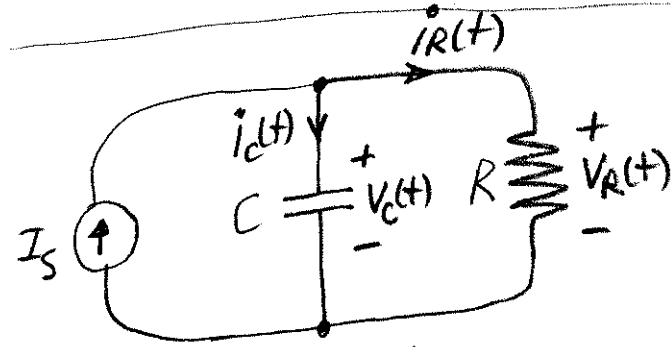
$$i_C(t) = C \frac{dV_C(t)}{dt} = -i_R(t) = -\frac{V_R(t)}{R} = -\frac{V_0}{R} e^{-t/RC} u(t)$$



$$V_C(t) = V_R(t)$$

$$i_C(t) + i_R(t) = I_S$$

$$C \frac{dV_C}{dt} + \frac{V_C}{R} = I_S$$

$$\frac{dV_C}{dt} + \frac{1}{RC} V_C = \frac{I_S}{C}$$

$\tau = RC$  Zaman Sabitesi

52 Durulma Zamanı

52'lik zamanda kapasitör sabit voltaj olur.

$V_C(0^+) = V_0$  olsun  
 $t = 0^+$  den itibaren devreye  $I_S$  sabit akımı veriliyor.


$$V_C(t) = (A e^{-t/RC} + B) u(t)$$

$$V_C(0^+) = A + B = V_0$$

$$V_C(\infty) = B = RI_S$$

$$A = V_0 - B$$

$$= V_0 - RI_S$$

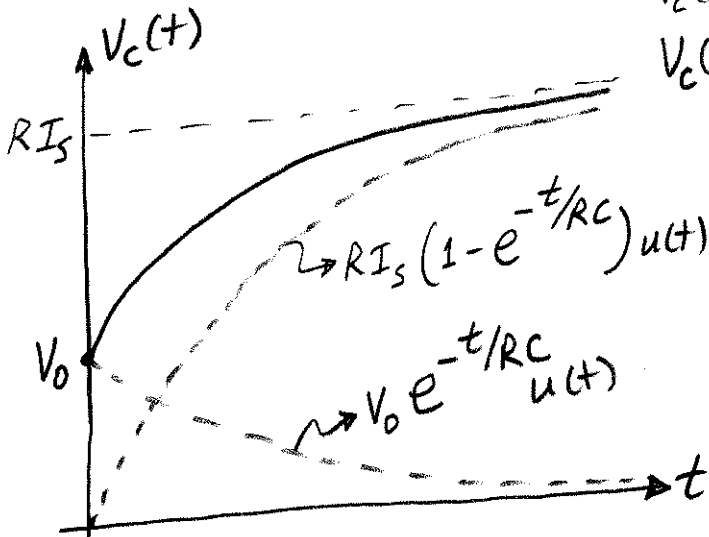


$$V_C(t) = ((V_0 - RI_S) e^{-t/RC} + RI_S) u(t)$$

$$= \underbrace{V_0 e^{-t/RC} u(t)}_{\text{Boşalma}} + \underbrace{RI_S (1 - e^{-t/RC}) u(t)}_{\text{Dolma}}$$

$$i_C(t) = C \frac{dV_C}{dt} = I_S - \frac{V_C(t)}{R}$$

$$= (I_S - \frac{V_0}{R}) e^{-t/RC} u(t)$$

$$i_C(0^+) = I_S - \frac{V_0}{R}$$

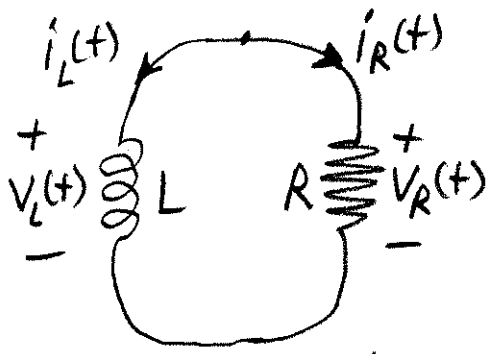

$$V_L(t) = V_R(t)$$

$$i_L(t) + i_R(t) = 0$$

$$i_L(t) + \frac{V_L(t)}{R} = 0$$

$$i_L(t) + \frac{L}{R} \frac{di_L(t)}{dt} = 0 \quad (48)$$

$$\frac{di_L}{dt} + \frac{R}{L} i_L = 0$$


$$i_L(0^+) = I_0 \text{ olsun}$$

$$i_L(t) = A e^{-t/RC} u(t) \quad i_L(0^+) = A = I_0$$


$\tau = L/R$  Zaman Sabitesi

52 ise Durulma Zamanıdır.

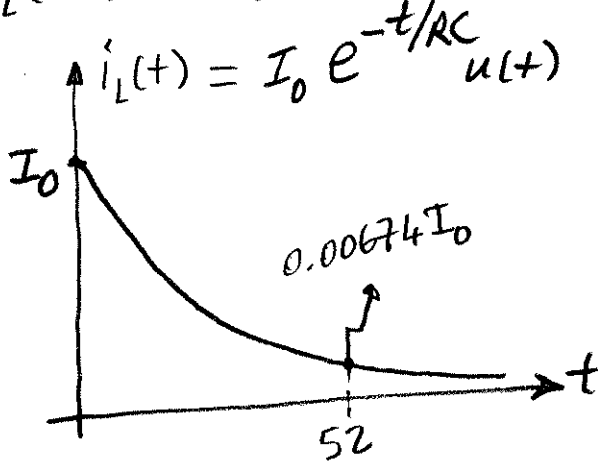52'lik sürede bobinden geçen akımın sıfır (veya sabit bir değer) olduğu kabul edilir.


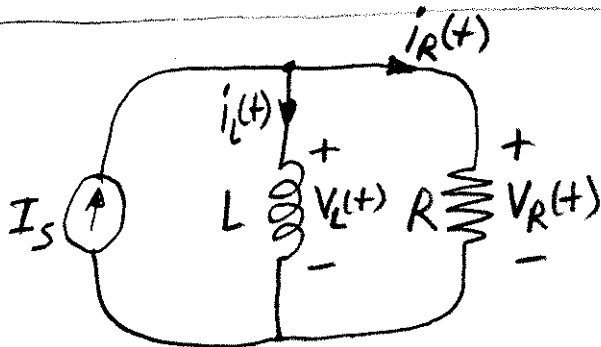
$$V_L(t) = V_R(t) = R i_R(t) = -R i_L(t) = -R I_0 e^{-Rt/L} u(t)$$



$$V_L(t) = V_R(t)$$

$$i_L(t) + i_R(t) = I_s$$

$$i_L(t) + \frac{V_L(t)}{R} = I_s$$

$$i_L(t) + \frac{L}{R} \frac{di_L}{dt} = I_s$$

$$\frac{di_L}{dt} + \frac{R}{L} i_L = \frac{R I_s}{L}$$

$$i_L(0^+) = I_0 \text{ olsun.}$$


$$i_L(t) = (A e^{-\frac{Rt}{L}} u(t) + B) u(t)$$

$t=0^+$ 'den itibaren devreye  $I_s$  sabit akımı veriliyor.

$$\left. \begin{aligned} i_L(0^+) &= A + B = I_0 \\ i_L(\infty) &= B = I_s \end{aligned} \right\} \begin{aligned} A &= I_0 - B \\ &= I_0 - I_s \end{aligned}$$

$$i_L(t) = ((I_0 - I_s) e^{-\frac{Rt}{L}} u(t) + I_s) u(t)$$
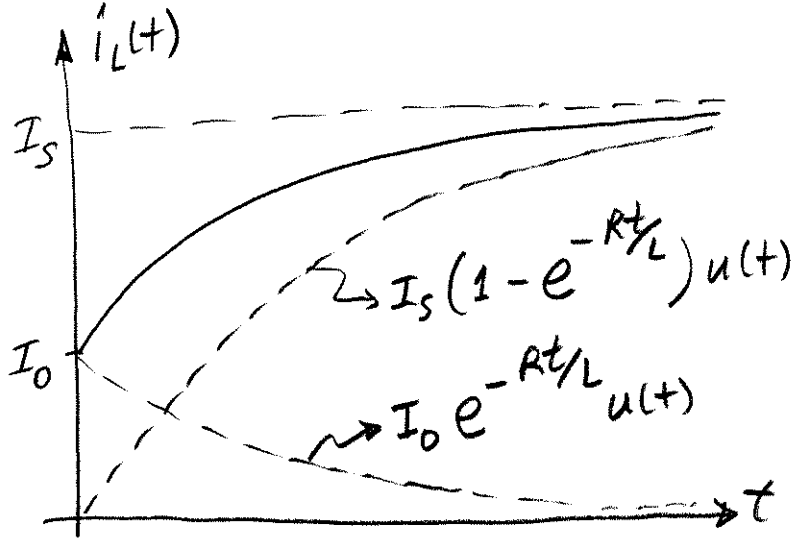
$$= \underbrace{I_0 e^{-\frac{Rt}{L}} u(t)}_{\text{Boşalma}} + \underbrace{I_s (1 - e^{-\frac{Rt}{L}}) u(t)}_{\text{Dolma}}$$




$$V_L(t) = L \frac{di_L}{dt} = V_R(t)$$


$$= R i_R(t) = R (I_s - i_L(t))$$
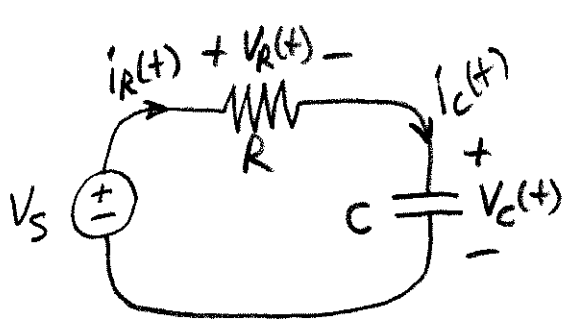
$$= R (I_s - I_0) e^{-\frac{Rt}{L}} u(t)$$





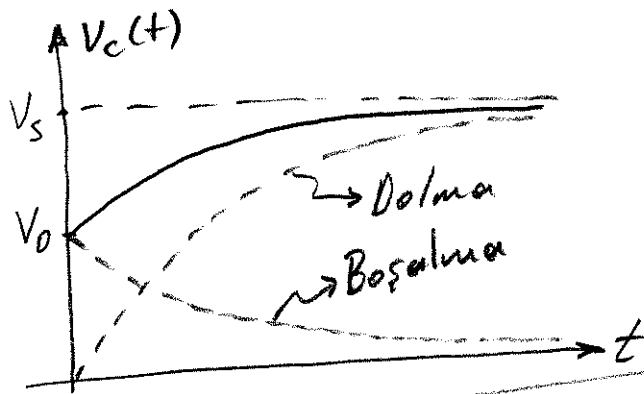$V_C(0^+) = V_0$  olsun.  
 $t=0^+$ 'den itibaren devreye  $V_s$  sabit voltajı veriliyor.



$$i_R(t) = i_C(t) = C \frac{dV_C(t)}{dt}$$

$$V_C(t) + V_R(t) = V_s \text{ göz önüne alarak}$$


$$\frac{dV_C}{dt} + \frac{1}{RC} V_C = \frac{V_s}{RC} \text{ elde edilir.}$$

$$V_C(t) = ((V_0 - V_s) e^{-t/RC} + V_s) u(t)$$


$$= \underbrace{V_0 e^{-t/RC} u(t)}_{\text{Boşalma}} + \underbrace{V_s (1 - e^{-t/RC}) u(t)}_{\text{Dolma}}$$

$$i_C(t) = C \frac{dV_C}{dt} = \frac{V_s - V_C}{R}$$

$$= \frac{V_s - V_0}{R} e^{-t/RC} u(t)$$

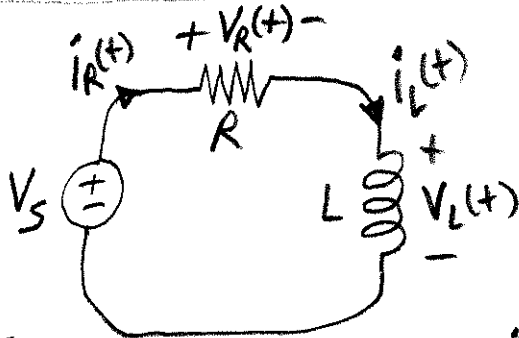

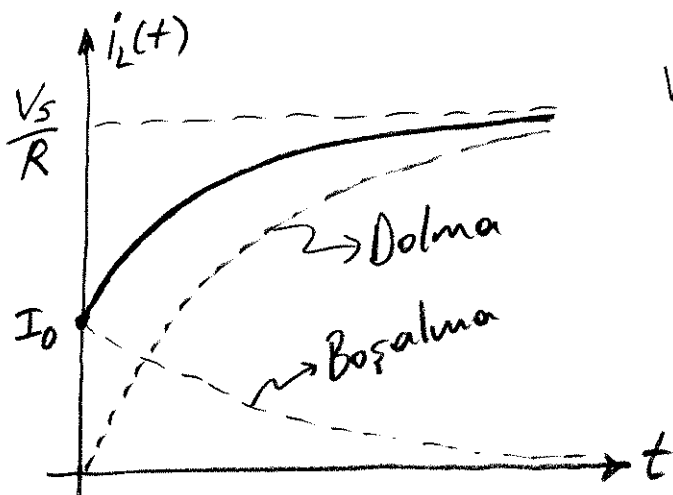$i_L(0^+) = I_0$  olsun.  
 $t=0^+$ 'den itibaren devreye  $V_s$  sabit voltajı veriliyor.



$$i_R(t) = i_L(t), \quad V_R(t) + V_L(t) = V_s$$

$$R i_L(t) + L \frac{di_L}{dt} = V_s \Rightarrow \frac{di_L}{dt} + \frac{R}{L} i_L = \frac{V_s}{L}$$

Dif. denklemi çözülürse

$$i_L(t) = \left( (I_0 - \frac{V_s}{R}) e^{-\frac{Rt}{L}} + \frac{V_s}{R} \right) u(t)$$

$$= \underbrace{I_0 e^{-\frac{Rt}{L}} u(t)}_{\text{Boşalma}} + \underbrace{\frac{V_s}{R} (1 - e^{-\frac{Rt}{L}}) u(t)}_{\text{Dolma}}$$


$$V_L(t) = L \frac{di_L(t)}{dt} = V_s - V_R(t)$$

$$= V_s - R i_L(t)$$

$$= (V_s - R I_0) e^{-\frac{Rt}{L}} u(t)$$

## İkinci Mertebeden Devreler

(50)

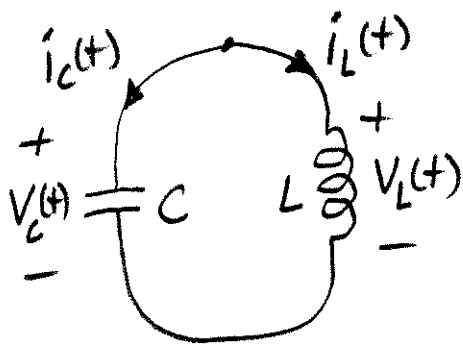

$$V_C(t) = V_L(t) = L \frac{di_L(t)}{dt}, \quad i_C(t) = C \frac{dV_C(t)}{dt}$$

$$i_C(t) + i_L(t) = 0 \Rightarrow C \frac{dV_C(t)}{dt} + i_L(t) = 0$$

$$C \frac{d^2V_C}{dt^2} + \frac{di_L}{dt} = 0 \Rightarrow \frac{d^2V_C}{dt^2} + \frac{1}{LC} V_C = 0$$

$$V_C(0^+) = V_0 \text{ olsun}$$

$$i_L(0^+) = I_0 \text{ olsun}$$

$$s^2 + \frac{1}{LC} = 0 \Rightarrow s = \pm j \frac{1}{\sqrt{LC}}$$

$$V_C(t) = \left( A \cos \frac{t}{\sqrt{LC}} + B \sin \frac{t}{\sqrt{LC}} \right) u(t)$$

$$i_L(t) = -i_C(t) = -C \frac{dV_C(t)}{dt} = \sqrt{\frac{C}{L}} \left( A \sin \frac{t}{\sqrt{LC}} - B \cos \frac{t}{\sqrt{LC}} \right) u(t)$$


$$V_C(0^+) = A = V_0$$

$$V_C(t) = \left( V_0 \cos \frac{t}{\sqrt{LC}} - \sqrt{\frac{L}{C}} I_0 \sin \frac{t}{\sqrt{LC}} \right) u(t)$$

$$i_L(0^+) = -B \sqrt{\frac{C}{L}} = I_0$$

$$i_L(t) = \left( I_0 \cos \frac{t}{\sqrt{LC}} + \sqrt{\frac{C}{L}} V_0 \sin \frac{t}{\sqrt{LC}} \right) u(t)$$

$$B = -I_0 \sqrt{\frac{L}{C}}$$

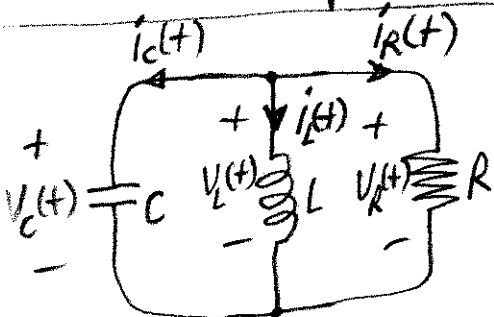

$$V_C(t) = V_L(t) = V_R(t)$$

$$i_C(t) + i_L(t) + i_R(t) = 0$$

$$C \frac{dV_C}{dt} + i_L + \frac{V_C}{R} = 0$$

$$C \frac{d^2V_C}{dt^2} + \frac{di_L}{dt} + \frac{1}{R} \frac{dV_C}{dt} = 0$$

$$LC \frac{d^2V_C}{dt^2} + L \frac{di_L}{dt} + \frac{L}{R} \frac{dV_C}{dt} = 0$$

$$\frac{d^2V_C}{dt^2} + \frac{1}{RC} \frac{dV_C}{dt} + \frac{1}{LC} V_C = 0$$

$$\alpha = \frac{1}{2RC} \text{ Sönümlenme frekansı}$$

$$\frac{d^2V_C}{dt^2} + 2\alpha \frac{dV_C}{dt} + \omega^2 V_C = 0$$

$$\omega = \frac{1}{\sqrt{LC}} \text{ Salınım frekansı}$$

$$s^2 + 2\alpha s + \omega^2 = 0$$

$$(s + \alpha)^2 + \omega^2 - \alpha^2 = 0$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega^2}$$

$$\omega_d = \sqrt{\omega^2 - \alpha^2}$$

$$\alpha > \omega \text{ ise}$$


$$V_C(t) = (A e^{s_1 t} + B e^{s_2 t}) u(t)$$

$$\alpha = \omega \text{ ise}$$

$$V_C(t) = (At + B) e^{-\alpha t} u(t)$$

$$\alpha < \omega \text{ ise}$$
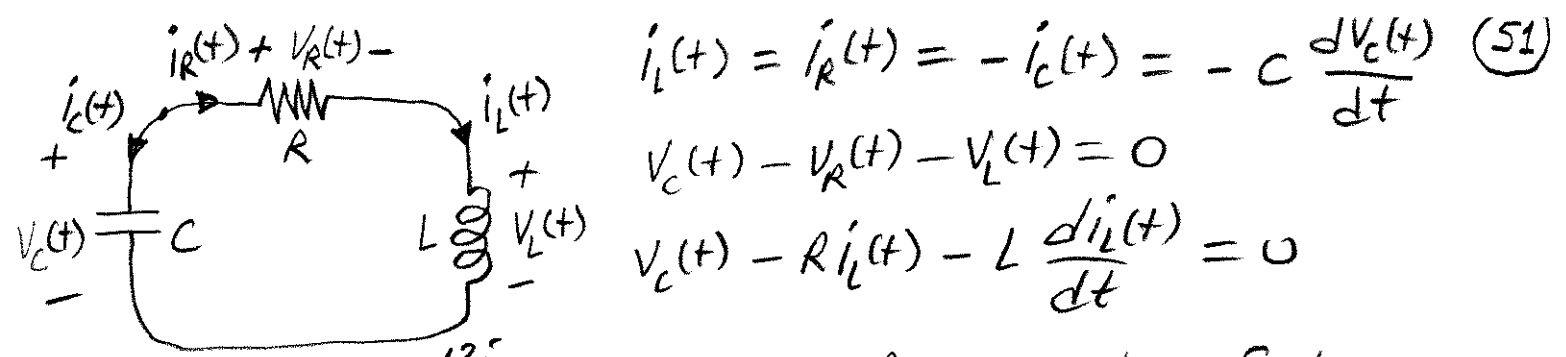
$$V_C(t) = (A \cos \omega_d t + B \sin \omega_d t) e^{-\alpha t} u(t)$$



$$\dot{i}_L(t) = \dot{i}_R(t) = -\dot{i}_C(t) = -C \frac{dV_C(t)}{dt} \quad (51)$$

$$V_C(t) - V_R(t) - V_L(t) = 0$$

$$V_C(t) - R\dot{i}_L(t) - L \frac{d\dot{i}_L(t)}{dt} = 0$$

$$\frac{dV_C}{dt} - R \frac{d\dot{i}_L}{dt} - L \frac{d^2\dot{i}_L}{dt^2} = 0$$

$$\alpha = \frac{R}{2L} \text{ Sönümlenme frekansı}$$

$$-C \frac{dV_C}{dt} + RC \frac{d\dot{i}_L}{dt} + LC \frac{d^2\dot{i}_L}{dt^2} = 0 \quad \omega = \frac{1}{\sqrt{LC}} \text{ Salınım frekansı}$$


$$\frac{d^2\dot{i}_L}{dt^2} + \frac{R}{L} \frac{d\dot{i}_L}{dt} + \frac{1}{LC} \dot{i}_L = 0 \Rightarrow \frac{d^2\dot{i}_L}{dt^2} + 2\alpha \frac{d\dot{i}_L}{dt} + \omega^2 \dot{i}_L = 0$$

$$s^2 + 2\alpha s + \omega^2 = 0 \Rightarrow s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega^2}, \quad \omega_d = \sqrt{\omega^2 - \alpha^2}$$

$$\alpha > \omega \text{ ise } \dot{i}_L(t) = (Ae^{s_1 t} + Be^{s_2 t}) u(t)$$

$$\alpha = \omega \text{ ise } \dot{i}_L(t) = (At + B) e^{-\alpha t} u(t)$$
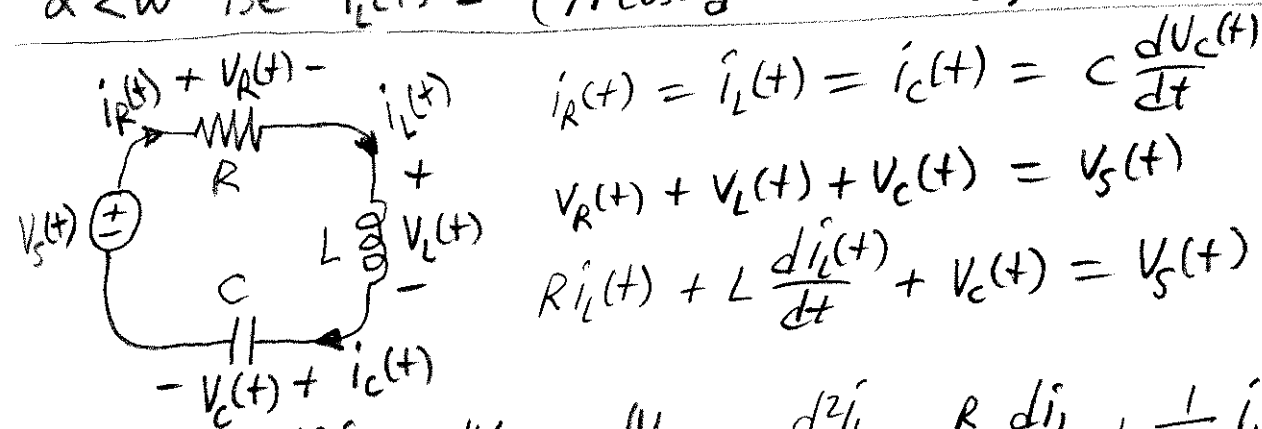
$$\alpha < \omega \text{ ise } \dot{i}_L(t) = (A \cos \omega_d t + B \sin \omega_d t) e^{-\alpha t} u(t)$$



$$\dot{i}_R(t) = \dot{i}_L(t) = \dot{i}_C(t) = C \frac{dV_C(t)}{dt}$$

$$V_R(t) + V_L(t) + V_C(t) = V_S(t)$$

$$R\dot{i}_L(t) + L \frac{d\dot{i}_L(t)}{dt} + V_C(t) = V_S(t)$$

$$R \frac{d\dot{i}_L}{dt} + L \frac{d^2\dot{i}_L}{dt^2} + \frac{dV_C}{dt} = \frac{dV_S}{dt} \Rightarrow \frac{d^2\dot{i}_L}{dt^2} + \frac{R}{L} \frac{d\dot{i}_L}{dt} + \frac{1}{LC} \dot{i}_L = \frac{1}{L} \frac{dV_S}{dt}$$

$$\alpha = \frac{R}{2L} \text{ Sönümlenme frekansı}$$

$$\frac{d^2\dot{i}_L}{dt^2} + 2\alpha \frac{d\dot{i}_L}{dt} + \omega^2 \dot{i}_L = \frac{1}{L} \frac{dV_S}{dt}$$

$$\omega = \frac{1}{\sqrt{LC}} \text{ Salınım frekansı}$$

2. mertebeden  
homojen olmayan  
lineer dif.  
denklemleri


$$\frac{dV_S}{dt} = 0 \quad \text{ için } \dot{i}_{L1} \text{ homojen çözüm}$$

$$\frac{dV_S}{dt} \neq 0 \quad \text{ için } \dot{i}_{L2} \text{ hom. olmayan çözüm}$$

$$\dot{i}_L(t) = \dot{i}_{L1}(t) + \dot{i}_{L2}(t)$$

$$x(t) \rightarrow \boxed{h(t)} \rightarrow y(t) = h(t) * x(t) = \int_{-\infty}^{\infty} h(\tau) x(t-\tau) d\tau \quad (52)$$
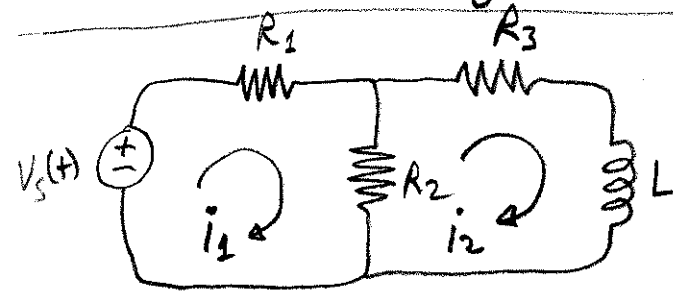
$$\left. \begin{array}{l} x(t) = \delta(t) \text{ ise } y(t) = h(t) \\ x(t) = u(t) \text{ ise } y(t) = s(t) \end{array} \right\} h(t) = \frac{ds(t)}{dt}, \quad s(t) = \int_{-\infty}^t h(\tau) d\tau$$



$$V_s(t) = 30u(t), \quad i_L(0^+) = 1A$$

$$R_1 = 3\Omega, R_2 = 6\Omega, R_3 = 3\Omega$$

$$L = 2H, \quad i_L(t) = ?, \quad V_L(t) = ?$$

$$-(R_1 + R_2)i_1 + R_2 i_2 = 0 \Rightarrow 10 - 3i_1 + 2i_2 = 0 \quad \text{1. denklemin}$$

$$R_2 i_1 - (R_2 + R_3)i_2 - L \frac{di_2}{dt} = 0 \Rightarrow 6i_1 - 9i_2 - 2 \frac{di_2}{dt} = 0 \quad \text{2. denklemin}$$

$$\text{1. denklemin 2 katıyla 2. denklemini toplarsak: } \frac{di_2}{dt} + 2.5i_2 = 10$$

$$i_2 = i_L \text{ olduğundan } \frac{di_L}{dt} + 2.5i_L = 10$$

$$\frac{di_L}{dt}(\infty) = 0 \text{ olduğundan } i_L(\infty) = 4A$$

$$i_L(t) = (A e^{-2.5t} + B)u(t) \quad i_L(t) = (4 - 3e^{-2.5t})u(t)$$


$$i_L(0^+) = A + B = 1 \quad \left. \begin{array}{l} A = 1 - B \\ B = -3 \end{array} \right\}$$

$$i_L(\infty) = B = 4$$

$$V_L(t) = L \frac{di_L}{dt} = 15e^{-2.5t}u(t)$$

$$R_L = (R_1 \parallel R_2) + R_3 = 3\Omega \parallel 6\Omega + 3\Omega = 5\Omega$$
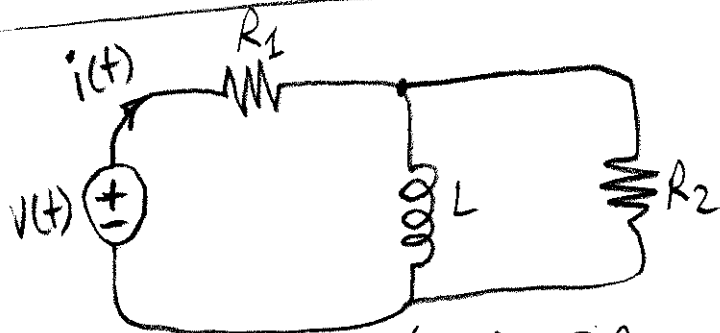
$$\tau = \frac{L}{R_L} = 0.4s \text{ Zaman Sabitesi} \quad 52 = 2s \text{ Durulma zamanı}$$



$$V(t) = 18\delta(t) \quad i_L(0^-) = 3A$$

$$R_1 = 3\Omega \quad R_2 = 6\Omega \quad L = 4H$$


$$i_L(t) = ?$$

$$t=0 \text{ için } V_L(t) = \frac{R_2 V(t)}{R_1 + R_2} = 12\delta(t)$$

$$i_L(0^+) = i_L(0^-) + \frac{1}{L} \int_{0^-}^{0^+} V_L(\tau) d\tau$$

$$= 3A + \frac{1}{4} \int_{0^-}^{0^+} 12\delta(\tau) d\tau$$
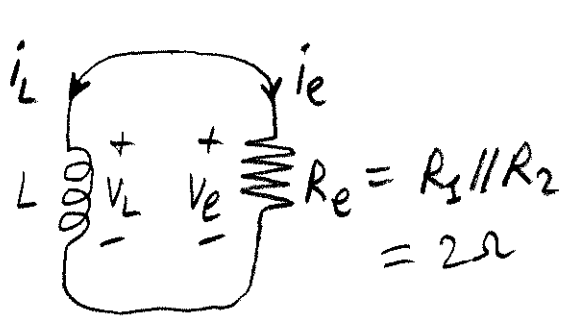
$$= 3A + 3 \int_{0^-}^{0^+} \delta(\tau) d\tau = 6A$$



$$\dot{i}_L(t) + \frac{V_L(t)}{R_e} = 0$$

$$\dot{i}_L(t) + \frac{L}{R_e} \frac{d\dot{i}_L(t)}{dt} = 0$$


$$\frac{d\dot{i}_L}{dt} + \frac{R_e}{L} \dot{i}_L = 0 \Rightarrow \frac{d\dot{i}_L}{dt} + 0.5 \dot{i}_L = 0 \Rightarrow \dot{i}_L(t) = 6 e^{-0.5t} u(t)$$

$$V_L(t) = L \frac{d\dot{i}_L}{dt} = -12 e^{-0.5t} u(t)$$

$$i(t) = \dot{i}_L(t) + \dot{i}_{R2}(t)$$

$$\dot{i}_{R2}(t) = \frac{V_L(t)}{R_2} = -2 e^{-0.5t} u(t)$$

$$= 4 e^{-0.5t} u(t)$$

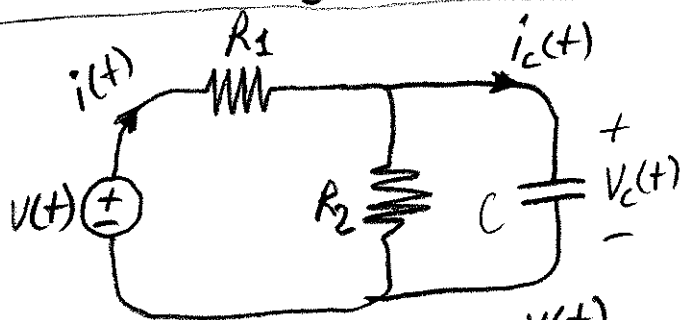


$$V(t) = 12\delta(t), \quad V_c(0^-) = 4V$$

$$R_1 = 3\Omega, \quad R_2 = 6\Omega, \quad C = 2F$$

$$i(t) = ? \quad z = ? \quad \text{Dur. Zam.} = ?$$

$$t=0 \text{ isin } \dot{i}_c(t) = \frac{V(t)}{R_1} = 4\delta(t) + \frac{4}{6}$$
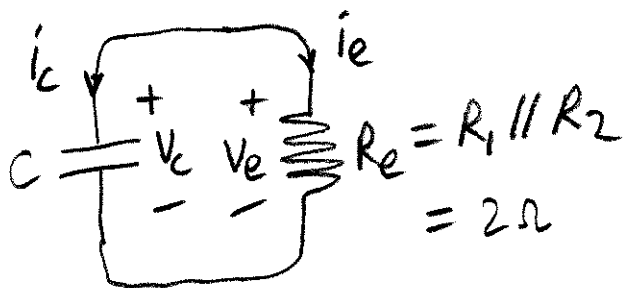
$$V_c(0^+) = V_c(0^-) + \frac{1}{C} \int_{0^-}^{0^+} \dot{i}_c(z) dz = 4V + \frac{1}{2} \int_{0^-}^{0^+} 4\delta(z) dz = 6V$$



$$C \frac{dV_c}{dt} + \frac{V_c}{R_e} = 0$$

$$\frac{dV_c}{dt} + \frac{1}{R_e C} V_c = 0$$

$$\frac{dV_c}{dt} + 0.25 V_c = 0 \Rightarrow V_c(t) = 6 e^{-0.25t} u(t)$$

$$\dot{i}_c(t) = C \frac{dV_c}{dt} = -3 e^{-0.25t} u(t)$$


$$i(t) = \dot{i}_c(t) + \dot{i}_R(t)$$

$$\dot{i}_{R2}(t) = \frac{V_c(t)}{R_2} = e^{-0.25t} u(t)$$

$$= -2 e^{-0.25t} u(t)$$

$$\tau = R_e C = 2\Omega \times 2F = 4s$$

$$\text{Durulma Zamanı} = 5\tau = 20s$$

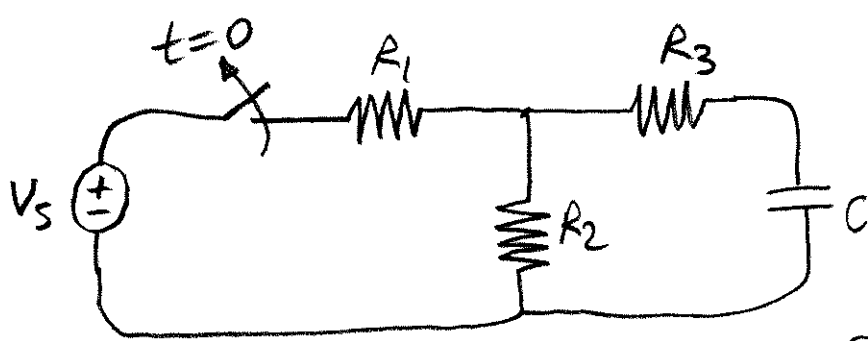


54  
 $V_s = 25V$ ,  $R_1 = 60\Omega$   
 $R_2 = 40\Omega$ ,  $R_3 = 10\Omega$   
 $C = 0.1F$

$V_c(0^+) = ?$ ,  $W_c(0^+) = ?$ ,  $V_c(t) = ?$ ,  $i_c(t) = ?$   
 $z = ?$  Durulma zamanı = ?

$$V_c(0^+) = V_c(0^-) = \frac{R_2 V_s}{R_1 + R_2} = \frac{40\Omega \times 25V}{100\Omega} = 10V$$
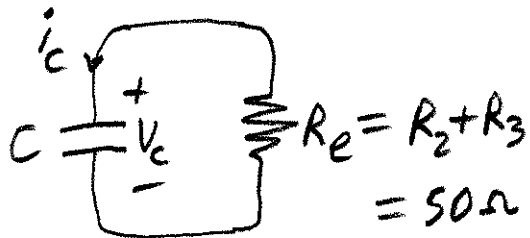
$$W_c(0^+) = \frac{1}{2} C V_c^2(0^+) = \frac{1}{2} \times 0.1F \times (10V)^2 = 5J$$




$$z = R_e C = 50\Omega \times 0.1F = 5s$$

Durulma zamanı =  $5z = 25s$

$$V_c(t) = V_c(0^+) e^{-t/z} u(t) = 10e^{-0.2t} u(t)$$
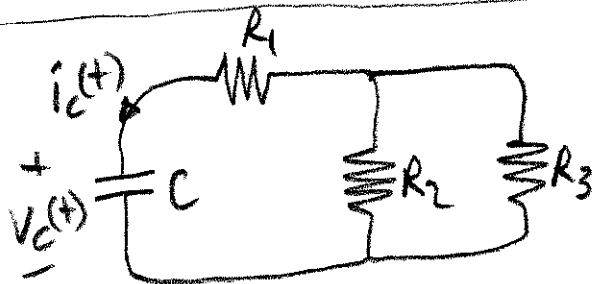
$$i_c(t) = C \frac{dV_c(t)}{dt} = -0.2 e^{-0.2t} u(t)$$



$V_c(0^+) = 30V$ ,  $R_1 = 30\Omega$ ,  $R_2 = 60\Omega$

$C = 40mF$ ,  $R_3 = 30\Omega$

$V_c(t) = ?$ ,  $i_c(t) = ?$  Dur. Zamm. = ?


$$R_e = R_1 + R_2 \parallel R_3 = 30\Omega + 60\Omega \parallel 30\Omega = 50\Omega$$

$$z = R_e C = 50\Omega \times 40mF = 2s$$


Durulma zamanı =  $5z = 10s$

$$V_c(t) = V_c(0^+) e^{-t/z} u(t) = 30e^{-0.5t} u(t)$$

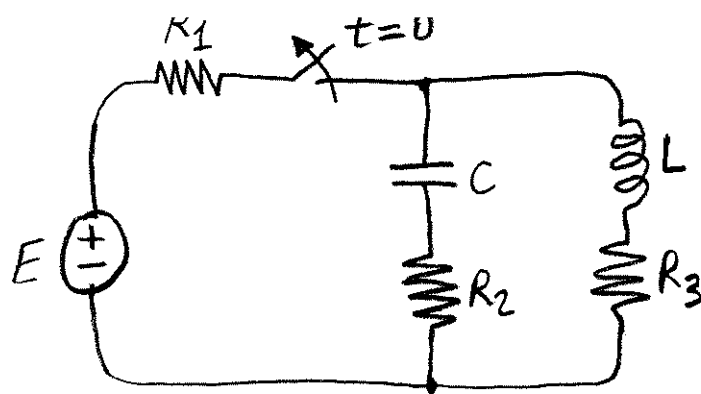
$$i_c(t) = C \frac{dV_c(t)}{dt} = -0.6 e^{-0.5t} u(t)$$



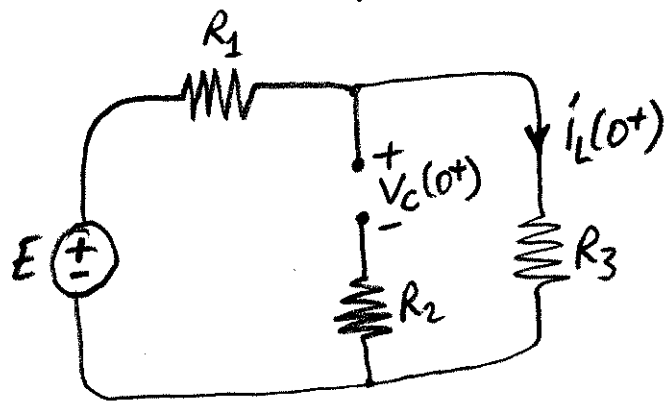$E = 12V, C = 8mF, L = 5H$   
 $R_1 = 15\Omega, R_2 = 21\Omega, R_3 = 9\Omega$   
 $\alpha = ? \quad \omega = ?$   
 $i_L(t) = ? \quad V_C(t) = ?$



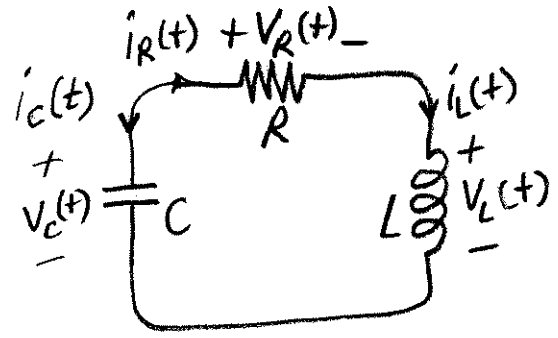$i_L(0^+) = \frac{E}{R_1 + R_3} = \frac{12V}{24\Omega} = 0.5A$   
 $V_C(0^+) = R_3 i_L(0^+) = 9\Omega \times 0.5A = 4.5V$



$R = R_2 + R_3 = 21\Omega + 9\Omega = 30\Omega$   
 $\alpha = \frac{R}{2L} = \frac{30\Omega}{2 \times 5H} = 3$   
 $\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{5H \times 8mF}} = \frac{1}{\sqrt{0.04}} = 5$

$\omega > \alpha$  olduğundan

$\omega_d = \sqrt{\omega^2 - \alpha^2} = \sqrt{25 - 9} = \sqrt{16} = 4$

$i_L(t) = (A \cos 4t + B \sin 4t) e^{-3t} u(t)$

$\frac{di_L}{dt} = ((4B - 3A) \cos 4t - (4A + 3B) \sin 4t) e^{-3t} u(t)$


$V_C(t) = V_R(t) + V_L(t) = R i_L(t) + L \frac{di_L}{dt} = 30 i_L(t) + 5 \frac{di_L}{dt}$

$= ((15A + 20B) \cos 4t + (15B - 20A) \sin 4t) \cdot e^{-3t} \cdot u(t)$

$\left. \begin{aligned} i_L(0^+) &= A = 0.5 \\ V_C(0^+) &= 15A + 20B = 4.5 \end{aligned} \right\} B = \frac{4.5 - 15A}{20} = -0.15$

$i_L(t) = (0.5 \cos 4t - 0.15 \sin 4t) e^{-3t} u(t)$

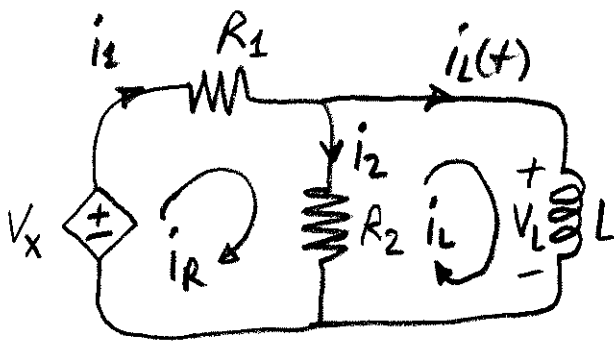$V_C(t) = (4.5 \cos 4t - 12.25 \sin 4t) e^{-3t} u(t)$



$$R_1 = 3\Omega, R_2 = 2\Omega$$

$$L = 8H, V_x(t) = 15 - 7\dot{i}_L(t)$$

$$i_L(0^+) = 5A \quad \dot{i}_L(t) = ?$$

$$V_L(t) = ? \quad \dot{i}_1(t) = ? \quad \dot{i}_2(t) = ?$$

$$V_x - (R_1 + R_2)\dot{i}_R + R_2\dot{i}_L = 0$$

$$15 - 7\dot{i}_L - 5\dot{i}_R + 2\dot{i}_L = 0$$

$$\dot{i}_R = 3 - \dot{i}_L$$

$$R_2(\dot{i}_R - \dot{i}_L) - L\frac{d\dot{i}_L}{dt} = 0$$

$$2(3 - \dot{i}_L - \dot{i}_L) - 8\frac{d\dot{i}_L}{dt} = 0$$

$$t = \infty \text{ için } \frac{d\dot{i}_L}{dt} = 0 \text{ olur.}$$

$$\dot{i}_L(\infty) = \frac{0.75}{0.5} A = 1.5 A$$

$$\frac{d\dot{i}_L}{dt} + 0.5\dot{i}_L = 0.75$$

$$\dot{i}_L(t) = (Ae^{-0.5t} + B)u(t)$$

$$\dot{i}_L(t) = (3.5e^{-0.5t} + 1.5)u(t)$$


$$\left. \begin{aligned} \dot{i}_L(0^+) = A + B = 5 \\ \dot{i}_L(\infty) = B = 1.5 \end{aligned} \right\} A = 3.5$$

$$V_L(t) = L\frac{d\dot{i}_L}{dt} = -14e^{-0.5t}u(t)$$

$$\dot{i}_1(t) = \dot{i}_R(t) = 3 - \dot{i}_L = (1.5 - 3.5e^{-0.5t})u(t)$$

$$\dot{i}_2(t) = \dot{i}_R(t) - \dot{i}_L(t) = 3 - 2\dot{i}_L = -7e^{-0.5t}u(t)$$

Node Analizle yapılırsa idi

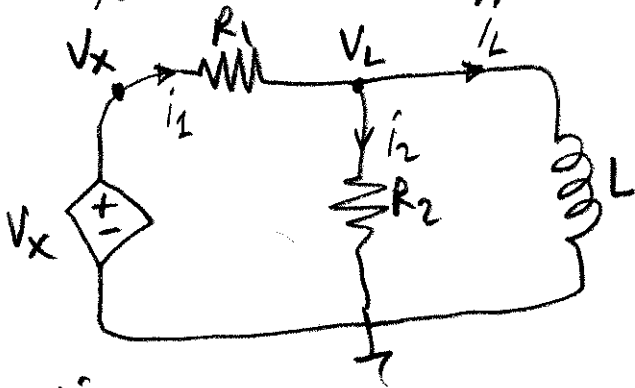

$$\frac{V_L - V_x}{R_1} + \frac{V_L}{R_2} + \dot{i}_L = 0$$

$$(R_1 + R_2)V_L - R_2V_x + R_1R_2\dot{i}_L = 0$$

$$(R_1 + R_2)L\frac{d\dot{i}_L}{dt} - R_2(15 - 7\dot{i}_L) + R_1R_2\dot{i}_L = 0$$


Diğer kısımlar yukarıdaki gibi yapılır.

$$\frac{d\dot{i}_L}{dt} + 0.5\dot{i}_L = 0.75$$

$$t = \infty \text{ için } \frac{d\dot{i}_L}{dt} = 0 \text{ olur.}$$

$$\dot{i}_L(\infty) = 1.5A$$



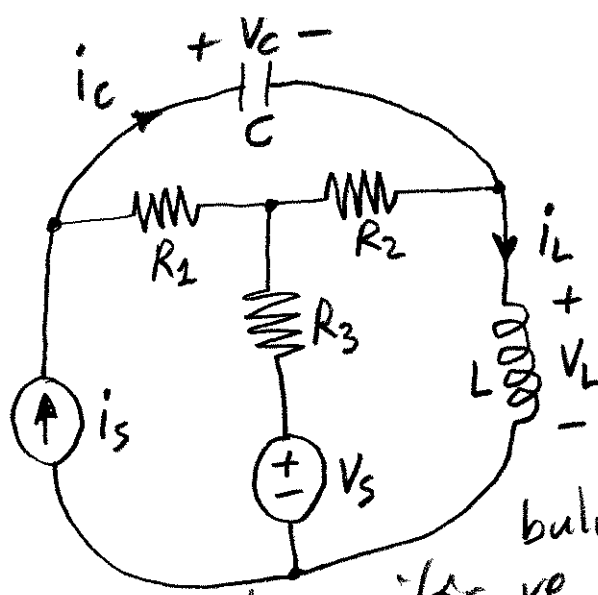


$$V_s = 13V, \quad \hat{i}_s = 2A$$

$$C = 16mF, \quad L = 4H$$

$$R_1 = 8\Omega, \quad R_2 = 3\Omega, \quad R_3 = 4\Omega$$

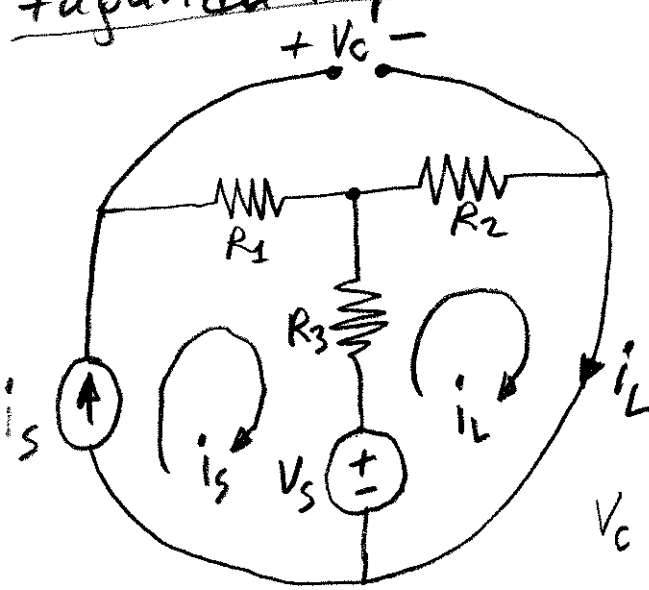DC şartlar oluştığında üretilen ve tüketilen güçleri bulunuz. Ayrıca, dc şartlar oluştuğunda kapasitör ve bobinde depolanan enerjiyi bulunuz.



$$V_s - (R_2 + R_3)\hat{i}_L + R_3\hat{i}_s = 0$$

$$\hat{i}_L = \frac{V_s + R_3\hat{i}_s}{R_2 + R_3} = \frac{13V + 4\Omega \times 2A}{3\Omega + 4\Omega}$$

$$= \frac{21V}{7\Omega} = 3A$$

$$V_C = R_1\hat{i}_s + R_2\hat{i}_L = 8\Omega \times 2A + 3\Omega \times 3A = 16V + 9V = 25V$$

$$P_i = V_C\hat{i}_s = 25V \times 2A = 50W$$

$$P_V = V_s(\hat{i}_L - \hat{i}_s) = 13V \times (3A - 2A) = 13W$$

$$\left. \begin{array}{l} P_{\text{ort}} = P_i + P_V \\ = 50W + 13W = 63W \end{array} \right\}$$

$$P_1 = R_1\hat{i}_s^2 = 8\Omega \times (2A)^2 = 32W$$


$$P_2 = R_2\hat{i}_L^2 = 3\Omega \times (3A)^2 = 27W$$

$$P_3 = R_3(\hat{i}_L - \hat{i}_s)^2 = 4\Omega \times (3A - 2A)^2 = 4W$$

$$\left. \begin{array}{l} P_{\text{tük}} = P_1 + P_2 + P_3 \\ = 32W + 27W + 4W \\ = 63W \end{array} \right\}$$

$$W_C = \frac{1}{2} C V_C^2 = \frac{1}{2} \times 16mF \times (25V)^2 = 5J$$
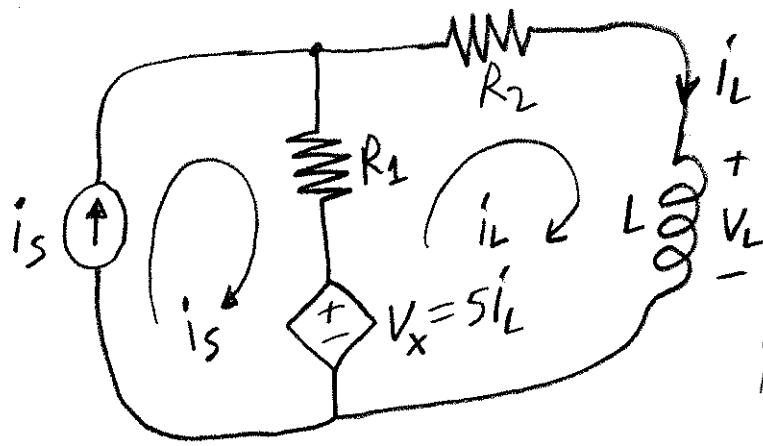
$$W_L = \frac{1}{2} L \hat{i}_L^2 = \frac{1}{2} \times 4H \times (3A)^2 = 18J$$



$$R_1 = 3\Omega, R_2 = 5\Omega$$

$$L = 6H, i_s = 5A$$

$$i_L(0^+) = 2A$$

$$i_L(t) = ? \quad V_L(t) = ?$$

$$V_x - (R_1 + R_2)i_L + R_1 i_s - L \frac{di_L}{dt} = 0$$

$$5i_L - 8i_L + 15 - 6 \frac{di_L}{dt} = 0$$

$$15 - 3i_L - 6 \frac{di_L}{dt} = 0 \Rightarrow \frac{di_L}{dt} + 0.5i_L = 2.5$$

$$t = \infty \text{ için } \frac{di_L}{dt} = 0 \text{ olduğundan}$$

$$\frac{di_L}{dt}(\infty) + 0.5i_L(\infty) = 2.5 \Rightarrow i_L(\infty) = 5A$$

$$i_L(t) = (Ae^{-0.5t} + B)u(t)$$


$$\left. \begin{aligned} i_L(0^+) = A + B = 2 \\ i_L(\infty) = B = 5 \end{aligned} \right\} A = 2 - B = -3$$

$$i_L(t) = (5 - 3e^{-0.5t})u(t)$$

$$V_L(t) = L \frac{di_L(t)}{dt} = 9e^{-0.5t}u(t)$$


## Türev Alıcı Devre

(59)

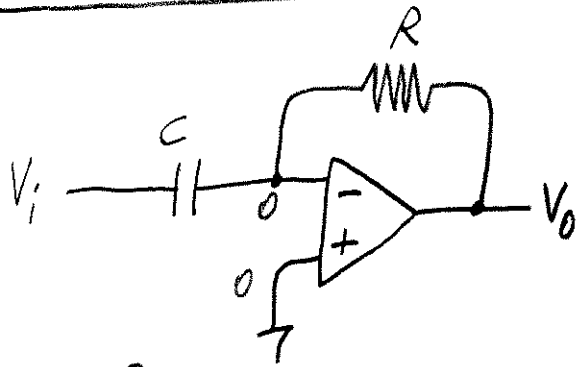

$$C \frac{dV_i}{dt} + \frac{V_o}{R} = 0$$


$$V_o(t) = -RC \frac{dV_i(t)}{dt}$$

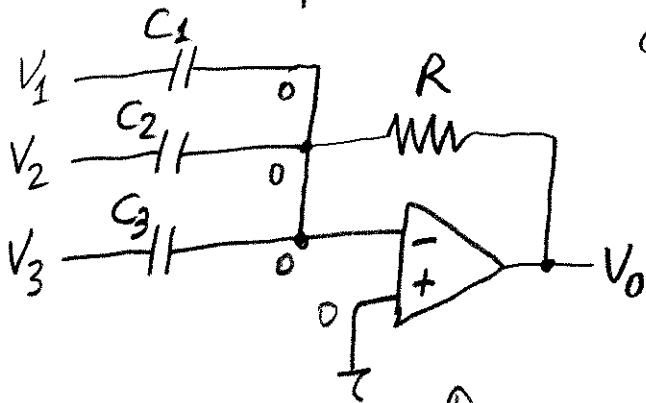

$$C_1 \frac{dV_1}{dt} + C_2 \frac{dV_2}{dt} + C_3 \frac{dV_3}{dt} + \frac{V_o}{R} = 0$$

$$V_o(t) = -RC_1 \frac{dV_1}{dt} - RC_2 \frac{dV_2}{dt} - RC_3 \frac{dV_3}{dt}$$


## Integral Alıcı Devre

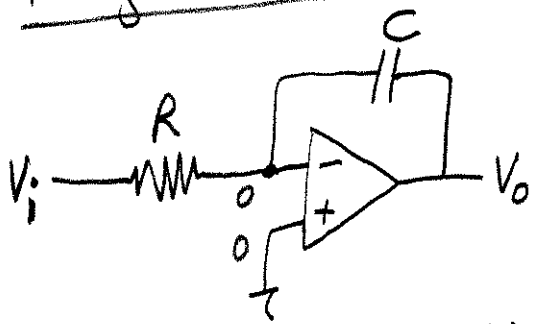

$$\frac{V_i}{R} + C \frac{dV_o}{dt} = 0$$

$$\frac{dV_o}{dt} = -\frac{1}{RC} V_i$$

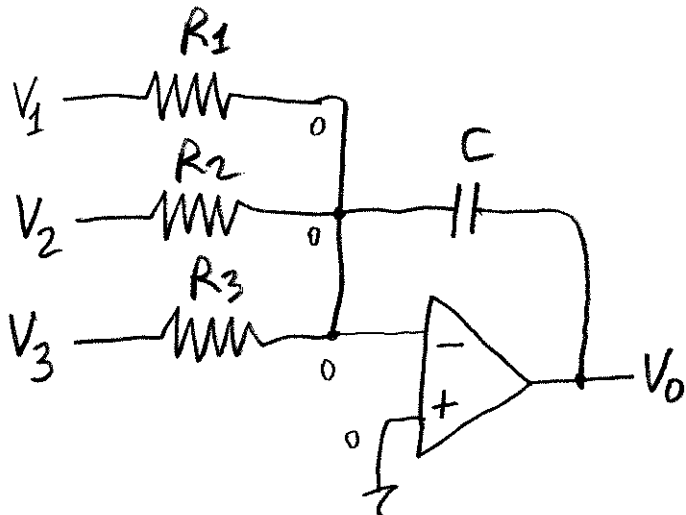
$$V_o(t) = V_o(0) - \frac{1}{RC} \int_0^t V_i(\tau) d\tau$$



$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + C \frac{dV_o}{dt} = 0$$

$$\frac{dV_o}{dt} = -\frac{V_1}{R_1 C} - \frac{V_2}{R_2 C} - \frac{V_3}{R_3 C}$$
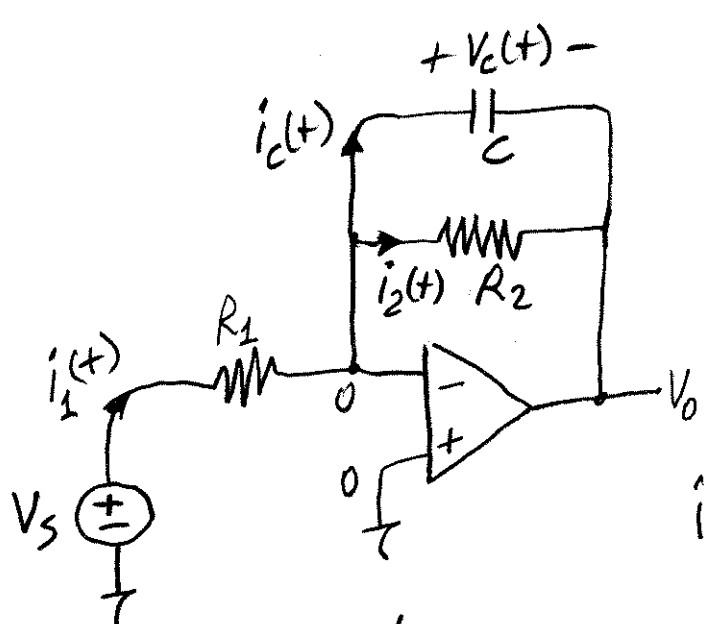
$$V_o(t) = V_o(0) - \frac{1}{R_1 C} \int_0^t V_1(\tau) d\tau - \frac{1}{R_2 C} \int_0^t V_2(\tau) d\tau - \frac{1}{R_3 C} \int_0^t V_3(\tau) d\tau$$



$V_s = 15V$ ,  $R_1 = 12K$ ,  $R_2 = 8K$  (60)  
 $C = 25\mu F$ ,  $V_c(0^+) = 4V$

$\tau = ?$  Dur. Zam. = ?

$V_o(t) = ?$   $i_c(t) = ?$

$i_1(t) = ?$   $i_2(t) = ?$

$$\frac{V_s}{R_1} + \frac{V_o}{R_2} + C \frac{dV_o}{dt} = 0$$

$$\frac{dV_o}{dt} + \frac{1}{R_2 C} V_o = -\frac{V_s}{R_1 C}$$

$$\frac{dV_o}{dt} + 5V_o = -50$$

$$V_o(t) = (A e^{-5t} + B) u(t)$$


$$\left. \begin{aligned} V_o(0^+) &= A + B = -4 \\ V_o(\infty) &= B = -10 \end{aligned} \right\} A = -4 - B = 6$$

$$V_o(t) = (6e^{-5t} - 10) u(t)$$


$$i_c(t) = C \frac{dV_c}{dt} = -C \frac{dV_o}{dt} = 0.75 \times 10^{-3} e^{-5t} u(t)$$

$$i_2(t) = -\frac{V_o(t)}{R_2} = (1.25 - 0.75e^{-5t}) \times 10^{-3} u(t)$$
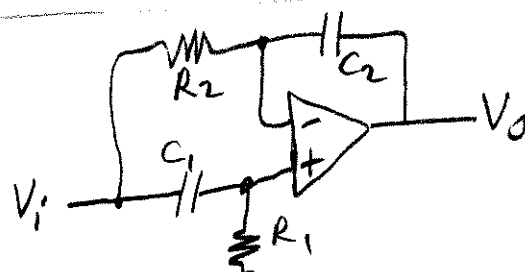
$$i_1(t) = i_c(t) + i_2(t) = 1.25 \times 10^{-3} u(t)$$



(61)

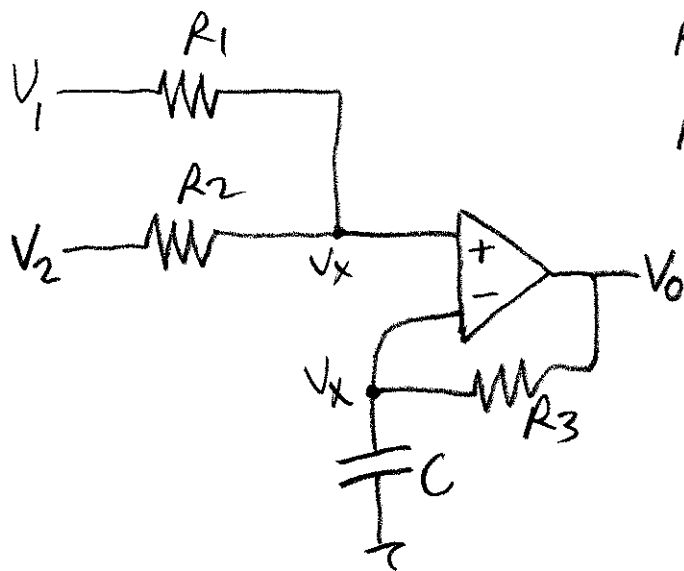

$$R_1 = 2k\Omega \quad R_2 = 3k\Omega$$

$$R_3 = 5k\Omega \quad C = 6\mu F$$

$$V_1(t) = 9 \cos 40t$$

$$V_2(t) = 7 \sin 40t$$

$$V_0(t) = ?$$

$$\frac{V_1 - V_x}{R_1} + \frac{V_2 - V_x}{R_2} = 0$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} = \frac{V_x}{R_1} + \frac{V_x}{R_2}$$

$$V_x = \frac{R_2}{R_1 + R_2} V_1 + \frac{R_1}{R_1 + R_2} V_2$$

$$V_x = 0.6V_1 + 0.4V_2$$

$$V_x = 5.4 \cos 40t + 2.8 \sin 40t$$

$$\frac{dV_x}{dt} = 112 \cos 40t - 216 \sin 40t$$

$$V_0(t) = (5.4 \cos 40t + 2.8 \sin 40t) + 0.03 (112 \cos 40t - 216 \sin 40t)$$


$$= 8.76 \cos 40t - 3.68 \sin 40t$$

$$C \frac{dV_x}{dt} + \frac{V_x - V_0}{R_3} = 0$$

$$V_0 = V_x + R_3 C \frac{dV_x}{dt}$$

$$= V_x + 0.03 \frac{dV_x}{dt}$$

(62)

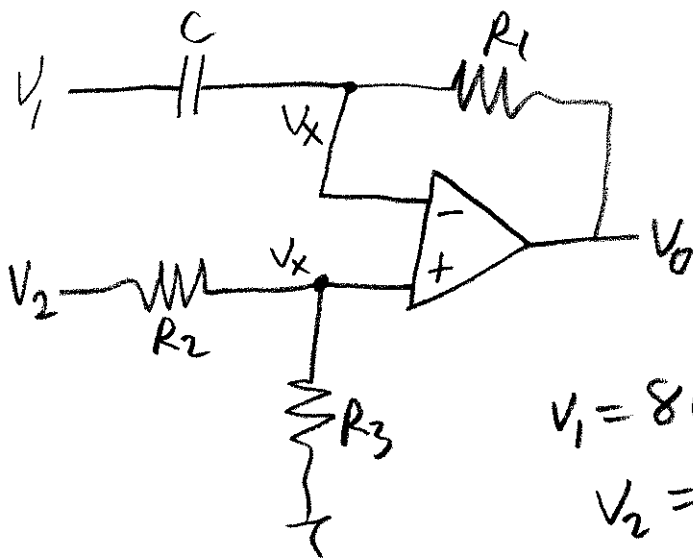

$$\begin{aligned}
 R_1 &= 5k\Omega \\
 R_2 &= 4k\Omega \\
 R_3 &= 6k\Omega \\
 C &= 10\mu F
 \end{aligned}$$

$$\begin{aligned}
 V_1 &= 8\cos 15t \\
 V_2 &= 6\sin 15t \quad V_0(t) = ?
 \end{aligned}$$

$$\frac{V_x - V_2}{R_2} + \frac{V_x}{R_3} = 0$$

$$\frac{V_x}{R_2} + \frac{V_x}{R_3} = \frac{V_2}{R_2}$$

$$V_x = \frac{R_3}{R_2 + R_3} V_2$$

$$= 0.6 V_2$$

$$C \frac{d}{dt}(V_x - V_1) + \frac{V_x - V_0}{R_1} = 0$$

$$V_0 = V_x + R_1 C \frac{dV_x}{dt} - R_1 C \frac{dV_1}{dt}$$

$$= V_x + 0.05 \frac{dV_x}{dt} - 0.05 \frac{dV_1}{dt}$$

$$= 0.6 V_2 + 0.03 \frac{dV_2}{dt} - 0.05 \frac{dV_1}{dt}$$

$$V_0(t) = 0.6 (6\sin 15t) + 0.03 (6 \times 15 \cos 15t) - 0.05 (-8 \times 15 \sin 15t)$$

$$= 3.6 \sin 15t + 2.7 \cos 15t + 6 \sin 15t$$

$$= 2.7 \cos 15t + 9.6 \sin 15t$$

## I. CIRCUIT BASICS

- Electrical quantities

- Current:**  $I = \frac{dq}{dt}$  [Units: C/s = Amps (A)]


- Voltage:**  $V = \frac{dw}{dq}$  [Units: J/C = Volts (V)]

- Power:**  $P = \frac{dw}{dt} = \frac{dw}{dq} \frac{dq}{dt} = VI$   
[Units: J/s = Watts (W)]

$P = IV > 0$ : power delivered


$P = IV < 0$ : power extracted

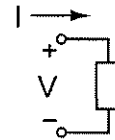avg power:  $\langle P \rangle = \frac{1}{T} \int_0^T I(t)V(t)dt$





- Primitive circuit elements

- Voltage Source**

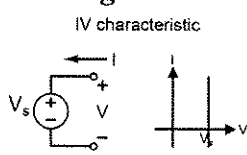


independent

dependent

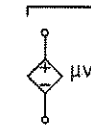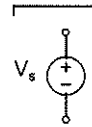



voltage-controlled  
current-controlled

- Current Source**

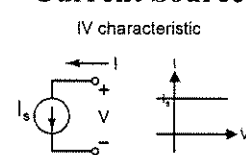

independent

dependent

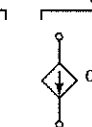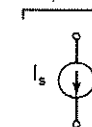


voltage-controlled  
current-controlled

- Resistor** – follows **Ohm's Law**:  $V = IR$  (note polarity)


$R$  = resistance [Units: V/A = Ohms ( $\Omega$ )]

$G = 1/R$  = conductance [Units: Siemens (S)]

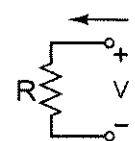Resistor power dissipation:  $P = IV = I^2 R = \frac{V^2}{R}$



IV characteristic

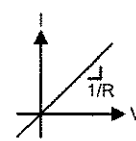

- Circuit definitions

- Node** – point where 2 or more circuit elements are connected

- Series elements** – same current flows through all elements

- Parallel elements** – same voltage across all elements

## II. CIRCUIT ANALYSIS BASICS

- KCL** (Kirchhoff's Current Law)

- Sum of all currents entering a node = 0

- Sum of all currents leaving a node = 0

- $\Sigma(\text{currents in}) = \Sigma(\text{currents out})$


- KVL** (Kirchhoff's Voltage Law)

- Sum of voltage drops around a loop = 0

- Sum of voltage rises around a loop = 0


- $\Sigma(\text{voltage drops}) = \Sigma(\text{voltage rises})$

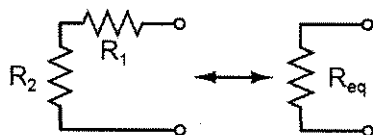- Series resistors:  $R_{eq} = \sum_{k=1}^n R_k$




$$R_{eq} = R_1 + R_2$$

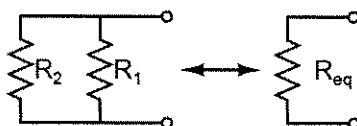- Parallel resistors:  $\frac{1}{R_{eq}} = \sum_{k=1}^n \frac{1}{R_k}$


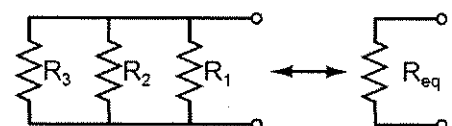
$$R_{eq} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$




$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

- Voltage divider




$$V_2 = \frac{R_2}{R_1 + R_2} V_s$$

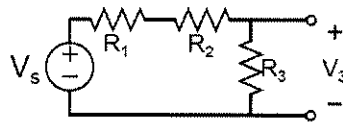


$$V_3 = \frac{R_3}{R_1 + R_2 + R_3} V_s$$

- Current divider


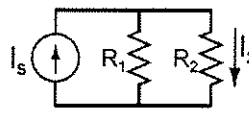


$$I_2 = \frac{R_1}{R_1 + R_2} I_s$$

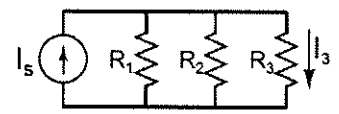


$$I_3 = \frac{1/R_3}{1/R_1 + 1/R_2 + 1/R_3} I_s$$

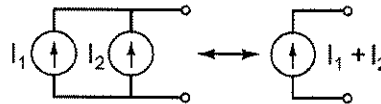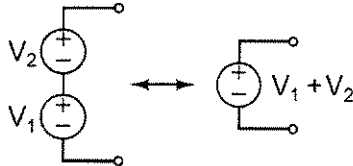- Source combinations (series voltage sources and parallel current sources)


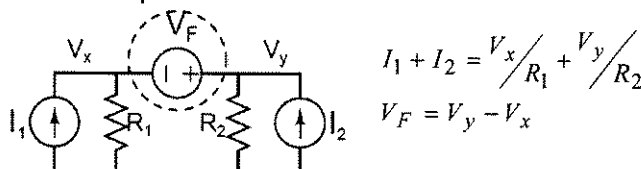
### III. CIRCUIT ANALYSIS METHODS

- **Nodal Analysis** – finds unknown node voltages in a circuit; once all node voltages are known, currents can be found through IV relationships of circuit elements (e.g., Ohm's Law)
  1. Choose a reference node ("ground")
  2. Define unknown voltages (those not fixed by voltage sources)
  3. Write KCL at each unknown node, expressing current in terms of node voltages
    - use IV relationships of the circuit elements (e.g.,  $I = V/R$  for resistors)
  4. Solve the set of independent equations (N eqn's for N unknown node voltages)
- **Supernode** – for a floating voltage source (where both terminals are unknown voltages), define a supernode around the source, write KCL at supernode, and use the voltage source equation



$$I_1 + I_2 = \frac{V_x}{R_1} + \frac{V_y}{R_2}$$


$$V_F = V_y - V_x$$


- **Superposition** – In any linear circuit containing multiple independent sources, any I or V in the circuit can be calculated as the sum of the individual contributions of each source acting alone
  - **Linear circuit** – circuit with only independent sources and linear elements (linear RLC, linear dependent sources). Linear elements have linear IV characteristics.
  1. Leave one source on and turn off all other sources
    - replace voltage source with short circuit ( $V=0$ )
    - replace current source with open circuit ( $I=0$ )
  2. Find the contribution from the "on" source
  3. Repeat for each independent source.
  4. Sum the individual contributions from each source to obtain the final result


Note: Superposition doesn't work for power, since power is nonlinear ( $P = I^2 R = V^2 / R$ )



#### IV. CAPACITORS AND INDUCTORS

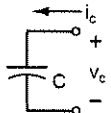- **Capacitor** – passive circuit element that stores electric energy
  - Capacitance:  $C = Q/V$  [Units: Coulombs/Volt = Farads (F)]
  - IV relationship:  $i_C = C \frac{dv_C}{dt}$   *note polarity!*
  - Energy stored:  $E_C = \frac{1}{2}CV^2$
  - voltage across capacitor  $v_C$  cannot change instantaneously:  $v_C(0^-) = v_C(0^+)$
  - in steady-state, capacitor is an open circuit ( $dv_C/dt = 0 \rightarrow i_C = 0$ )
  - low freq: open circuit; high freq: short-circuit
- Parallel capacitors:  $C_{eq} = \sum_{k=1}^n C_k$       • Series capacitors:  $\frac{1}{C_{eq}} = \sum_{k=1}^n \frac{1}{C_k}$
- Capacitive voltage divider

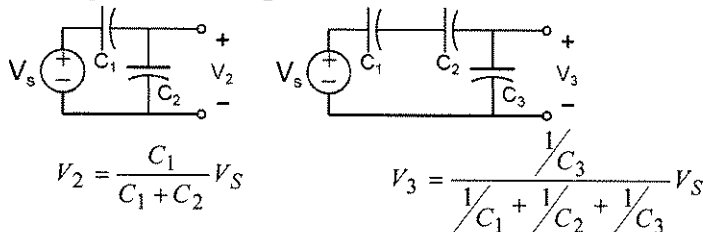


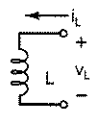- **Inductor** – passive circuit element that stores magnetic energy
  - Inductance:  $L = \Phi/I$  [Units: Webers/Amps = Henrys (H)]
  - IV relationship:  $v_L = L \frac{di_L}{dt}$   *note polarity!*
  - Energy stored:  $E_L = \frac{1}{2}LI^2$
  - current through inductor  $i_L$  cannot change instantaneously:  $i_L(0^-) = i_L(0^+)$
  - in steady-state, inductor is a short circuit ( $di_L/dt = 0 \rightarrow v_L = 0$ )
  - low freq: short circuit; high freq: open-circuit
- Series inductors:  $L_{eq} = \sum_{k=1}^n L_k$       • Parallel inductors:  $\frac{1}{L_{eq}} = \sum_{k=1}^n \frac{1}{L_k}$


Capacitor and Inductor Summary :

	Capacitor	Inductor
IV relationship	$i = C \frac{dv}{dt}$	$v = L \frac{di}{dt}$
Energy storage	$E_C = \frac{1}{2}CV^2$	$E_L = \frac{1}{2}LI^2$
Continuity	Voltage: $v_C(0^-) = v_C(0^+)$	Current: $i_L(0^-) = i_L(0^+)$
Steady-state	Open circuit ( $I=0$ )	Short circuit ( $V=0$ )
Series	$\frac{1}{C_{eq}} = \sum_{k=1}^n \frac{1}{C_k}$	$L_{eq} = \sum_{k=1}^n L_k$
Parallel	$C_{eq} = \sum_{k=1}^n C_k$	$\frac{1}{L_{eq}} = \sum_{k=1}^n \frac{1}{L_k}$

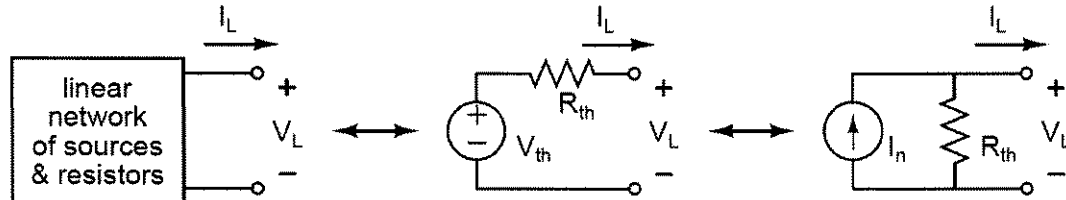- **Thevenin/Norton Equivalent Circuit Models** – Any linear 2-terminal network of independent sources and linear resistors can be replaced by an equivalent circuit consisting of 1 independent voltage source in series with 1 resistor (Thevenin) or 1 independent current source in parallel with 1 resistor (Norton). The circuit models have the same IV characteristics.




- Three variables:  $V_{th}=V_{oc}$ ,  $R_{th}=R_N$ ,  $I_N=I_{sc}$ .
- Thevenin/Norton relationship:  $V_{th}=I_N R_{th} \rightarrow$  only 2 of the 3 variables are required
- $V_{th} = V_{oc}$ : open-circuit voltage – Leave the port open ( $I_L=0$ ) and solve for  $V_{oc}$ .
- $I_N = I_{sc}$ : short-circuit current – Short the port ( $V_L=0$ ) and solve for  $I_N$ .
- $R_{th}$ : Thevenin/Norton resistance – Turn off all independent sources (leave the dependent sources alone). If there are no dependent sources, simplify the resistive network using series and parallel reductions to find the equivalent resistance. If dependent sources are present, attach  $I_{test}$  or  $V_{test}$  and use KCL/KVL to find  $R_{th}=V_{test}/I_{test}$ .

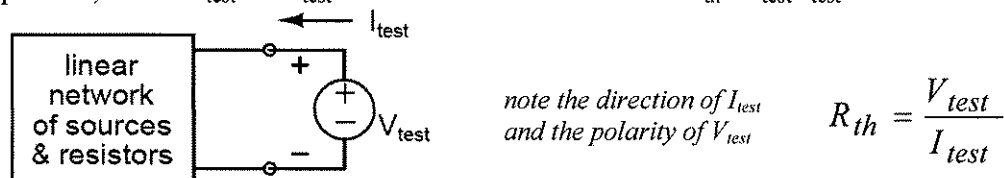


- **Source Transformations** – conversion between Thevenin and Norton equivalent circuits

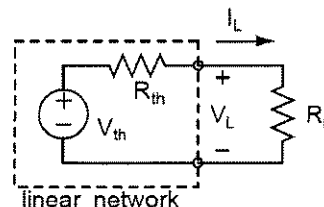- **Maximum Power Transfer Theorem**  
 $\rightarrow$  power transferred to load resistor  $R_L$  is maximized when  $R_L=R_{th}$




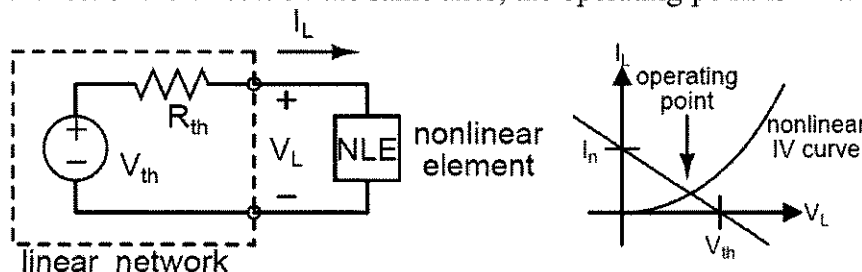- **Load-line Analysis** – graphical method solving circuits with 1 nonlinear circuit element  
 $\rightarrow$  graph the IV curves for the nonlinear circuit element and the Thevenin/Norton equivalent of the rest of the circuit on the same axes; the operating point is where the two curves intersect


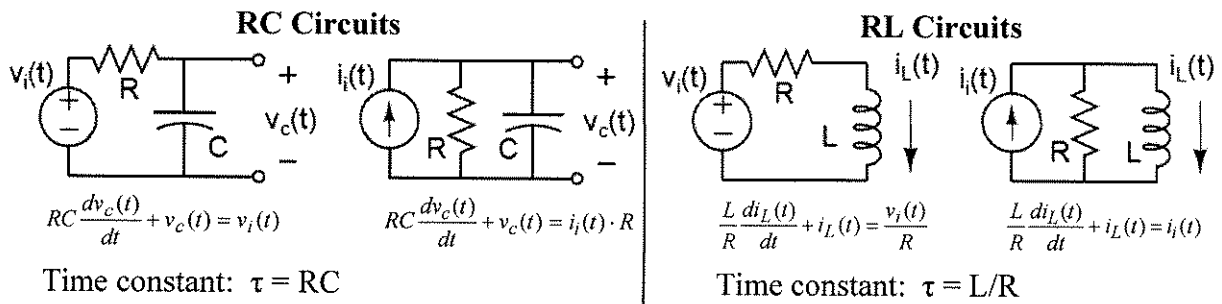
## V. FIRST-ORDER CIRCUITS

- **RC circuit** – contains only sources, resistors, and 1 capacitor
- **RL circuit** – contains only sources, resistors, and 1 inductor  
→ voltages and currents are described by 1<sup>st</sup>-order ODE (ordinary differential equation)



### • Time-domain Analysis for 1<sup>st</sup>-order Circuits

1. Write the ODE in terms of the variable of interest  $X(t)$ , using KCL/KVL and IV relationships for R, L, C.
2. Find the **homogeneous solution**  $X_h(t)$  by setting input to 0 and substituting  $X_h(t) = Ke^{-t/\tau}$  as the solution to find the time constant  $\tau$  ( $\tau = RC$  for RC circuit and  $\tau = L/R$  for RL circuit).  
(Note: The value of K cannot be found until the complete solution is found in Step 4.)
3. Find the **particular solution**  $X_p(t)$ . Remember the output follows the form of the input:

input function	constant	exponential	sinusoid
particular solution	A	$Ae^{-at} + B \cdot te^{-at}$	$A \cos(wt) + B \sin(wt)$

Guess the form of the solution and solve the ODE to find any arbitrary constants.

(Note: For sinusoidal inputs, the particular solution can be found more easily using complex impedance.)

4. Combine the homogeneous and particular solutions to get the complete solution:  $X(t) = X_h(t) + X_p(t)$ . Use the initial conditions to find the missing variables (i.e., the K in  $X_h(t)$ ).

Example: Find  $v_c(t > 0)$  for RC circuit w/  $v_i(t) = V_{DD}$ ,  $v_c(0^-) = 0V$ .

- 1)  $RC \frac{dv_c(t)}{dt} + v_c(t) = v_i(t)$       2)  $v_{c,h}(t) = Ke^{-t/\tau} \rightarrow RC \left( -\frac{K}{\tau} \right) e^{-t/\tau} + Ke^{-t/\tau} = 0 \rightarrow \tau = RC$
- 3) Since  $v_i(t)$  is a constant, guess  $v_{c,p}(t) = A$ . Plugging into the ODE,  $A = V_{DD} = v_{c,p}(t)$ .
- 4)  $v_c(t) = v_{c,h}(t) + v_{c,p}(t) = Ke^{-t/\tau} + V_{DD}$ .  $v_c(0^-) = v_c(0^+)$  by capacitor voltage continuity.  
 $v_c(0) = 0 = K + V_{DD} \rightarrow K = -V_{DD}$ . So,  $v_c(t) = V_{DD} - V_{DD}e^{-t/\tau}$ .

Note:  $X_h(t)$  represents the **transient response** of the circuit and should decay to 0 as time passes.  $X_p(t)$  represents the **steady-state response** of the circuit which persists after the transients have died away and which takes the form of the input.

- **Time constant  $\tau$**  – amount of time for the transient exponential response  $e^{-t/\tau}$  to decay by 63% ( $e^{-1} = 0.63$ ). In 5 time constants, the response decays by 99%. Faster circuits have smaller  $\tau$ .
- **General 1<sup>st</sup>-order Transient Response for Voltage/Current Step**

$$X(t) = X_f + [X(t_0^+) - X_f] e^{-(t-t_0^+)/\tau} \quad (X \text{ is any voltage or current in the circuit})$$

$X_f$  = final value,  $t_0$  = time voltage/current step occurred

(1) Find initial value  $X(t_0^+)$  and final value  $X_f$ . Use continuity ( $x(0^-) = x(0^+)$ ) and steady-state rules (open/short) for cap/ind. (2) Calculate  $\tau$  ( $\tau = RC$  for RC circuit,  $\tau = L/R$  for LR circuit).  $R$  is the Thevenin equivalent resistance “seen” by the cap/ind.

## VI. SECOND-ORDER CIRCUITS


- **RLC circuit** – contains only sources, resistors, 1 capacitor, and 1 inductor  
→ voltages and currents are described by 2<sup>nd</sup>-order ODE (ordinary differential equation)

General 2<sup>nd</sup>-order ODE:  $\frac{d^2 x(t)}{dt^2} + 2\alpha \frac{dx(t)}{dt} + \omega_o^2 x(t) = f(t)$

$\alpha$  = damping coefficient,  $\omega_o$  = undamped natural freq (AKA resonant freq)


$\zeta = \alpha/\omega_o$  = damping ratio,  $f(t)$  = forcing function (related to the input)

### Series RLC Circuit

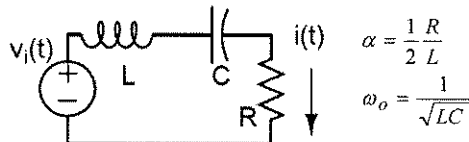

$$\frac{d^2 i(t)}{dt^2} + \frac{R}{L} \frac{di(t)}{dt} + \frac{1}{LC} i(t) = \frac{1}{L} \frac{dv_i(t)}{dt}$$

### Parallel RLC Circuit

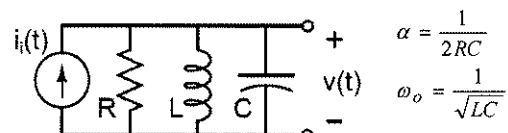

$$\frac{d^2 v(t)}{dt^2} + \frac{1}{RC} \frac{dv(t)}{dt} + \frac{1}{LC} v(t) = \frac{1}{C} \frac{di_i(t)}{dt}$$

### • Time-domain Analysis for 2<sup>st</sup>-order Circuits

1. Write the ODE in terms of the variable of interest  $X(t)$ , using KCL/KVL and IV relationships for R, L, C.
2. Obtain the **characteristic equation** by setting the input to 0 and substituting  $X(t) = Ke^{st}$  into the ODE:  $s^2 + 2\alpha s + \omega_o^2 = 0$ . Find  $\alpha$  and  $\omega_o$ . The roots of the characteristic equation are  $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_o^2}$ ; the form of the solution depends on the damping ratio  $\zeta = \alpha/\omega_o$ .
3. Find the **homogeneous solution**  $X_h(t)$  depending on  $\zeta$ :

*overdamped:*  $\alpha > \omega_o, \zeta > 1$   $X_h(t) = K_1 e^{(-\alpha + \sqrt{\alpha^2 - \omega_o^2})t} + K_2 e^{(-\alpha - \sqrt{\alpha^2 - \omega_o^2})t}$

*critically damped:*  $\alpha = \omega_o, \zeta = 1$   $X_h(t) = K_1 e^{-\alpha t} + K_2 t e^{-\alpha t}$

*underdamped:*  $\alpha < \omega_o, \zeta < 1$   $X_h(t) = K_1 e^{-\alpha t} \cos(\omega_n t) + K_2 e^{-\alpha t} \sin(\omega_n t)$

$\omega_n = \sqrt{\omega_o^2 - \alpha^2}$  = damped natural frequency

(Note: The value of  $K_1$  and  $K_2$  cannot be found until the complete solution is found.)

4. Find the **particular solution**  $X_p(t)$ . Remember the output follows the form of the input:

input function	constant	exponential	Sinusoid
particular solution	A	$Ae^{-\alpha t} + B \cdot te^{-\alpha t}$	$A \cos(\omega t) + B \sin(\omega t)$

Guess the form of the solution and solve the ODE to find any arbitrary constants.

(Note: For sinusoidal inputs, the particular solution can be found more easily using complex impedance.)

5. Combine the homogeneous and particular solutions to get the complete solution:  $X(t) = X_h(t) + X_p(t)$ . Use the initial conditions to find the missing variables (i.e.,  $K_1, K_2$  in  $X_h(t)$ ).

## VII. SINUSOIDAL STEADY-STATE ANALYSIS

Any steady-state (SS) voltage or current in a linear time-invariant (LTI) circuit with a sinusoidal input source is sinusoidal with the same frequency. Only the magnitude and phase (relative to the source) may be different.

- **Phasors** – vectors (i.e., complex numbers) that represent sinusoids. Since all V,I in the circuit are sinusoids with the same frequency, only magnitude & phase are needed to describe any V,I sinusoids:  $v(t) = V\cos(\omega t + \theta) = \text{Re}[Ve^{j(\omega t + \theta)}] = \text{Re}[Ve^{j\theta}e^{j\omega t}] \rightarrow$  phasor:  $Ve^{j\theta} = V\angle\theta$   
 $v(t) = V\sin(\omega t + \theta) = V\cos(\omega t + \theta - \pi/2) \rightarrow$  phasor:  $V\angle(\theta - \pi/2)$

$\rightarrow$  For convenience, define phasors in terms of cosine (i.e., the real part of a complex exponential)

- Euler's Identity:  $e^{jx} = \cos(x) + j\sin(x)$ ,  $\cos(x) = \frac{1}{2}(e^{jx} + e^{-jx})$ ,  $\sin(x) = \frac{1}{2j}(e^{jx} - e^{-jx})$
- Differentiation/integration become algebraic operations w/ phasors (i.e., complex exponentials)

$$\frac{d}{dt} \Leftrightarrow j\omega \quad \int dt \Leftrightarrow \frac{1}{j\omega} \quad \text{Ex: } \frac{d}{dt}(e^{j(\omega t + \theta)}) = j\omega e^{j(\omega t + \theta)}$$

- **Capacitor Impedance:**  $Z_C = \frac{1}{j\omega C}$   $\rightarrow$  ICE – Current (I) LEADS Voltage (EMF) by  $90^\circ$


- **Inductor Impedance:**  $Z_L = j\omega L$   $\rightarrow$  ELI – Voltage (EMF) LEADS Current (I) by  $90^\circ$

- **Complex Impedance/Generalized Ohm's Law:**  $Z = \frac{V}{I}$

$\rightarrow$  allows for easy nodal analysis (no differential equations); series/parallel resistor laws apply

- **Maximum Average Power Transfer Theorem**

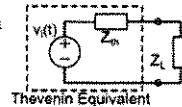$\rightarrow$  power transferred to load impedance  $Z_L$  is maximized when  $Z_L = Z_{th}^*$



- **Decibel (dB)** – unit of measure for ratios of power, voltage, and current levels (often used to express gain). Power:  $1\text{dB} = 10\log_{10}(P_1/P_2)$ ; V,I:  $1\text{dB} = 20\log_{10}(V_1/V_2) = 20\log_{10}(I_1/I_2)$

- **Frequency Response** – system's input  $\rightarrow$  output transfer function vs. frequency (given sinusoidal input). Both magnitude and phase plots are needed (output freq = input freq)

◦ General transfer function – can be written as a product of poles and zeroes

$$H(\omega) = Ae^{j\theta} \cdot (j\omega)^n \cdot \frac{(1 + j\omega/\omega_{z1})(1 + j\omega/\omega_{z2}) \dots}{(1 + j\omega/\omega_{p1})(1 + j\omega/\omega_{p2}) \dots}$$


- **zeroes** – roots of the numerator
- **poles** – roots of the denominator

◦ **Break point frequency**  $\omega_{BP}$  – poles and zeros are break point freq's

$\rightarrow$  at a zero frequency, the magnitude is  $+3\text{dB}$  ( $=\sqrt{2}$ ) and the phase is  $+45^\circ$

$\rightarrow$  at a pole frequency, the magnitude is  $-3\text{dB}$  ( $=1/\sqrt{2}$ ) and the phase is  $-45^\circ$

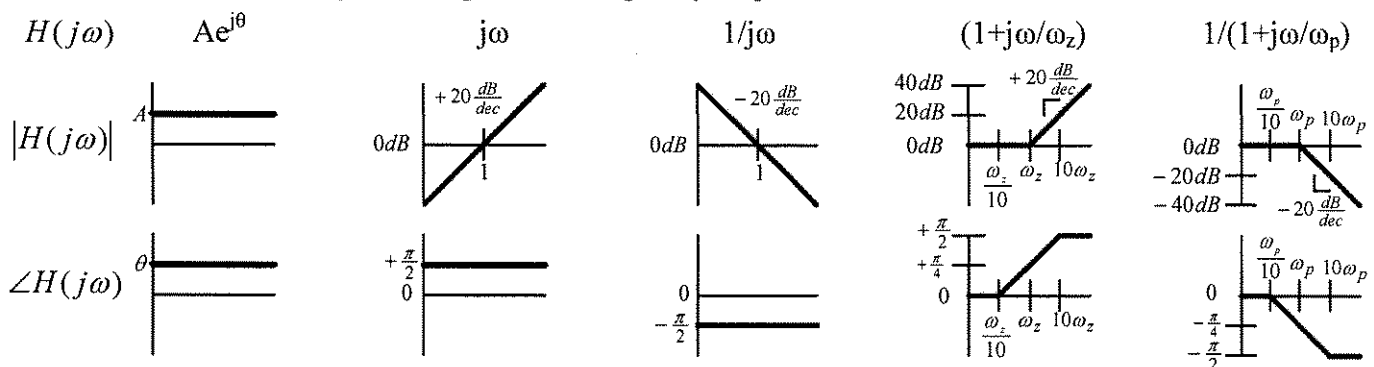
- **Bode Plot** – logarithmic plots for frequency response




◦ to draw Bode plot for general transfer function, add individual pole and zero plots
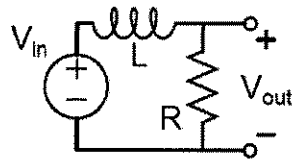
## • Filters


- Lowpass Filter (LPF) –  $V_C$  in RC circuit /  $V_R$  in RL circuit /  $V_C$  and RLC circuit  
(for current output, switch from series to parallel and switch L and C)


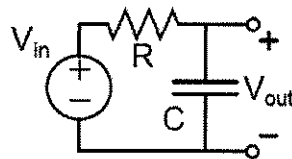
$$H(\omega) = \frac{V_{out}}{V_{in}} = \frac{1}{1+j\omega L/R}$$



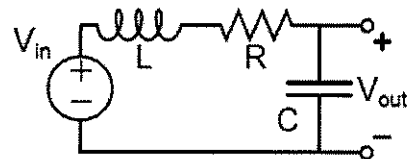
$$H(\omega) = \frac{V_{out}}{V_{in}} = \frac{1}{1+j\omega RC}$$




$$H(\omega) = \frac{V_{out}}{V_{in}} = \frac{1}{1+j\omega RC+(j\omega)^2 LC}$$

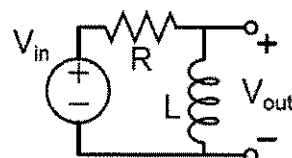
- Highpass Filter (HPF) –  $V_L$  in RL circuit /  $V_R$  in RC circuit /  $V_L$  in RLC circuit  
(for current output, switch from series to parallel and switch L and C)


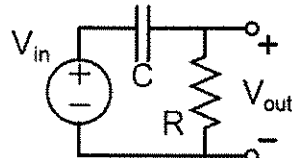
$$H(\omega) = \frac{V_{out}}{V_{in}} = \frac{j\omega L/R}{1+j\omega L/R}$$



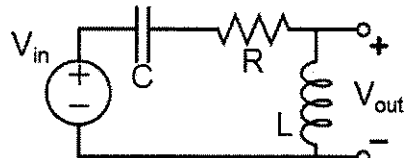
$$H(\omega) = \frac{V_{out}}{V_{in}} = \frac{j\omega RC}{1+j\omega RC}$$





$$H(\omega) = \frac{V_{out}}{V_{in}} = \frac{(j\omega)^2 LC}{1+j\omega RC+(j\omega)^2 LC}$$

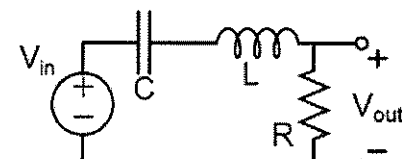- Bandpass Filter (BPF) –  $V_R$ ,  $I_R$  in RLC circuit


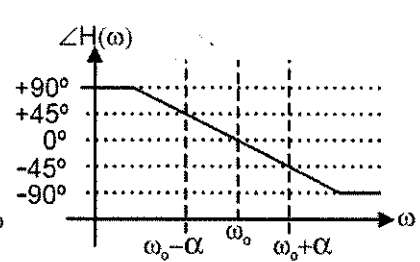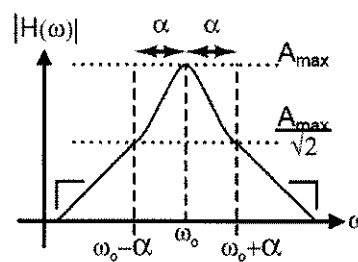
$$H(\omega) = \frac{V_{out}}{V_{in}} = \frac{j\omega RC}{1+j\omega RC+(j\omega)^2 LC}$$



→ at low freq, cap. impedance  $Z_C = \frac{1}{j\omega C}$  dominates →  $I = \frac{V_{in}}{Z_{tot}} \approx \frac{V_{in}}{Z_C} = j\omega C V_{in}$ ,  $V_{out} = IR \approx j\omega RC V_{in}$

→ at high freq, ind. impedance  $Z_L = j\omega L$  dominates →  $I = \frac{V_{in}}{Z_{tot}} \approx \frac{V_{in}}{Z_L} = \frac{V_{in}}{j\omega L}$ ,  $V_{out} = IR \approx \frac{V_{in}}{j\omega L/R}$

- Resonant Frequency  $\omega_o = \frac{1}{\sqrt{LC}}$

→ At  $\omega_o$ ,  $Z_C = \frac{1}{j\omega_o C} = -j\sqrt{\frac{L}{C}} = -jZ_o$ ,  $Z_L = j\omega_o L = +j\sqrt{\frac{L}{C}} = +jZ_o$  →  $V_{out} = V_{in}$

(capacitor and inductor impedances are equal in magnitude, opposite in sign)

→ Characteristic Impedance:  $Z_o = \sqrt{L/C}$

- BPF Bandwidth  $\Delta\omega = 2\alpha$  = difference between half-power frequencies

- Quality Factor Q – (1) measure of “peakiness” or filter selectivity (high Q → low bandwidth)  
(2) measure of energy stored vs. energy dissipated (high Q → low loss)

$$Q = \frac{\omega_o}{\Delta\omega} = \frac{\omega_o}{2\alpha} = \frac{1}{2\zeta} \quad \text{series RLC: } Q = \frac{Z_o}{R} = \frac{\sqrt{L/C}}{R} \quad \text{parallel RLC: } Q = \frac{R}{Z_o} = \frac{R}{\sqrt{L/C}}$$

Tradeoffs: Bandwidth/selectivity/speed/energy loss

(e.g., high Q → low  $\Delta\omega$  (high selectivity) → low  $\alpha$  → slow transients  $e^{-\alpha t}$ )